

Méthodologie de conception et langages de description matérielle

VHDL

Support de cours

Master SECIL

François Thiebolt
Daniela Dragomirescu


RISC - V

FF
PP
GG
AA

UE-SSM | Plan


Part I - VHDL language

Part Ia - SystemVerilog language (upcoming)

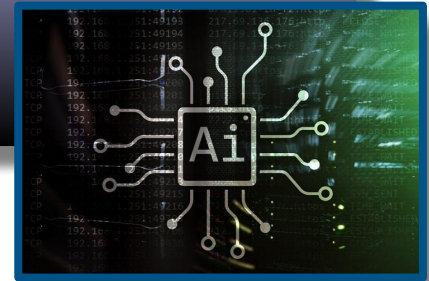

Part II - Synthesis for FPGA targets

Part IIa - [Advanced] Xilinx Zynq architecture

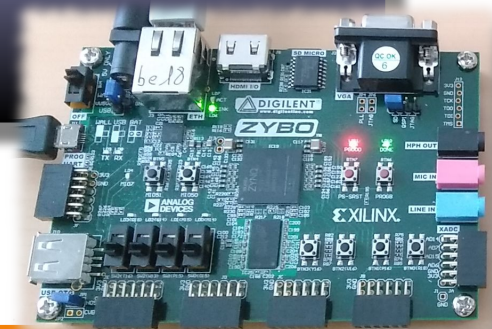


Part III - Electronics for dummies all :)

This course → https://secil.univ-tlse3.fr/teaching/francois/UE-VHDL/VHDL_course.pdf

Foreword

- HDL & friends | The big picture

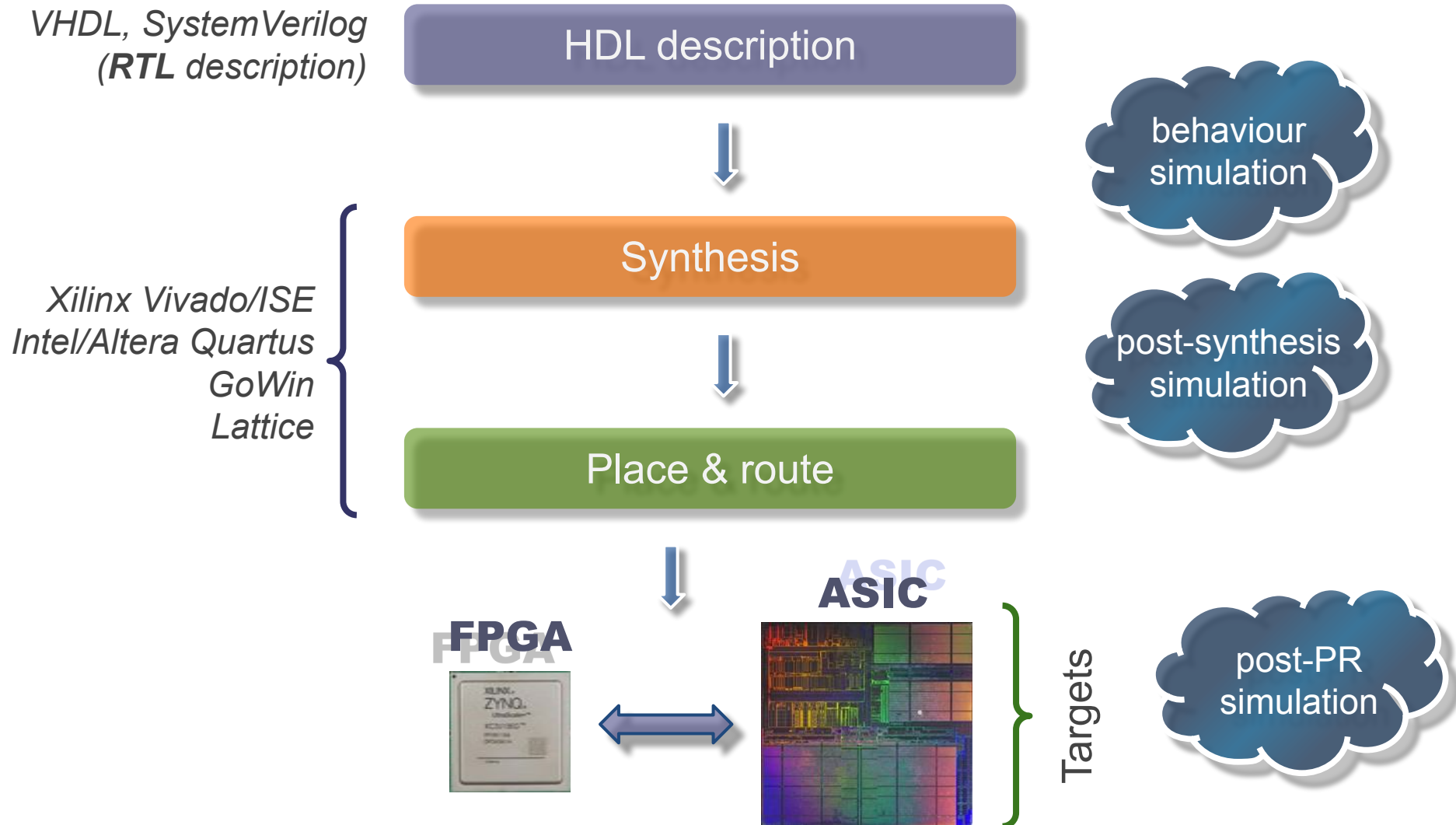

Foreword

- ... one step beyond



VIVADO

export
Hardware



FSBL



uboot



linux kernel with
Zynq support +
DTB



ARMBIAN
ARM rootFS




Linux on Zynq with HW
accelerated features 😊

Foreword

For those who can't stand waiting for things to come ...

Sipeed Tang Nano 4K/9K/20K

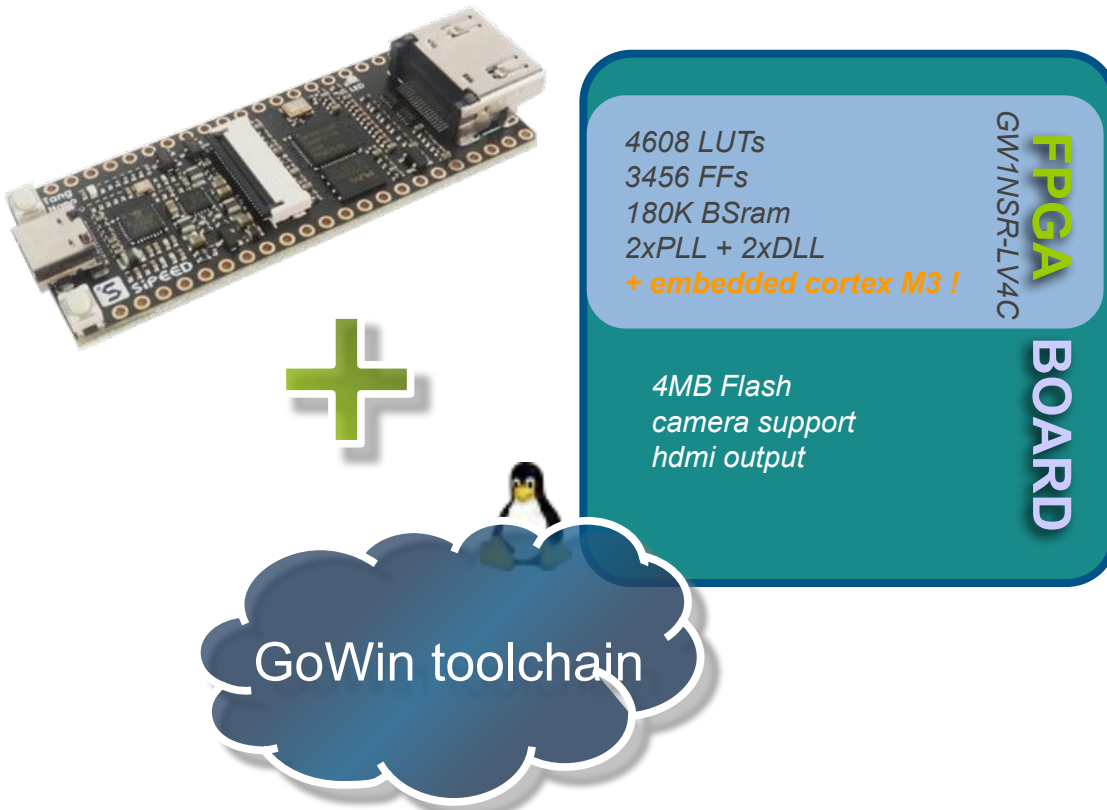

<https://tangnano.sipeed.com/en/>



Additional online resources like
<https://edaplayground.com>




What's all this VHDL stuff, Anyhow* ?

Part I - VHDL language

- Introduction,
- VHDL basics,
- Exercises.

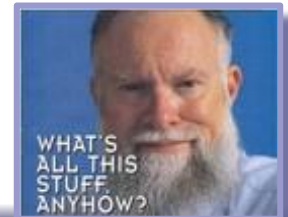**Robert Allen Pease [1940 - 2011] was a famous TI's analog engineer,
his favourite programming language was ... solder!*



Introduction

Rappels :

- Circuits logiques combinatoires

Leur sortie est déterminé par la valeur courante de l'entrée:
portes logiques, multiplexeurs, démultiplexeurs, décodeurs, circuits arithmétiques


- Circuits logiques séquentielles

Leur sortie est partiellement déterminée par l'évolution de l'entrée. La réponse du circuit dépend de l'histoire plus ou moins récente du fonctionnement du circuit.

Fonction **MÉMOIRE** interne:





Bascule D, registres, mémoires RAM, compteurs

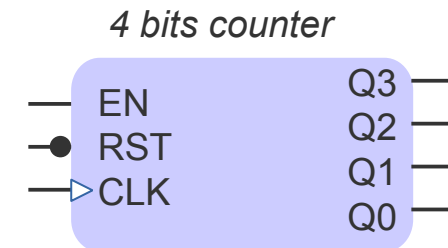- Exercice : réalisez un compteur 4 bits en utilisant des bascules D en logique séquentielle synchrone



Introduction

Rappels : D flip-flop vs D latch

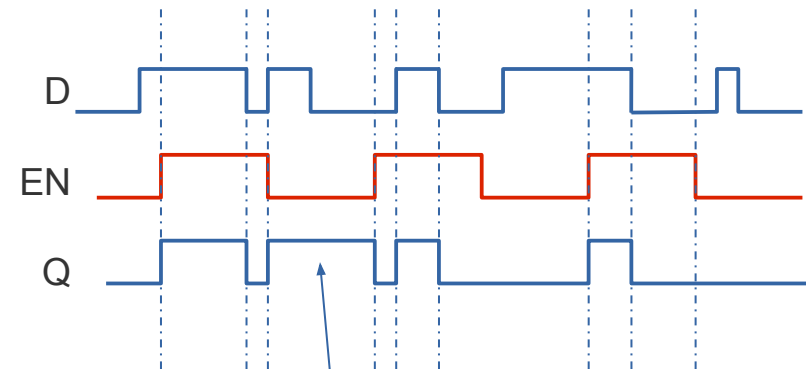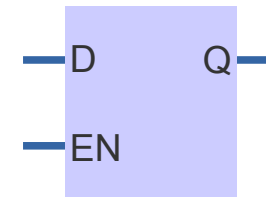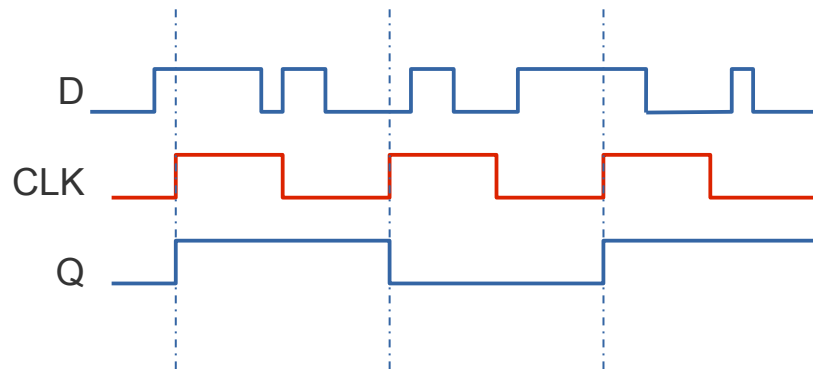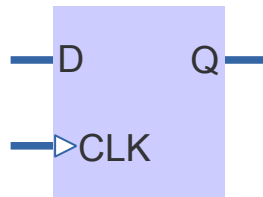


*Unsure about the output ...
guess why ??*

Introduction


Rappels :

- Totem-pole (*push-pull*) output

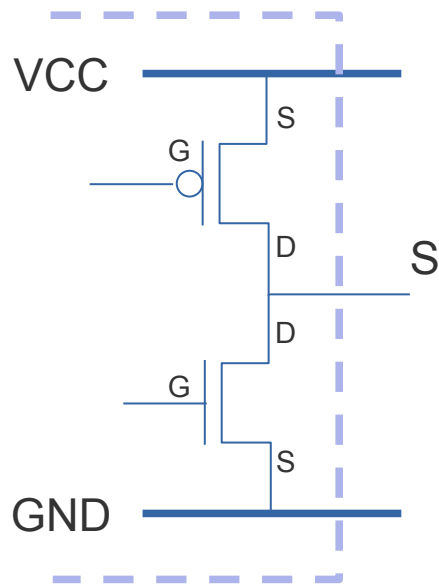

Note: same design with bipolar transistors

- Open-Drain / Open-Collector output

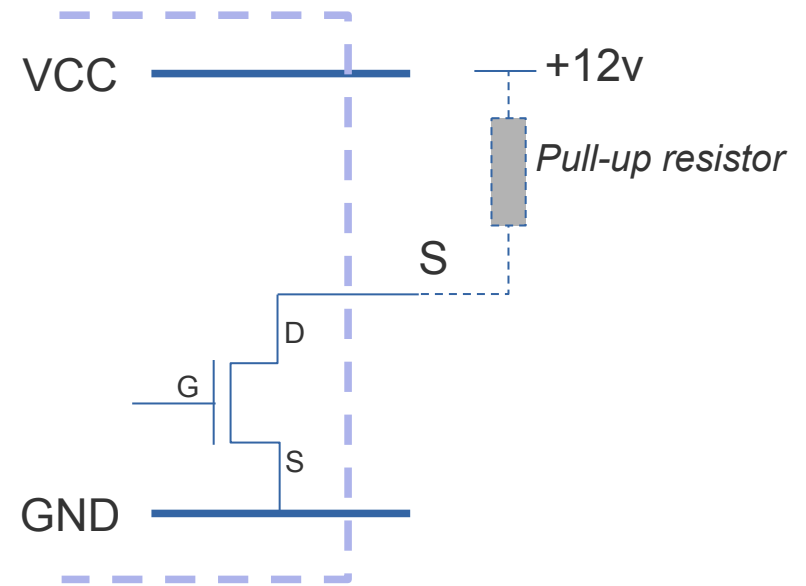

Note: same design with bipolar transistors

Introduction

- Évolution des puces

Chips	Year	Frequency	Transistors	Tech.
Intel 8086	1978	8 MHz	29K	3.2µm
Intel 80486 DX	1989	25 MHz	1.2M	1µm
Pentium III XEON	1999	700 MHz	28M	180nm
Pentium IV	2001	1.7 GHz	42M	180nm
Core i7 Westmere	2010	3.2 GHz	1.17B	32nm
nVidia GT400	2010		3B	40nm
nVidia Tesla V100	2017		21.1B	12nm
ARM Cortex A-76 (Kirin 990)	2019	2.86 GHz	10.3B	7nm
Apple M1	2020	3.1 GHz	16B	5nm
Apple M2	2023	3.5 GHz	20B	5nm
SiFive P670 RISC-V (IP)	2023	> 3GHz		5nm

Intel's XEON family starts to feature FPGA :)

2018



Introduction

- Accroissement de la complexité des puces:

Impose une évolution des méthodes des conception:

→ *la demande viendra du département de la défense des États-Unis en 1980:*

ADA pour le logiciel, VHDL pour le matériel.

Apparition des langages HDL - **H**ardware **D**escription **L**anguage

Verilog
VHDL

Même principe, syntaxe différente.

Sont des langages de niveau **Register **T**ransfert **L**evel**

Ces langages 'décrivent' le matériel, ils n'exécutent rien!

Travail avec des cellules standard - briques de base appartenant à une bibliothèque spécifique à chaque fondeur de circuits intégrés



Standard cells - design kit



Introduction

- VHDL: pro

VHDL est standardisé - standard IEEE

pérennité assurée par la norme

conception modulaire et hiérarchique

VHDL est un langage moderne, puissant et général

haute modularité

sécurité d'emploi

fiabilité

notion de temps bien définie

unités de compilation séparées

typage fort

généricité

En utilisant VHDL on minimise le risque d'erreur sur le circuit intégré en silicium - on diminue le coût de production

- VHDL: cons

langage de simulation



tout n'est pas synthétisable !



Introduction

- Standardization

- ✦ IEEE VHDL'87 - 1987

- ✦ IEEE VHDL'93 - 1993

- ✦ IEEE VHDL'03 - 2003

- ✦ IEEE VHDL'08 - 2008

Specifications


Simulator

Synthesis tools ! →


Never forget the overall objective: to produce chips through the use of synthesis tools!

Quick start

- VHDL: D flip-flop vs D latch

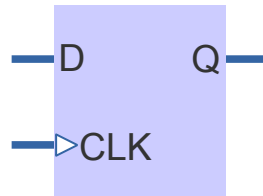


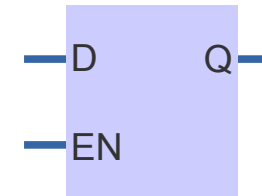
```
process( CLK )  
begin  
    if CLK'event and CLK='1' then  
        Q <= D;  
    end if;  
end process;
```



```
process( D, EN )  
begin  
    if EN='1' then  
        Q <= D;  
    end if;  
end process;
```

Quick start

- VHDL: 4 bits counter

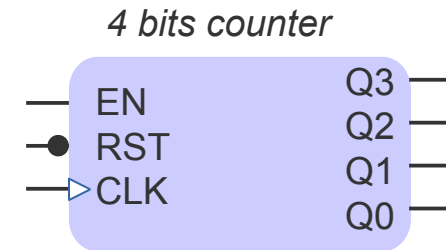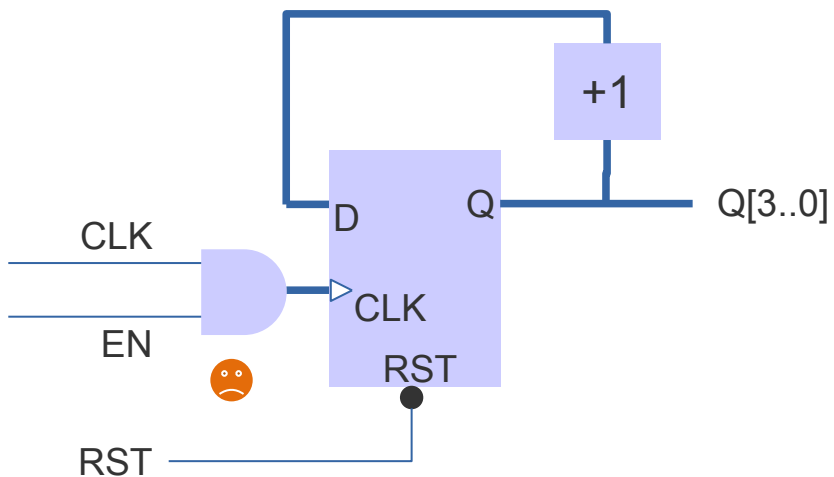


```
process( RST,CLK )
    variable cpt:std_logic_vector(3 downto 0);
begin
    if RST='0' then
        cpt := (others=>'0');
    elsif CLK'event and CLK='1' and EN='1' then
        cpt := cpt + '1';
    end if;
end process;
```

Some adjustment required ... we'll discover later.

Plan

Part I - VHDL language

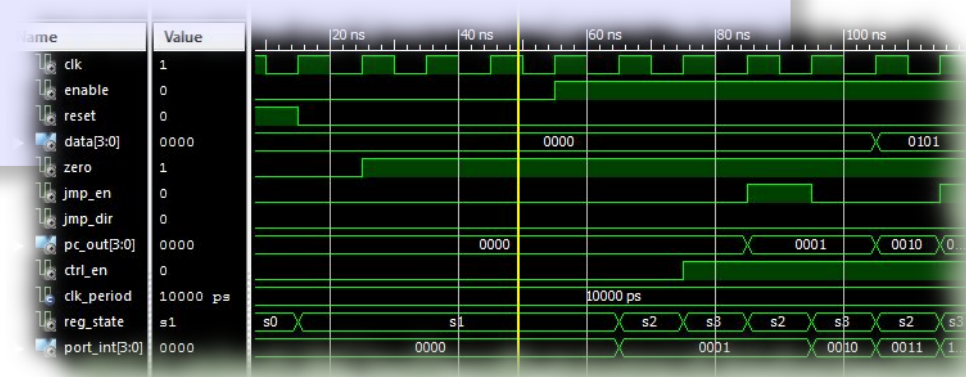- Introduction,
- VHDL basics,
- Exercises.





VHDL basics

Language features

- Packages

Along with package_body will hold all of your **types**, **constants**, **functions** and **procedures** definitions.

- Libraries

IEEE_std_logic_1164 is a compiled package provided as a system library.
Your compiled stuff will go in your **WORK** library.

- Entity + Architecture of components

For each of your components: **entity** + **architecture** descriptions.

- Configurations

For each instantiated component, you can specify an architecture;
e.g: behaviour, synthesized, routed.

- Tests architecture

Yes, it's like a component with an empty **entity** (usually) along with instantiated components you want to test in its **architecture**.



VHDL basics

- Libraries

Langage modulaire - unités petites et hiérarchisées

Unités de conception - peuvent être compilées séparément

Description VHDL correcte - bibliothèque de travail - **WORK**
portabilité

Utilitaires ou modèles généraux - bibliothèques de ressources
facilite le travail en équipe

Bibliothèques : IEEE , STD

package IEEE.std_logic_1164 et **package** IEEE.std_logic_arith


package STD.textio et **package** STD.STANDARD

VHDL basics

- Unités de conception: **entity**

Entité - modèle VHDL

Vue externe

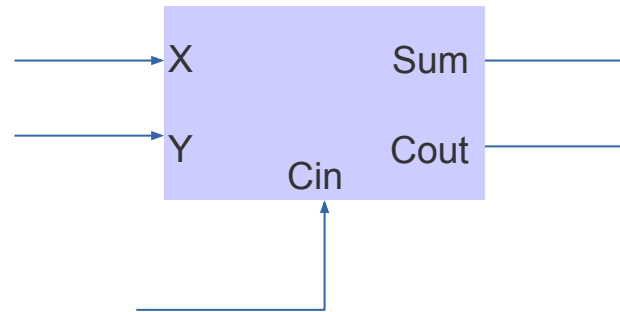

```
entity myadder is
    port (
        X, Y, Cin:    in std_logic;
        Sum, Cout:    out std_logic );
end myadder;
```


VHDL basics

- ports modes


Formal def. vs Connected object	Mode IN	Mode OUT	Mode INOUT	Mode BUFFER
Port de mode IN	✓			
Port de mode OUT		✓		
Port de mode INOUT	✓	✓	✓	
Port de mode BUFFER	✓			✓
Local signal	✓	✓	✓	✓
open keyword (not connected)		✓	✓	✓

VHDL basics

- ports modes: **BUFFER** vs **INOUT**

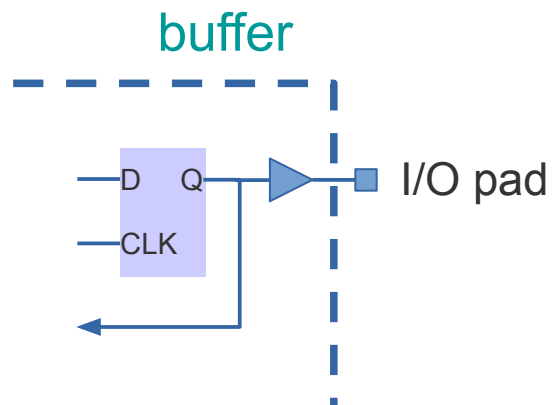

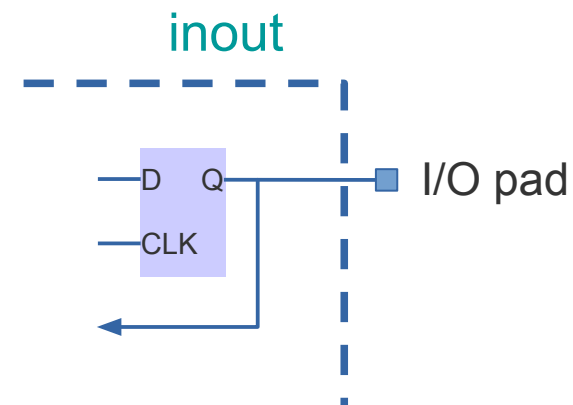Output pin is buffered: you can **read what you wrote** but you can't read the value of the pin.




The value on the pin may differ from what you wrote !

VHDL basics

- Unités de conception: **architecture**

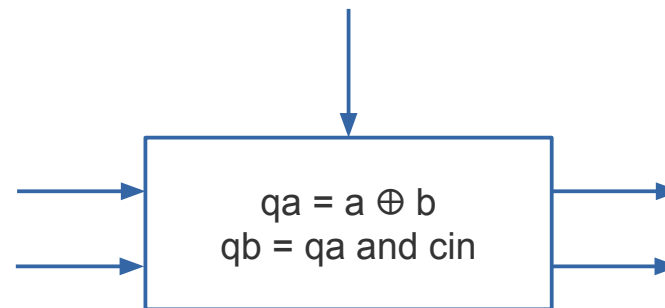Vue interne d'une entité - **ARCHITECTURE**



Style de description de l'architecture :

- Description **structurelle** : interconnexion de composants
- Description **flot de données** : comportement sous forme d'équations
- Description **comportementale** : comportement sous forme algorithmique

On peut combiner les différents styles de descriptions dans une même architecture.

*La synthèse produit une description **structurelle**.*

VHDL basics

- Architecture **structurelle** de l'additionneur

```
architecture vue_structurale of myadder is
```

```
    signal a,b,c : std_logic;
```


```
begin;
```

```
    U1:entity work.adder(behaviour)  
        port map(X,Y,a,b);
```

```
    U2:entity work.adder(behaviour)  
        port map(b,Cin,c,Sum);
```

```
    U3:entity work.or_gate(behaviour)  
        port map(a,c,Cout);
```

```
end vue_structurale;
```

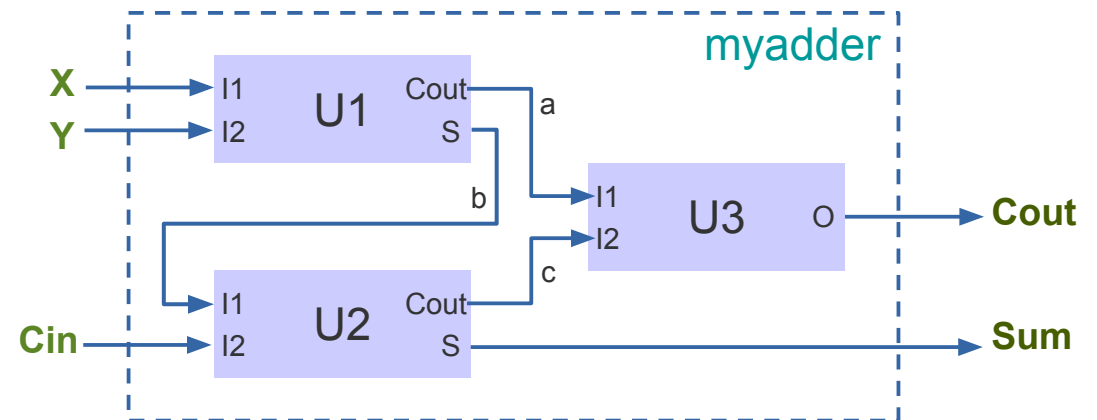



VHDL basics

- Architecture **flot de données** de l'additionneur

$$\begin{aligned} S &= X \oplus Y \\ \text{Somme} &= S \oplus \text{Cin} \\ \text{Cout} &= X.Y + S.\text{Cin} \end{aligned}$$

Equations booléennes de l'additionneur

```
architecture data_flow of myadder is
    signal S : std_logic;
begin;
    Somme <= S xor Cin after 10 ns;
    S <= X xor Y after 10 ns;
    Cout <= (X and Y) or (S and Cin) after 20 ns;
end data_flow;
```

VHDL basics

- Architecture **comportementale** de l'additionneur décrite par une table de vérité

```
architecture vue_comportementale of myadder is  
begin;
```

```
    process -- instruction concurrente
```

```
        variable N: integer; 😞
```

```
        constant sum_vector: std_logic_vector(3 downto 0):= "1010";
```

```
        constant carry_vector: std_logic_vector(3 downto 0):= "1100";
```

```
    begin
```

```
        N:=0;
```

```
        if X= '1' then N:=N+1; end if;
```

```
        if Y= '1' then N:=N+1; end if;
```

```
        if Cin=1 then N:=N+1; end if;
```

```
        Somme <= sum_vector(N) after 20 ns;
```

```
        Cout <= carry_vector(N) after 30 ns;
```

```
        wait on X, Y, Cin;
```

```
    end process;
```

```
end vue_comportementale;
```

X	Y	Cin	Sum	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1



VHDL basics

- Configurations

Donne la correspondance entre le composant et le modèle dont il est instancié

Permet de faire la liaison entre des composants utilisés dans une architecture et leur réalisation effective

Ex: Soit une entité « trois_registres » avec une architecture « beh » ayant 3 registres R1, R2 et R3

```
use work.trois_registres;  
configuration alpha of trois_registres is  
  for beh  
    for R1,R2 : registre_8bit use entity work.registre_8bit(arch);  
    for R3 : registre_8bit use entity work.registre_8bit(decalage);  
  end for;  
end alpha;
```

alternative to apply the same architecture for all instantiated components:

```
FOR ALL : registre_8bit use entity work.registre_8bit(arch);
```

VHDL basics

- Configuration example for our adder

```
library work;
entity myadder is
    port (X, Y, Cin : in std_logic;
          Sum, Cout : out std_logic);
end myadder;
architecture vue_structurale of myadder is

    for all : adder use entity work.adder(beh);
    for all : or_gate use entity work.or_gate(struct);

    signal a,b,c : std_logic;
begin
    U1:entity work.adder(behaviour)
        port map(X,Y,a,b);
    U2:entity work.adder(behaviour)
        port map(b,Cin,c,Sum);
    U3:entity work.or_gate(behaviour)
        port map(a,c,Cout);
end vue_structurale;
```

```
library my_lib;

architecture ...

    for all : adder use entity my_lib.adder(beh);

begin
```



VHDL basics

- Packages

Ensemble des algorithmes, sous-programmes, nouveau types et sous-types, des objets: signaux et constantes (pas de variables)

Un ou plusieurs paquetage dans la même bibliothèque

2 unités de conception :

Spécification d'un paquetage - vue externe

présente tout ce qu'exporte le paquetage (algorithmes, objets, types)

Corps du paquetage - vue interne - *optionnel*

contient la description des algorithmes, déclarations locales des types, objets

Pour avoir accès à un paquetage il faut le référencer par une clause **use**

```
library IEEE;
```

```
use IEEE.std_logic_1164.all ;
```

```
library my_lib;
```

```
use my_lib.mon_paquetage.all;
```

- Packages

Spécification du paquetage :

```
package SIMPLE is
```

```
    constant TAILLE_MAX: integer :=1024;
```

```
    type mon_integer is INTEGER range 0 to TAILLE_MAX;
```

```
    signal addition_10bits : mon_integer ;
```

```
    function MIN(A,B:INTEGER) return INTEGER;
```

```
    function MAX(A,B:INTEGER) return INTEGER;
```

```
end SIMPLE;
```

Les déclarations faites dans la spécification du paquetage sont connues dans le corps du paquetage.

- Packages - **body**

Corps du paquetage

```
package body SIMPLE is
  function MIN(A,B:INTEGER) return INTEGER is
  begin
    if A<B then return A;
    else return B;
  end if;
end MIN;

  function MAX(A,B:INTEGER) return INTEGER is
  begin
    if B<A then return A;
    else return B;
  end if;
end MAX;
end SIMPLE;
```

- Concurrent and Sequential domains

La description d'un système matériel est naturellement concurrente.

Le fond d'une description VHDL est **concurrent**.

Les 2 domaines cohabitent en VHDL

Domaine **concurrent**

La zone de déclarations des **entités**

La zone de déclarations des **architectures**

Domaine **séquentiel**

La zone de déclarations de **processus**

Le **corps du paquetage**

VHDL basics

- Tests

Pour **vérifier** (**simuler**) le comportement du composant décrit en VHDL il faut le **tester**

Le programme de test - un programme VHDL, avec la même structure (entity, architecture)

Applique les stimuli en entrée et à vous de contrôler les sorties du composant en test (e.g assertions)

Si possible - test exhaustif

Difficile à mettre en œuvre pour des systèmes complexes


Preuve formelle

Create a test component **without I/O**

Instantiation of **your** component

Processes to generate a clock, inputs stimulus, asserts on outputs ...

architecture behaviour of test;

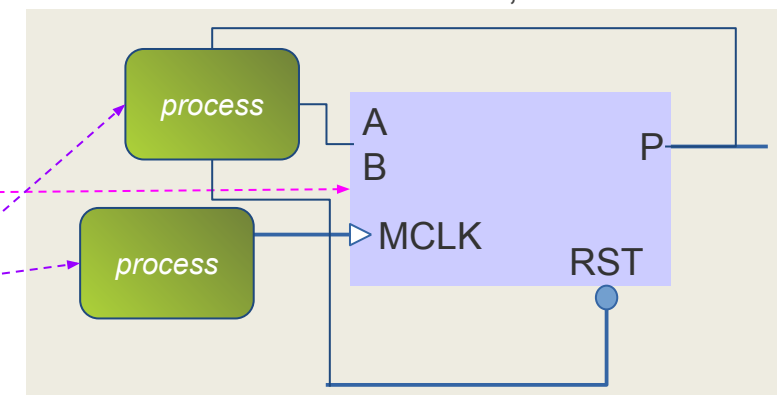



VHDL basics

Exemple: test de l'additionneur

```
entity test_adder is
end test_adder;

architecture bench of test_adder is
    For all : adder use entity work.adder(vue_structurale);

    signal data1, data2, data3 : std_logic;
    signal data_out, carry_out : std_logic;
begin
    additionneur: entity work.adder PORT MAP (data1,data2, data3,data_out,carry_out);
    data1 <= '0', '1' after 30 ns;
    data2 <= '1', '0' after 50 ns, '1' after 60 ns;
    data3 <= '0', '1' after 12 ns;
end bench;
```

Test non exhaustif !!

● Opérateurs et littéraux

Classes d'opérateurs par ordre de priorité croissante

1. Logiques : and or nand nor xor;

- défini sur les types booléen et BIT

2. Relationnels: = /= < <= > >=

- défini sur tous les types sauf le type file

3. Arithmétiques et concaténation: + - &

4. Signe: + -

- les opérateurs de signe sont moins prioritaires que les opérateurs de multiplication !!!!!

5. Multiplication: * / mod rem

6. Exposant, valeur absolue, complément: ** abs not

- ** élévation à la puissance : opérande de droite (la puissance) doit être entière

Il est possible de **surcharger** les opérateurs; ceci ne change pas leur priorité.



VHDL basics

- Opérateurs et **littéraux**

Classifications:

numérique - notation décimale - entier (1345 ou 1_345) ou réel (13.0)

- notation basée - base 16 : X"A2"

caractères ou chaîne de caractères ('a' , "Bonjour", "1234")

énumérés (type ALU_OPS is (ADD,SUB,ADDI,SUBU, ...))

chaînes de bits ("1010")

null

WARNING: 1 - nombre entier '1' - bit

Expressions - portent un type, et au moment de l'exécution une valeur

Identificateurs - ils commencent avec une lettre; pas de différence entre majuscules et minuscules.

- Objets

Les objets contiennent des valeurs. Il y a 4 classes d'objets en VHDL :
constantes, variables, fichiers et signaux.

Les constantes ont une valeur unique fixe

Les variables ont une valeur unique modifiable

Les fichiers contiennent des séquences de valeurs qui peuvent être lues ou écrites

Les **signaux** conservent l'histoire des valeurs passées, de la valeur présente et des valeurs prévues dans le futur : seules les valeurs futures peuvent être modifiées par affectation de signal

Tous les objets ont un type

- Types

VHDL est un langage typé

Un type est un ensemble de valeurs ordonnées

Le type est **statique** : il ne peut pas être modifié

Il est possible de définir de nouveaux types en utilisant les types prédéfinis et des constructeurs de types

Classification :

- Types scalaires

- Types composites

- Types **access** (pointeur) - seules **les variables** peuvent être de type access

- Types fichiers - mot clé **file**

- Types scalaires

Les entiers

```
type mon_integer is INTEGER range -65_536 to 65_535 ;
```

Les flottants

```
type mon_flottant is REAL range 5.36 downto 2.15;
```

Les types énumérés

```
type COULEUR is (BLEU, VERT, ROUGE);
```

```
type BOOLEAN is (FALSE, TRUE);
```

```
type LOGIC4 is ('X', '0', '1', 'Z');
```

Les types physiques

TIME - défini dans le paquetage STANDARD

TIME - la notion de temps que connaît le simulateur

Sont caractérisés par l'unité de base, l'intervalle de ses valeurs autorisées, collection des sous-unités et leur correspondance.



VHDL basics

- Types physiques

```
type TIME is range -9_223_372_036_854_775_808 to 9_223_372_036_854_775_807
```

```
-- codage sur 64 bits ;
```

```
units fs ;
```

```
ps = 1000 fs;
```

```
ms = 1000 us;
```

```
ns = 1000 ps;
```

```
sec = 1000 ms;
```

```
us = 1000 ns;
```

```
min = 60 sec ;
```

```
hr = 60 min;
```

```
end units;
```

```
type DISTANCE is range 0 to 1E16
```

```
units A ;
```

```
nm = 10 A;
```

```
um = 1000 nm;
```

```
mm = 1000 um;
```

```
cm = 10 mm;
```

```
m = 1000 mm;
```

```
km = 1000 m;
```

```
end units;
```

VHDL basics

- Type **STD_LOGIC**

Se trouve dans le paquetage IEEE.std_logic_1164

Paquetage IEEE.std_logic_unsigned

Paquetage IEEE.std_logic_arith

std_logic est le type **résolu** de std_u**l**ogic

u stands for unsolved ... not unsigned!

'1' – 1 *strong*

'0' – 0 *strong*

'Z' – high impedance

'U' – uninitialized

'X' – undetermined

'H' – 1 *weak*

'L' – 0 *weak*

'W' – *weak* unknown

STD_LOGIC_VECTOR


```
signal A,B : std_logic_vector(7 downto 0);
```

```
signal mycpt: std_logic_vector(0 to 3);
```

std_logic resolution function

A	B	out
'1'	'Z'	'1'
'0'	'H'	'0'
'0'	'1'	'X'
'H'	'L'	'W'
...	...	...

array of std_logic

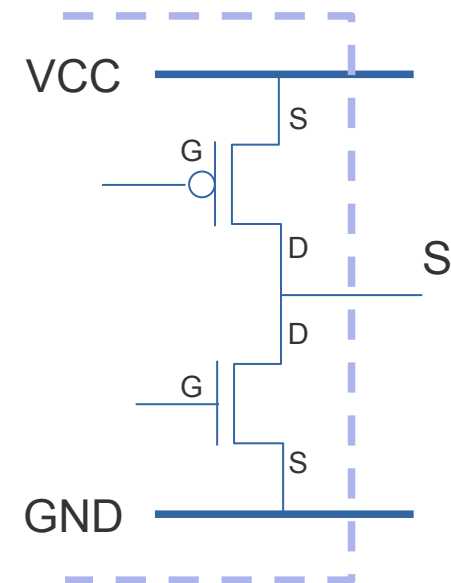



VHDL basics

- Types composites

Classification :

Tableaux : collection d'objets de même type - **array**

Articles : collection d'objets de types différents - **record**

Tableaux

Ses éléments sont désignés par un indice:

- ❖ Constraint (un entier)

type MOT **is array** (*integer range* 0 to 31) **of** STD_LOGIC;

- ❖ Non-constraint

type STD_LOGIC_VECTOR **is array** (NATURAL **range <>**) **of** STD_LOGIC;

Définition d'un intervalle d'indiaçage lors de l'exécution

signal bus : STD_LOGIC_VECTOR (63 **downto** 0);

Attributs de tableaux :

LEFT, RIGHT, HIGH, LOW, RANGE, REVERSE_RANGE, LENGTH

```
type FILE_REGS is array(0 to (2**3)-1) of std_logic_vector(31 downto 0);  
signal regs : FILE_REGS;
```



VHDL basics

- Tableaux - **attributs**

Exemple :

```
type INDEX 1 is INTEGER range 1 to 20;
```

```
type INDEX2 is INTEGER range 7 downto 3;
```

```
type VECTEUR1 is array (INDEX1) of STD_LOGIC;
```

```
type VECTEUR2 is array (INDEX2) of STD_LOGIC;
```

VECTEUR1'**LEFT** rendra 1 et VECTEUR2'**RIGHT** rendra 3

VECTEUR1'**HIGH** rendra 20 et VECTEUR2'**HIGH** rendra 7

VECTEUR1'**LOW** rendra 1 et VECTEUR2'**LOW** rendra 3

VECTEUR1'**RANGE** rendra 1 to 20 - utilisation pour des boucles

VECTEUR1'**REVERSE_RANGE** rendra 20 **downto** 1

VECTEUR1'**LENGTH** rend le nombre d'éléments du tableau - donc 20



VHDL basics

- Types composites - articles

Articles - mot clé **record** - **end record**

Contient des éléments de types différents

Ses éléments sont désignés par un **nom**

Exemple :

```
type BIT_COMPLET is record
```

```
    valeur : std_logic;
```

```
    sortance_min, sortance_typ, sortance_max: integer;
```

```
end record;
```

```
signal A : BIT_COMPLET;
```

```
variable B : BIT_COMPLET;
```

alors A.valeur est de type `std_logic`, **A.sortance_typ** est de type entier

Affectation

```
A <= B ;
```

```
ou
```

```
A.valeur <= B.valeur after 50 ns;
```

● Aggrégats

Un agrégat est une façon d'indiquer la valeur d'un type composite

Un agrégat se note entre parenthèse, les éléments étant séparés par des virgules

Vérification de type faite par le compilateur

Exemple : soit

```
type TAB is array (1 to 3) of INTEGER ;
```

```
type ART is record
```

```
    Champ1 : NATURAL;
```

```
    Champ2 : STD_LOGIC;
```

```
    Champ3 : NATURAL;
```

```
end record;
```

```
signal A : TAB; signal B : ART;
```

3 notations distinctes de l'agrégat :

notation positionnelle

```
A <= (12, 13, 14);
```

```
B <= (5, '0', 15);
```

notation par denomination

```
A <= (1=>12, 2=>13, 3=>14);
```

```
B <=(Champ3 =>15, Champ1 => 5, Champ2 =>'0' );
```

notation mixte (positionnelle -denomination)

```
A <=(5, others =>0);
```

```
B <=(Champ2 =>'0', others =>0);
```

```
A <=(others =>0);
```

- Sous-types

Déclaration de sous-type quand on souhaite restreindre les valeurs d'un certain type

Un sous-type est toujours compatible avec son type de base

Exemples:

```
subtype integer_8bits is INTEGER range 0 to 255 ;
```

```
subtype NATURAL is INTEGER range 0 to INTEGER'HIGH;
```

Sous-types dynamiques:

Font intervenir des expressions calculables à la simulations

```
Subtype MOT is STD_LOGIC_VECTOR (1 to MAX);
```

ou MAX est un paramètre d'un sous-programme ou un paramètre générique d'une entité



VHDL basics

- Notions de signal et affectations du signal

Un signal correspond à la représentation matérielle du support de l'information en VHDL.

Un signal a une évolution dans le temps (une variable - non)

Toute déclaration de signal se fait dans le domaine concurrent - la zone de déclaration des architectures, des entités et la spécification du paquetage

Tout signal peut conserver l'historique de ses valeurs passées si celles-ci sont utilisées par ailleurs, la valeur présente et les valeurs prévues dans le futur - le «pilote » du signal

Affectation du signal :

- connexion à un port de sortie d'un composant

- affectation du signal dans le domaine concurrent

- affectation du signal dans le domaine séquentiel



VHDL basics

- Affectation inconditionnelle de signal

```
S <='0', '1' after 20 ns;
```

La valeur doit avoir un type compatible avec celui du signal affecté

Chaque élément de l'expression a une partie valeur et une partie délai de type physique TIME (délai nul par défaut sans la clause **after**)

```
S <= A after 10 ns ;
```

Tous les signaux utilisés dans l'expression sont soit locaux, soit des ports définis en entrée



VHDL basics

- Exécution d'une affectation de signal

L'affectation du signal ne change pas la valeur présente du signal, mais modifie les valeurs futures que ce signal sera susceptible de prendre

$A \leq B$; ou $A \leq B$ after 0 ns;

Le signal A prend la valeur présente du signal B après un delta délai

Delta délai - est un délai qui est nul pour la simulation et ne représente que la causalité des événements.



VHDL basics

- Exécution d'une affectation de signal

$S \leq A+B$ **after** 20 ns;

L'expression affectée à un signal est évaluée à chaque changement de valeur sur l'un de ses signaux d'entrée (réponse événementielle)

Chaque valeur calculée par l'expression est mémorisée dans le signal destination avec son délai d'apparition

Si l'affectation est de nouveau évaluée, les anciennes valeurs prévues pour le futur peuvent être remplacées par les nouvelles valeurs - voir exemple affectation conditionnelle



VHDL basics

- Affectation conditionnelle de signal

Condition simple:

```
S <= A when condition else  
      B;
```

Instruction conditionnelle concurrente

```
S <= A after 20 ns when condition else  
      B after 10ns;
```

Condition multiple avec ordre de précedence

```
S <= 5 when A='1' and B='1' else  
      4 when A='1' else  
      0;
```

Instruction conditionnelle concurrente

Quand n'importe quel signal d'entrée change de valeur,
l'ensemble des conditions est évalué dans l'ordre (de gauche à droite)



La première valeur produite par la première expression dont la condition est vraie est affectée au signal !

VHDL basics

- Affectation sélective de signal

Une condition unique détermine quelle expression sera affectée au signal

```
type alu_ops is (add, sub, and, xor);
```

```
signal opcode: alu_ops;
```

```
signal result, A, B, : std_logic;
```

```
with opcode select -- instruction de choix concurrente
```

```
    result <= A + B when add,  
              A - B when sub,  
              A and B when and,  
              A xor B when xor,  
              '0' when others;
```

```
result <= A + B when opcode==add else  
        A - B when opcode==sub else  
        A and B when opcode==and else  
        A xor B when opcode==xor;
```

L'affectation sélective modélise les composants de type multiplexeurs et décodeurs.

*not anymore a muxer ...
guess why ?*

VHDL basics

● Attributs

L'attribut est une caractéristique associée à un type ou à un objet

L'utilisateur peut définir des nouveaux attributs

aucune affectation du pilote.

Prédéfini :

S'**quiet**(T) - TRUE si le signal S est "tranquile" pendant au moins T

S'**stable**(T) - TRUE si aucun événement sur le signal S depuis T

S'**delayed**(T) - signal S différé de T après **NOW** ← des affectations au delà du temps T

S'**event** - TRUE si un événement vient d'arriver sur S

des affectations mais qui ne changent pas la valeur

S'**last_value** - dernière valeur de S avant le dernier événement

S'**last_event** - valeur du temps écoulé depuis le dernier événement de S

```
S <= transport A and B after 20ns;
```

also **inertial** and **reject** to model propagation on wires.



VHDL basics

- Variable vs Signal

Les variables se déclarent dans le **domaine séquentiel des processus ou des sous-programmes**

Les variables s'utilisent et s'affectent dans le domaine séquentiel uniquement `a := '1'`

Les signaux se déclarent dans le **domaine concurrent** des entités, architectures, spécification du paquetage, des blocs

Les signaux s'utilisent dans les 2 domaines séquentiel et concurrent
`a <= '1'`

Une affectation de variable est **immédiate**, alors qu'une affectation de signal est différée jusqu'à la fin de l'évaluation de toutes les affectations.

i.e lorsque l'on arrive à la fin d'un `process` ou lorsque l'on tombe sur une instruction `wait`

- Instructions concurrentes

On ne simule pas en temps « réel » - on simule en temps virtuel
(temps de simulation)

Ces fonctionnements seront décrits par des instructions concurrentes
s'exécutant de manière asynchrone

Assignations de signaux (conditionnelle ou sélective ou inconditionnelle)

Instanciations de composants

Instruction **processus**

Appels concurrents de procédures

Instructions d'assertion

Instructions de bloc

Instruction **generate**

- Instructions concurrentes

Processus

est l'objet fondamental manipulé par le simulateur

toute instruction concurrente peut toujours être traduite par un processus

un processus est sensible aux signaux

il contient que des instructions séquentielles

la durée de vie d'un processus est celle de la simulation; un processus est cyclique

e.g affectation dans le domaine concurrent:

```
S <= A + B;
```

est en fait un processus avec en liste de sensibilité les signaux situés en partie droite de l'affectation (i.e A, B)

VHDL basics

- Instructions concurrentes - **Processus**

```
{label: } process { liste_des_signaux_surveillés}  
  Déclarations  
  begin  
    Instructions séquentielles  
  end process {label};
```

liste de sensibilité

Les déclarations sont élaborés une seule fois, à l'initialisation
un processus s'exécute au moins une fois à l'initialisation jusqu'à
l'instruction **WAIT** (si elle existe)
à chaque événement intervenant sur un des signaux surveillés, le
processus va s'exécuter

Restrictions:

l'instruction **wait** bloque le processus – voir instruction **wait** plus loin

l'instruction **wait** ne peut s'utiliser à l'intérieur d'un processus que si
celui-ci ne possède pas de liste de signaux surveillés



VHDL basics

- Instructions concurrentes - **Processus**

Processus avec liste de sensibilité:

```
{label: } process( {watched_signals} )  
    Déclarations  
begin  
    Instructions séquentielles  
end process {label};
```

Not executed at initialization

Processus sans liste de sensibilité:

```
{label: } process  
    Déclarations  
begin  
    wait on {signaux_surveillés }  
    Instructions séquentielles  
end process {label};
```

Executed one time during initialization

- Instructions concurrentes

Block

réuni des instructions **concurrentes**

est la base de hiérarchie en VHDL

toute hiérarchie VHDL se ramène à un ou plusieurs blocs imbriqués

permet de garder des affectations de signaux - circuits synchrones

label : block

{ généricité et port }

... Déclarations ...

begin

....Instruction concurrentes

end block;

Appel concurrent de procédure

a la même syntaxe que l'appel séquentiel de procédure

**domaine concurrent - paramètres de la procédure ne peuvent être que de signaux
ou de constantes**

```
procedure alu(A:in std_logic_vector, ..., signal S: out std_logic,... );
```

Instruction concurrente d'assertion

- Instructions séquentielles

Domaine d'utilisation des instructions séquentielles : dans le corps d'un **processus** ou sous-programme

Instruction **WAIT**

Instruction **ASSERT**

Instructions d'affectation de variables et de signaux

Appel de procédures

Instructions conditionnelles

Instructions de contrôle

Instruction nulle - **null**

VHDL basics

- Instructions séquentielles

Instruction **WAIT**

L'exécution de processus ou de programme peut être suspendue en fonction d'une condition donnée et pour un temps indiqué par l'instruction **wait**

wait {**on** liste _signaux} {**until** condition_booléenne} {**for** temps};

Tout événement arrivant sur un signal de la liste donnée provoque l'évaluation de la condition booléenne.

Exemple:

Clock generator in a test architecture:

```
signal clk: std_logic;
.....
clock: process
begin
  clk <= '1';
  wait for 5ns;
  clk <= '0';
  wait for 5ns;
end process clock;
```

```
process
begin
  wait on CLK;
  if clk'event and CLK='1' then
    q <= d after 10 ns;
  end if;
end process;
```

```
process
begin
  wait until CLK'event and CLK ='1';
  q <= d after 10 ns;
end process;
```

wait until <condition>
attend un événement sur l'un des signaux
ET teste ensuite la condition !!



VHDL basics

- Instructions séquentielles

Instruction **ASSERT**

Surveille une condition et émet un message dans le cas où celle-ci est **fausse**.

L'exécution du programme reprend alors immédiatement derrière l'instruction d'assertion.

assert condition {**report** mesg} {**severity** niveau}

assert NOW<1 min report "Fin simu" severity ERROR;

Type Severity_Level is (note, warning, error, failure);

Timeout generator in a test architecture:

```
timeout: process
begin
    wait for 150ns;
    assert false report "Timeout !!!" severity failure;
end process timeout;
```

- Instructions séquentielles

Instructions d'affectation de variables et de signaux

```
Variable1 := 2;  
Signal1 <= 2 after 20 ns;
```

Appel de procedure

```
procedure alfa (nr : integer, msg : string) --définition de la procédure  
Alfa(4, "GO");                          --appel positionnel  
Alfa(nr =>4, msg =>"GO");
```

Instruction **return**

Réservée aux sous-programmes

Instruction nulle

null

l'exécution passe à la ligne suivante

L'instruction nulle n'est pas nécessaire à la compilation de processus ou de corps de procédures vides.

VHDL basics

- Instructions séquentielles

Instructions conditionnelles

```
if condition1 then traitement1
elsif condition2 then traitement2
else traitement3
end if;
```

Instructions de choix:

```
case expression is
  when val1 => instructions1
  when val2 => instructions2
  when others => instr3
end case;
```

e.g procedure alu

```
type ALU_OPS is (ALU_ADD, ALU_SUB, ALU_AND ...);
signal CTRL_ALU : ALU_OPS;
.....
case CTRL_ALU is
  when ALU_ADD | ALU_SUB | ALU_SLT =>
    b_in := B;
    c_in := '0';
    if (CTRL_ALU /= ALU_ADD) then
      b_in := not(B);
      c_in := '1';
    end if;
    adder_cla(A,b_in,c_in,tmp_S,tmp_C,tmp_V);
    if (CTRL_ALU = ALU_SLT) then
      tmp_S := .....
      tmp_C := '0';
      tmp_V := '0';
    else
      tmp_C := not(SIGNED_OP) and tmp_C;
      tmp_N := SIGNED_OP and tmp_S(DATA_WIDTH-1);
      tmp_V := SIGNED_OP and tmp_V;
    end if;
  when ALU_AND =>
    tmp_S := A and B;
    .....
  when others =>
    .....
end case;
```

VHDL basics

- Instructions séquentielles

Instructions de boucles

loop

instructions séquentielles;

end loop;

for indice **in** intervalle **loop**

instructions séquentielles;

end loop;

while condition **loop**

Instructions séquentielles;

end loop;

next label_de_boucle **when** condition --arrête l'itération en cours

exit label_de_boucle **when** condition

zero detector


```
signal reg:std_logic_vector(7 downto 0);
.....
process( reg )
    variable zero:std_logic := '1';
begin
    zero:='1';
    for i in reg'range loop
        if reg(i)/='0' then
            zero:='0';
            exit;
        end if;
    end loop;
    if zero='1' then ...
    end if;
end process;
```

... then the same using vector comparison :)

```
if reg/=conv_std_logic_vector(0,reg'length) then
    .....
end if;
```

Exercises

• Pulse generator

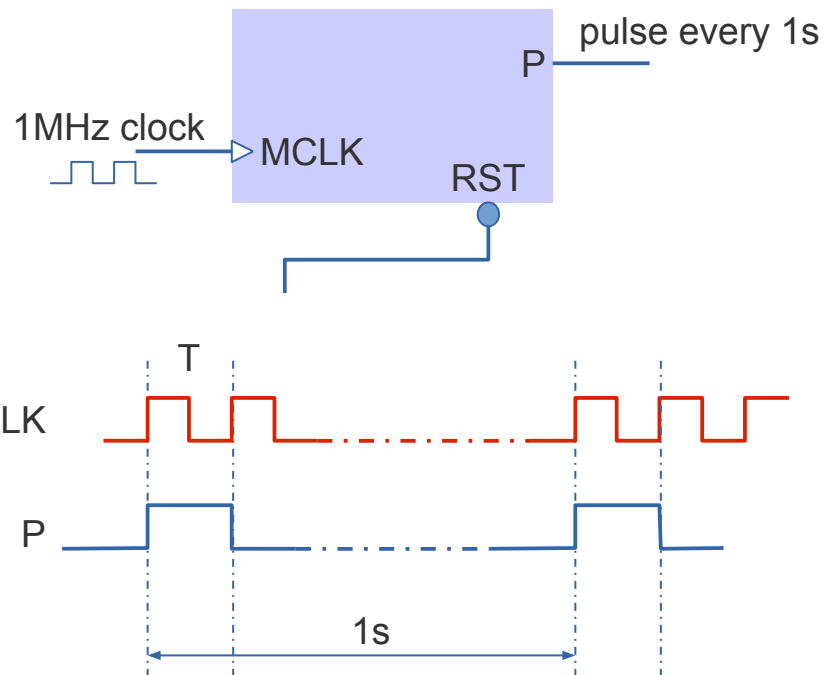

```
entity pulse_gen is
  port( RST,MCLK:in std_logic;
        P:out std_logic );
end pulse_gen;
```

Whenever a reset occurs (i.e. $RST = '0'$), system resets itself. Normal operation restarts when reset is no more active.

Retrieve and edit the following files:

- pulse_gen.vhd → entity + architecture of your component
- test_pulse_gen.vhd → test architecture.

Compilation:

```
ghdl -a --ieee=synopsys -fexplicit \
pulse_gen.vhd test_pulse_gen.vhd
```

Elaborate:

```
ghdl -e --ieee=synopsys -fexplicit test_pulse_gen
```

Run:

```
ghdl -r --ieee=synopsys -fexplicit test_pulse_gen \
--wave=test_pulse_gen.ghw
```

Visualisation:

```
gtkwave test_pulse_gen.ghw
```

Note: search for **ghdl makefile** to ease things a bit.

- *log2* function


Allows you to get the number of bits required to encode a value:

$\log_2(1)=0$
 $\log_2(2)=1$
 $\log_2(4)=2$
 $\log_2(8)=3$

```
function log2(V:natural) return natural is
begin
    .....
end log2;
```

VHDL basics

- D flip-flop

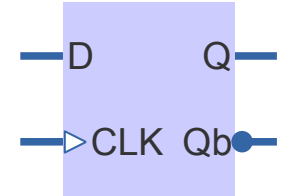

What's wrong here ??

```
entity basculeD is
port(
  D, CLK: in std_logic;
  Q: inout std_logic;
  Qb: out std_logic);
end basculeD;
architecture beh1 of basculeD is
begin
  process
  begin
    wait until clk'event and clk='1';
    Q <= d;
    Qb <= not Q;
  end process;
end beh1 ;
```

entity basculeD is

port(

D, CLK: in std_logic;

Q: inout std_logic;

really ??

Qb: out std_logic);

end basculeD;

architecture beh2 of basculeD is

Begin

```
Qb <= not Q; process001
```

```
process process002
```

```
begin
```

```
  wait until clk'event and clk='1';
```


```
  Q <= d;
```

```
end process;
```


end beh2 ;

VHDL basics

beh1 architecture

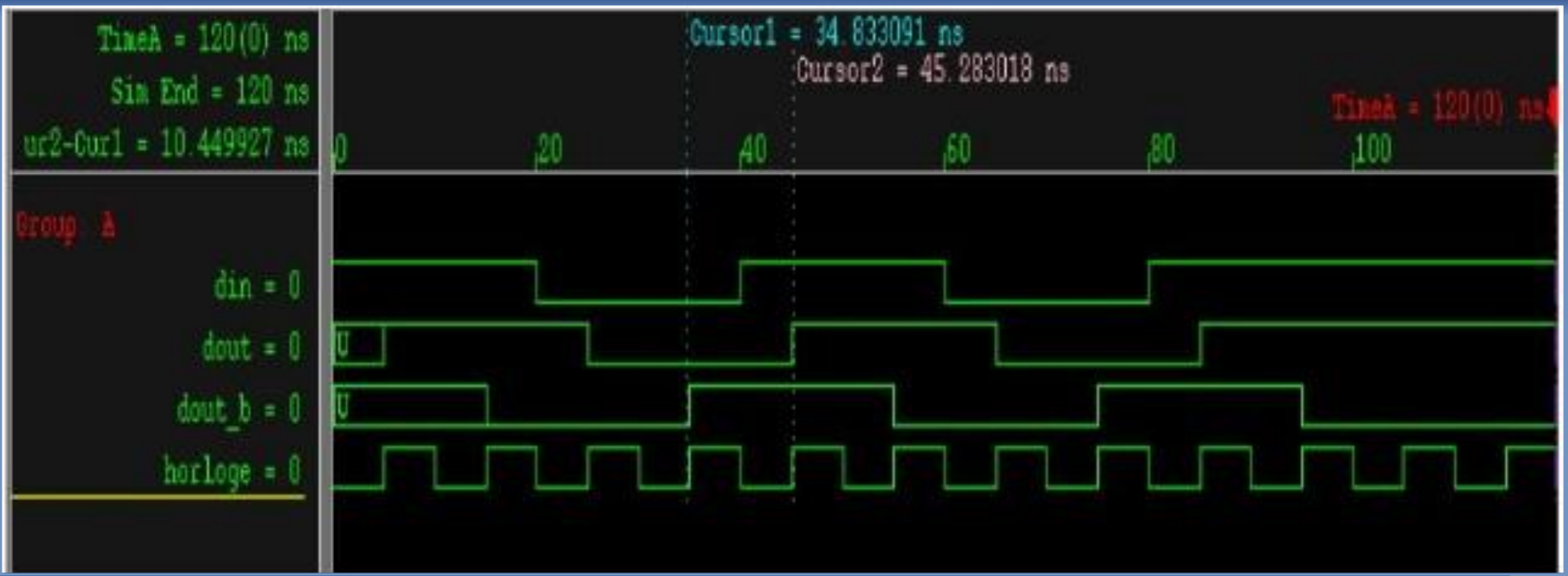

beh2 architecture

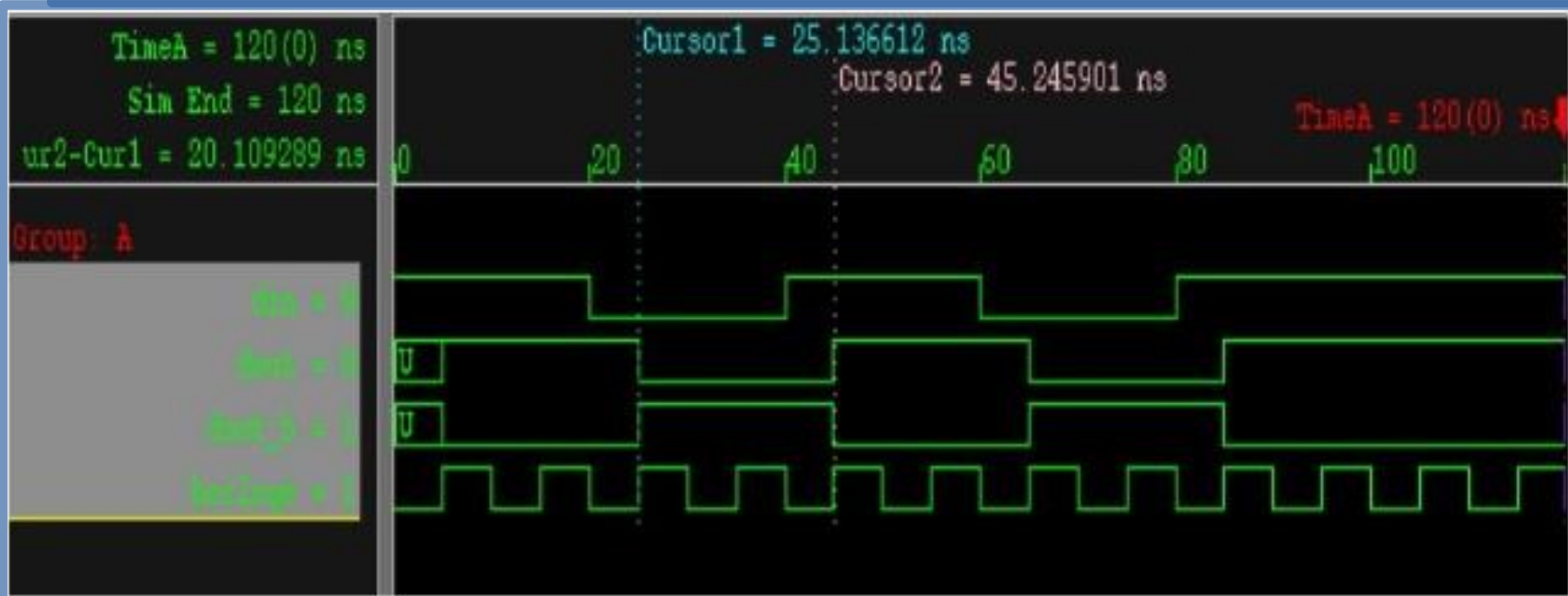

VHDL basics

- D flip-flop – Reset featured

asynchronous


```
entity basculeD is
  port(
    RST, D, CLK: in std_logic;
    Q: out std_logic;
    Qb: out std_logic );
end basculeD;
```

```
architecture beh3 of basculeD is
begin
  process( RST, CLK )
  begin
    if RST='0' then
      Q <= '0'; Qb <= '1';
    elsif rising_edge( CLK ) then
      Q <= d;
      Qb <= not D;
    end if;
  end process;
```

synchronous


```
entity basculeD is
  port(
    RST, D, CLK: in std_logic;
    Q: out std_logic;
    Qb: out std_logic );
end basculeD;
```
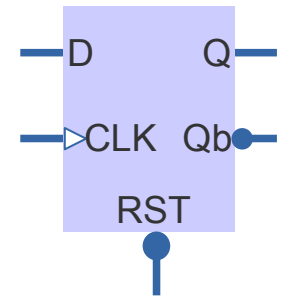
```
architecture beh3 of basculeD is
begin
  process( CLK )
  begin
    if rising_edge( CLK ) then
      if RST='0' then
        Q <= '0'; Qb <= '1';
      else
        Q <= d; Qb <= not D;
      end if;
    end if;
  end process;
```



Exercises

• 8 bits multiplexer

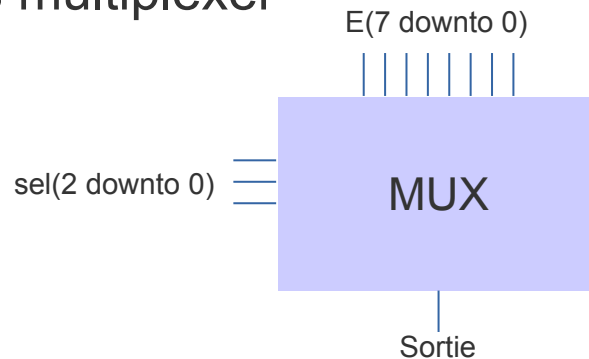


```
entity mux is
port (
    sel : in integer range 0 to 7 ;
    entree : in std_logic_vector(7 downto 0);
    Sortie : out std_logic);
end mux;
architecture beh of mux is
begin
    with sel select -- instruction de choix concurrente
        sortie <= entree(0) when 0,
                entree(1) when 1,
                entree(2) when 2,
                entree(3) when 3,
                entree(4) when 4,
                entree(5) when 5,
                entree(6) when 6,
                entree(7) when 7;
end beh;
```

Ré-écrivez ce multiplexeur en utilisant les affectations conditionnelles :

- dans le domaine combinatoire,
- puis dans un process.

Exercises

- 3 → 8 decoder

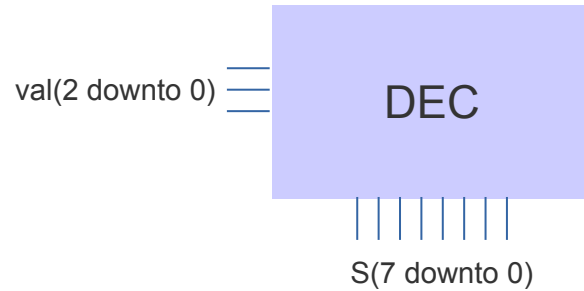

val	S0	S1	S2	S3	S4	S5	S6	S7
0	1							
1		1						
2			1					
3				1				
4					1			
5						1		
6							1	
7								1



Only one output activated for each input value ... **now it's up to you !**

VHDL basics

- Généricité

une entité est générique, jamais une architecture.

permet de définir une famille de composants par rapport à une caractéristique donnée.

valeur fixée lors de l'instance de l'entité

default value

```
entity mydecoder is
  generic ( size: natural:=4 );
  port ( S: out STD_LOGIC_VECTOR (size-1 downto 0);
        val: in STD_LOGIC_VECTOR( _____ downto 0) );
end myadder;
```

Instanciation du composant :

```
dec1 : entity work.mydecoder(behaviour)
  generic map (8)
  port map (val=> xxx, S=> yyy);
```

guess what to set here ??

- Généricité – instruction concurrente **generate**

Permet l'élaboration itérative ou conditionnelle de lignes de code

2 formes : conditionnelle et itérative

Forme conditionnelle

label : **if** condition_booléenne **generate**

 suite d'instructions concurrentes

end generate {label};

Forme itérative

label : **for** nom_du_paramètre_de_la_génération **in** intervalle discret **generate**

 suite d'instructions concurrentes

end generate {label};

VHDL basics

- Généricité

Exemple: registre à décalage **générique** (N)

entrées Data et Clock - std_logic;

sortie S est un std_logic_vector (N-1 downto 0)

architecture structurelle en utilisant un composant de type bascule D


entity reg_decalage **is**

GENERIC(N: natural :=8);

port (Data, clock : **in** std_logic;

S : **out** std_logic_vector(N-1 downto 0));

end reg_decalage;

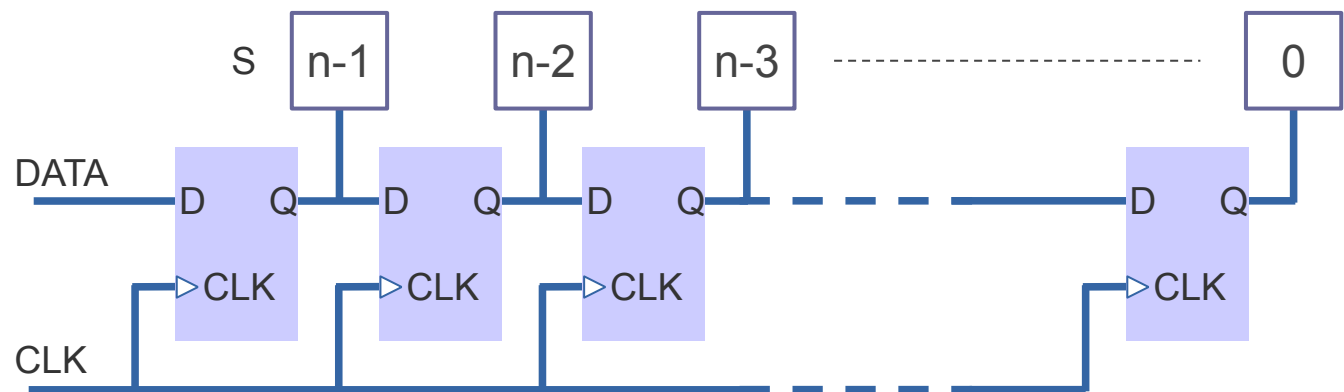



VHDL basics

- Généricité

```
library work;  
use work.basculeD.all;
```

```
ARCHITECTURE structurelle OF reg_decalage IS
```

```
    for all : basculeD use entity work.basculeD(beh3);
```

```
begin
```

```
    gauche : basculeD port map (data, clock, S(N-1), open);
```

```
    boucle : for i IN 1 to N-1 generate
```

```
        circ : basculeD PORT MAP (S(N-i), clock, S(N-i-1), open);
```

```
    END GENERATE boucle;
```

```
END structurelle ;
```

What's wrong here ??

VHDL basics

- Généricité

```
library work;  
use work.basculeD.all;
```

```
ARCHITECTURE structurelle OF reg_decalage IS
```

```
    signal aux : std_logic_vector (N-1 downto 0);
```

```
    for all : basculeD use entity work.basculeD(beh3);
```

```
begin
```

```
    gauche : basculeD port map (data, clock, aux(N-1), open);
```

```
    boucle : for i IN 1 to N-1 generate
```

```
        circ : basculeD PORT MAP (aux(N-i), clock, aux(N-i-1), open);
```

```
    END GENERATE boucle;
```

```
    S <= aux;
```

```
END structurelle ;
```

Now it's ok :)



VHDL basics

- Généricité

architecture comportementale

```
ARCHITECTURE beh OF reg_decalage IS
```

```
begin
```

```
  comport : process
```

```
  begin
```

```
    wait until clock'event and clock ='1';
```

```
    s(n-1) <= Data ;
```

```
    copie : For i IN n-1 to 1 LOOP
```

```
      s(n-i-1) <= s(n-i);
```

```
    end loop copie;
```

```
  end process comport ;
```

```
END beh;
```

What's wrong here ??



VHDL basics

- Généricité

ARCHITECTURE beh **OF** reg_decalage **IS**

signal aux : std_logic_vector (N-1 downto 0);

begin

s <= aux ;

comport : **process**

begin

wait until clock'event and clock ='1';

aux(n-1) <= Data ;

copie : **For** i **IN** n-1 **to** 1 **LOOP**

aux(n-i-1) <= aux(n-i);

end loop copie;

end process comport ;

end beh;

Now it's ok :)

- Compilation, élaboration, exécution, exploitation

Utilisation du VHDL :

- compilation et éditions de liens
 - aspects statiques de la description
- élaboration
 - aspects paramétrables de la description;
 - effectue l'instanciation de la description VHDL;
 - si la structure est hiérarchique il faut commencer par le plus haut niveau
- exécution
 - pour un simulateur $\Leftrightarrow$ simulation
 - pour un synthétiseur $\Leftrightarrow$ la synthèse
- exploitation des résultats plus spécifique de la simulation

VHDL basics

concurrent domain

sequential domain

```
Q <= value1 when condition else  
  value2;
```

affectations
conditionnelles

```
if condition then  
  Q <= value1;  
else  
  Q <= value2;  
end if;
```

boucles

```
for indice in intervalle generate  
  affectations concurrentes;  
end generate;
```

```
for indice in intervalle loop  
  instructions séquentielles;  
end loop;
```

```
while condition loop  
  Instructions séquentielles;  
end loop;
```


Part II - Synthesis for FPGA targets

- Introduction,
- VHDL logic synthesis,
- Xilinx Zynq,
- GoWin GW1NSR-4C (cortex M3+FPGA)



Introduction

- ICs wrapping nightmare in the 80's ...

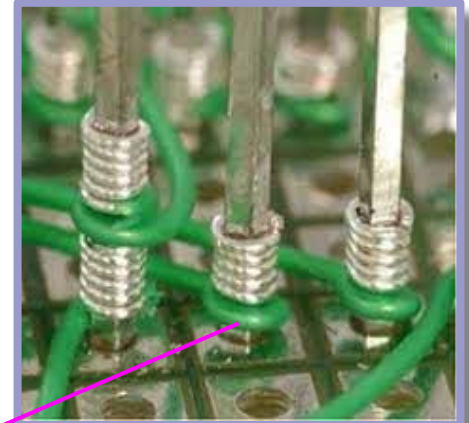

[PAL] Programmable Array Logic collapsed **numerous** combinatorial functions **into a single chip** :)

... then PALs evolved to [GALs]


While PALs were OTP*, GALs enabled reprogramming and added sequential logic (D flip-flop, ...)

By the end of the 80's, Xilinx invents FPGA !

Introduction

- starting in the 90's, **FPGA** & **CPLD** as synthesis targets :)

FPGA / CPLD

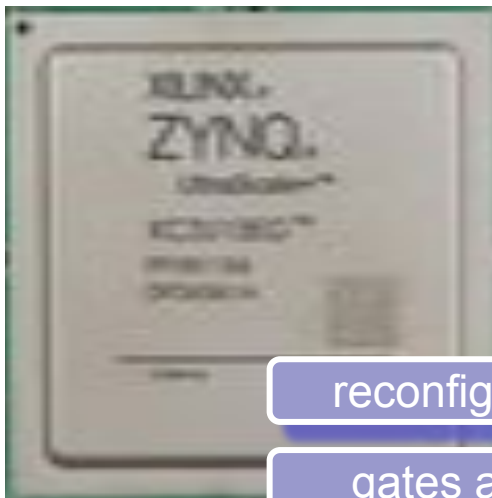


reconfigurable

gates arrays

€€, Moderate speed, convert to ASIC for high volumes, partially customisable, errors ⇒ just **reflash** :)

ASIC

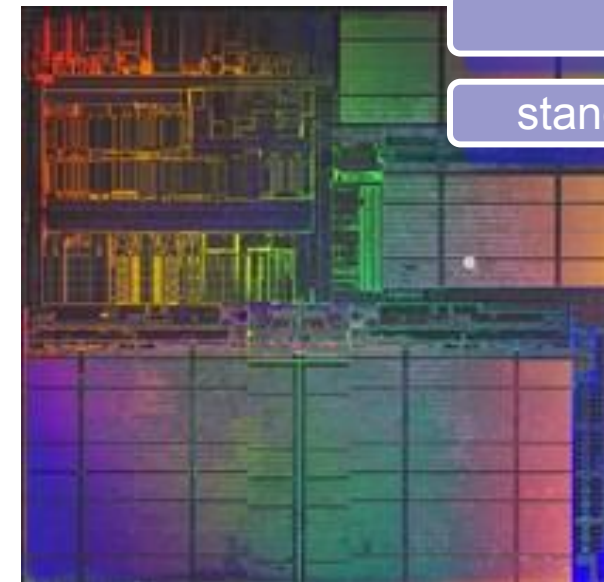

fixed


standard cells

(HP PA-RISC 8500 die)

€€€€, Highest speed, low-cost on (*high*) volumes, fully customisable ... but errors ⇒ you're dead!

Introduction


• Synthesis workflow

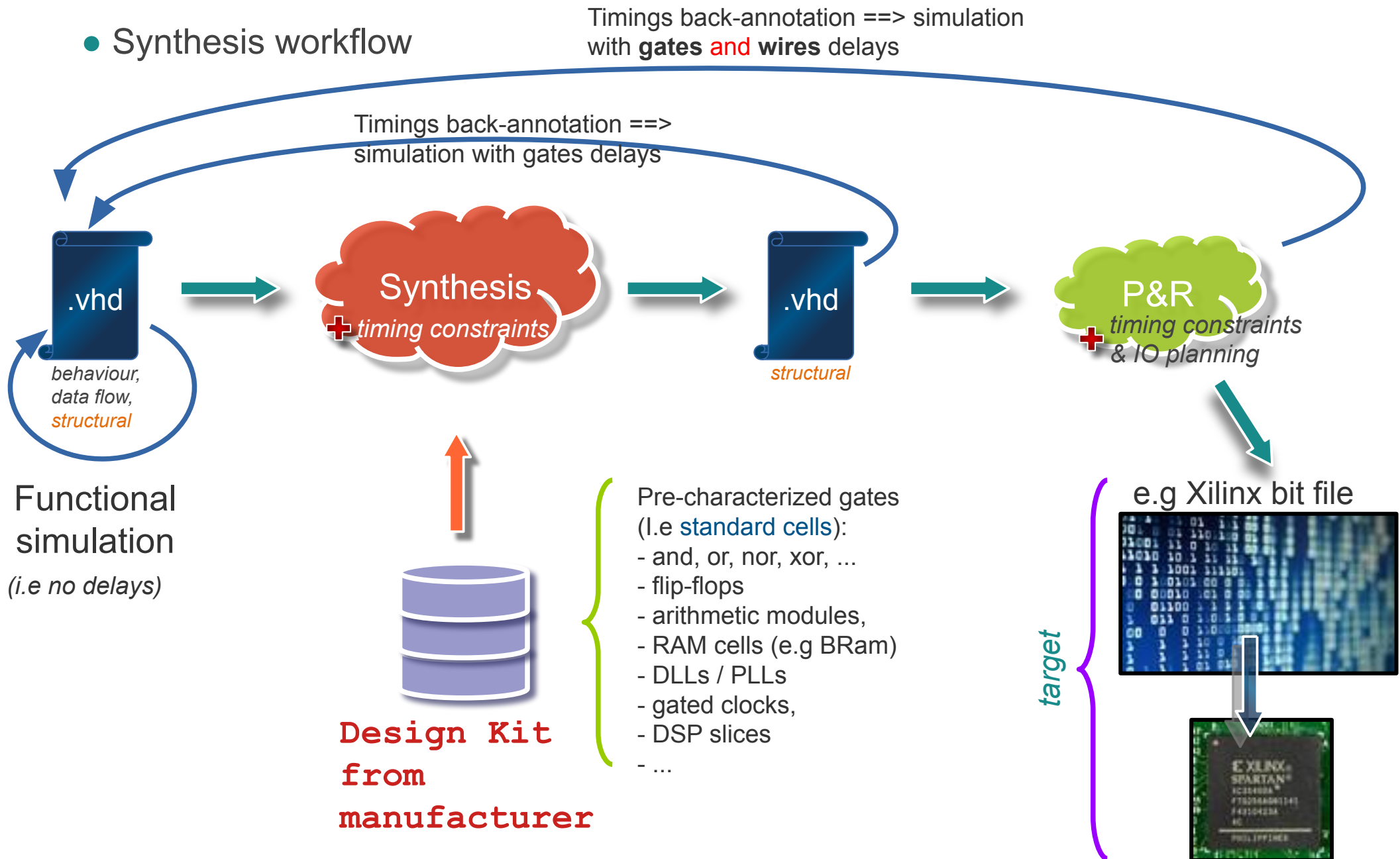

Introduction


- Synthesis to **reconfigurable hardware**

FPGA

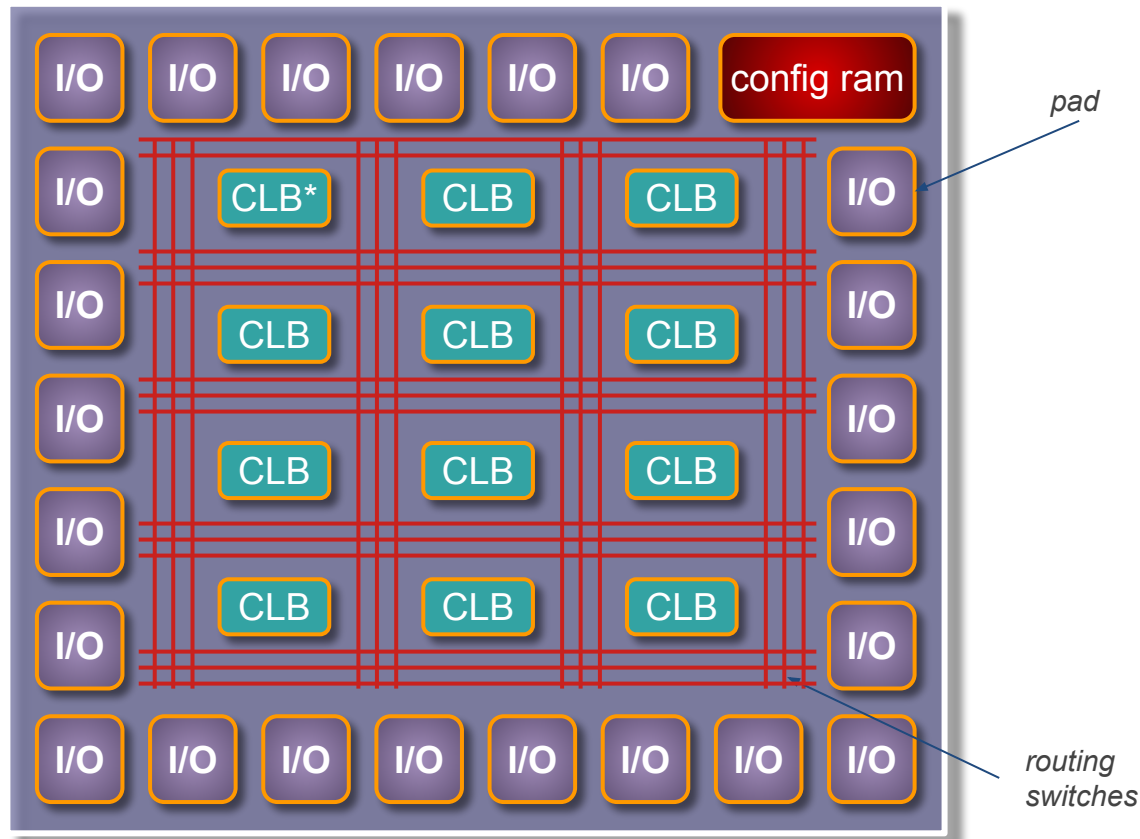

pad 2 pad delay depends on internal routing
⇒ **non deterministic !**

CPLD

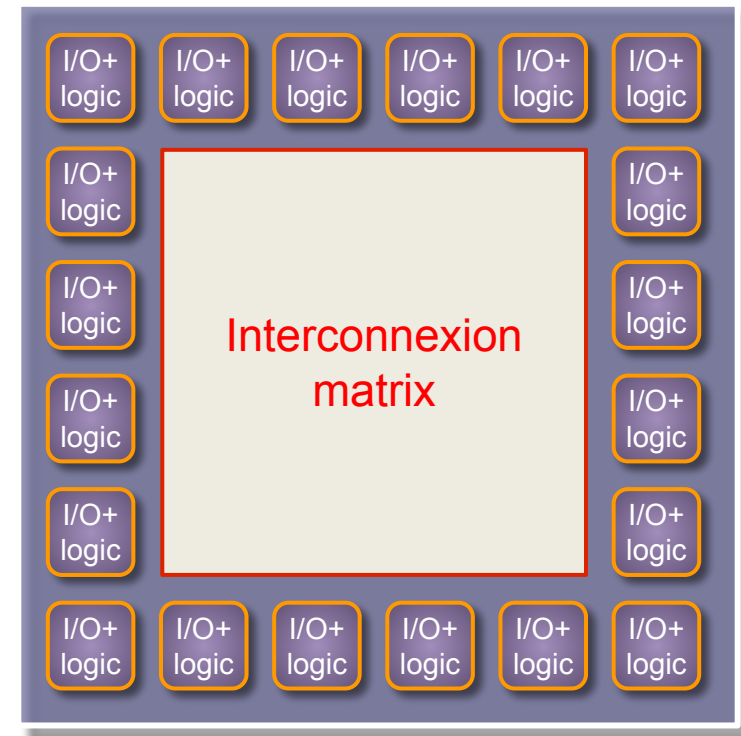

pad 2 pad propagation delay is **deterministic.**

* **C**onfigurable **L**ogic **B**loc features LUT(s) with registers.



Introduction


- Hardware (re)configurable targets
 - ✦ CPLD → huge crossbar with surrounding I/O pads
 - ✦ FPGA → CLBs spread over the entire chip with huge interconnexion matrix

High-End FPGA may contains either
Hard-IP processors (e.g dual ARM9 in Xilinx **Zynq**)
Softcore processor (e.g RISC-V, MicroBlaze or Leon)

CPLD features less logic blocks but it exhibits deterministic propagation delays.

Introduction

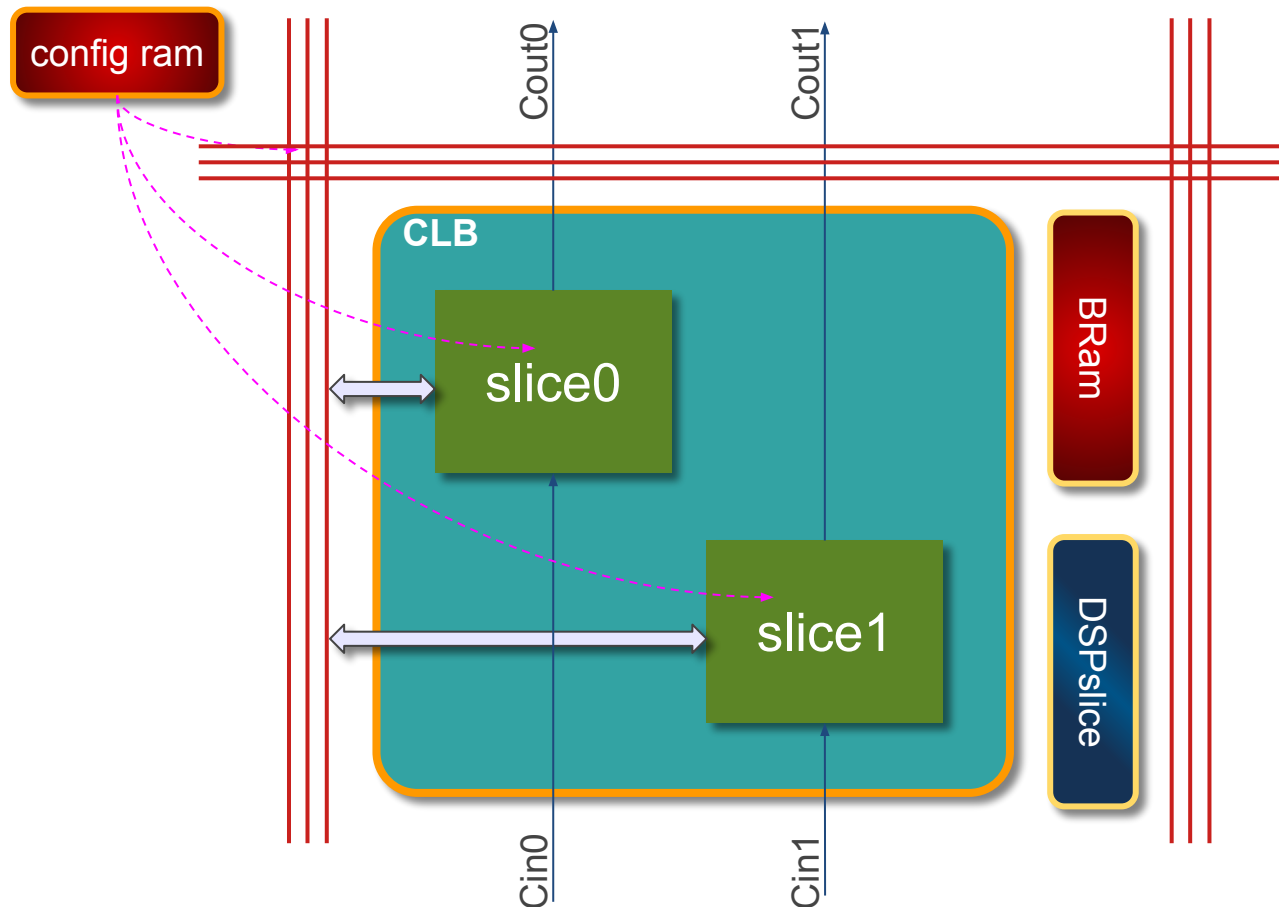- Anatomy of a CLB (Configurable Logic Block)




- **config ram** configure every piece of inner hardware. It holds content of the bitfile generated by synthesis tools.
- **sliceX** hold LUTs, registers, adders, ...
- **BlockRAMs** spread within routing matrix,
- **DSPslices** to build signal processing engines,
- Clock distribution management along with PLL and/or DLL (not shown), ...

Excerpt from SOC Zynq-7000 CLB architecture. Slices count may differ according to versions and manufacturers.

Introduction

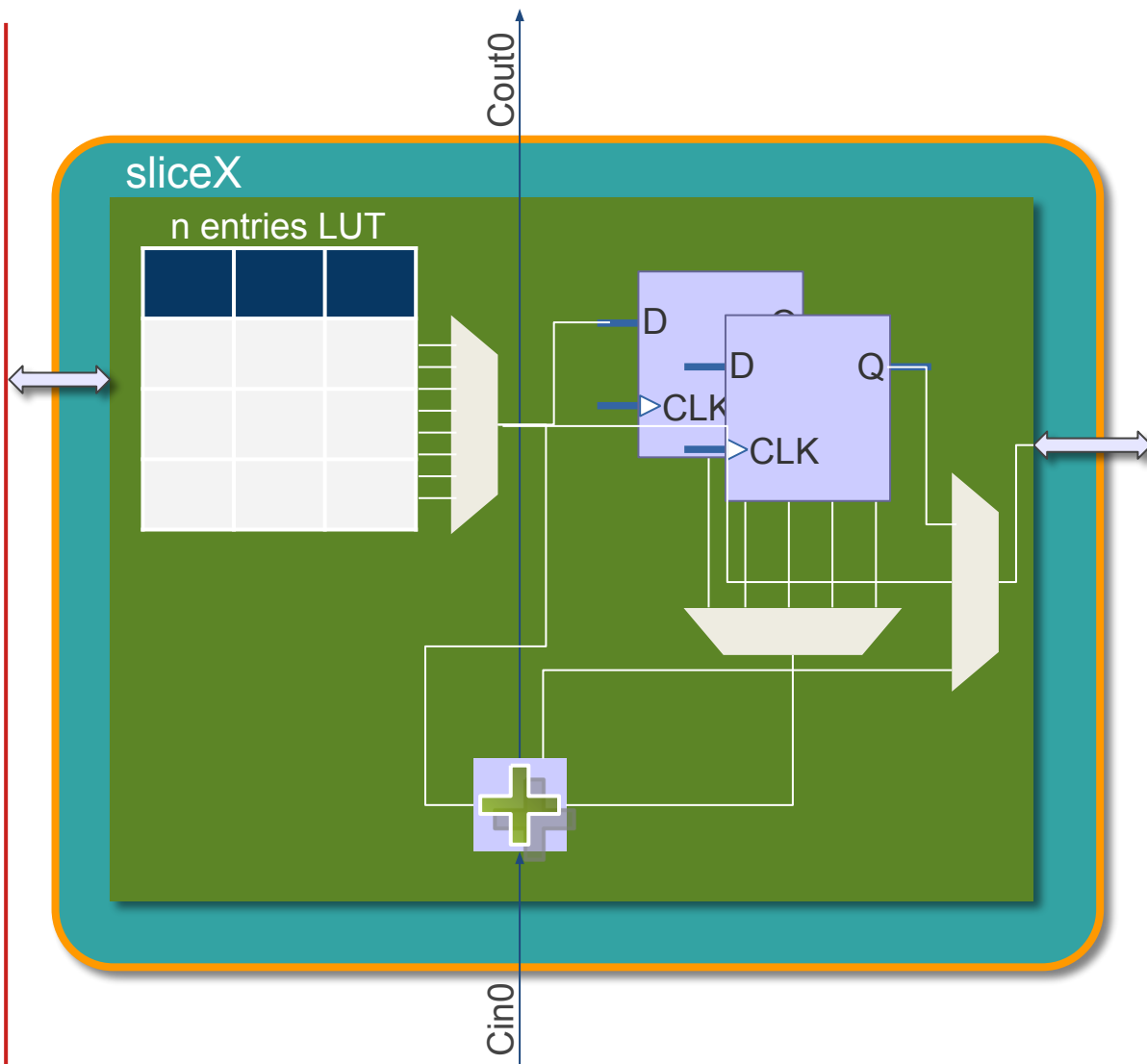- CLB (Configurable Logic Block) anatomy: slice inner view



- LUT stands for Look Up Table,
- a LUT features n inputs, 1 or 2 outputs
- a LUT is basically a table of truth: determine the output for any given input,
- LUT represents the combinatorial logic,
- D flip-flop enables sequential logic,
- all configurations from **config ram**

Plan

Part II - Synthesis for FPGA targets

- Introduction,
- VHDL logic synthesis,
- Xilinx Zynq,
- GoWin GW1NSR-4C (cortex M3+FPGA),





VHDL logic synthesis

- RTL level synthesis*

C'est un processus de traduction :

entrée : description comportementale ou de type flot de données

sortie : description **structurelle** à partir d'éléments de base prédéfinis -
standard cells

Respect de la fonctionnalité originale

Respect des contraintes en temps et en topologie

Représentation physique :

- ASIC
- FPGA

IEEE 1076.6-2004 defines a subset of VHDL for RTL synthesis

**High Level Synthesis on its side (e.g Vivado "HLS") enables architectures explorations as a custom partitioning between hardware and software. This way, you usually start from a C,C++ or SystemC application for example.*



VHDL logic synthesis

- Types pour la synthèse logique

énumérés

type BIT et opérations associées

types du package STD_LOGIC

entiers :

- la plage de variation détermine le nombre de bits nécessaires
- les bits ne sont pas individuellement accessibles

Types **non synthétisables**

- REAL, ACCES, FILE
- Types physiques: TIME ou définis par l'utilisateur



VHDL logic synthesis

- Remarques

usage des types énumérés fortement recommandé : on reste synthétique et on laisse à l'outil de synthèse le choix de la bonne stratégie de codage

il n'y a pas de consensus quant au codage des types énumérés

seuls les tableaux à une dimension sont synthétisables à cause de la difficulté du calcul d'adresse. Les agrégats sont mis à plat.

les types prédéfinis du package IEEE_1164 sont fortement recommandés



VHDL logic synthesis

- Objets et synthèse logique

- Constantes

Acceptées pour tous les types synthétisables. Leur déclaration ne produit aucun matériel. Leur usage produit du matériel dans les cas suivants :

- ❖ partie droite d'affectation de signal
 - ❖ dans une instruction **if** ou **case**
 - ❖ dans une instruction concurrente conditionnelle

- Signaux

assimilables à des fils ou bus

- Variables (affectation de variable)

pas de règle générale pour déduire le matériel produit
c'est le contexte d'utilisation qui est déterminant



VHDL logic synthesis

- Initial values

En VHDL 3 types:

- ❖ Valeurs par défaut héritée de la définition du type ou du sous-type
- ❖ Initialisation explicite à la déclaration de l'objet
- ❖ Valeur affectée par instruction au début d'un *process*

Synthèse - les 2 premiers cas sont ignorés par les outils de synthèse

- Generic parameters

Permet de définir une famille de composants par rapport à une caractéristique donnée

Valeur est fixé lors de l'instanciation de l'entité

Synthèse :

Le type de paramètres génériques synthétisable est restreint en fonction de l'outil

Pour SYNOPSIS : seulement les paramètres génériques de type **INTEGER** ou **énumérés** sont synthétisable



VHDL logic synthesis

- Sequential instructions and logic synthesis

- Instruction de synchronisation :

- sur signal de la liste de sensibilité (process (A,B,C) ou wait A,B,C)

- ⇒ matériel combinatoire

- sur signal d'horloge (clk'event and clk='1') ou (clk'event and clk='0')

- ⇒ D flip-flop (FF)

- sur niveau de signal (en='1' ou en='0')

- ⇒ Latch

- Instructions d'itération

- for : synthétisable dans la mesure où les bornes de variation de l'index sont statiques.

- while : non-synthétisable au niveau RTL

- Appel de sous-programmes

- certaines fonctions sont connues de la synthèse - pas de matériel additionnel

- fonctions passage de paramètres par valeurs - combinatoire

- fonctions passage de paramètres par référence - pas du domaine de la synthèse logique



VHDL logic synthesis

- **Processes** and logic synthesis

Problème principal : combinatoire ou séquentiel ?

Processus combinatoire si :

- ❖ liste de sensibilité ou un seul point de synchronisation (wait)
- ❖ pas de déclaration de variable ou bien variables locales systématiquement affectées avant d'être lues
- ❖ les signaux lus se trouvent tous dans la liste de sensibilité
- ❖ Les signaux écrits sont tous affectés quelques soient les branchements parcourus

Si création de mémoire - processus séquentiel

- ❖ style synchrone - bascule D



VHDL logic synthesis

- Concurrent instructions and logic synthesis

Affectation de signal simple - matériel combinatoire

Affectation conditionnelle ou sélectionnée

`S <= A when X=' 1 ' else B when Y=' 1 ' else C` - combinatoire

`S <= A when X=' 1 ' else B when Y=' 1 ' else S` - séquentiel

Instanciation (de composants, generate)

Les notions d'entité et de composant permettent de hiérarchiser la description d'un système

Configuration - ne sont pas supportées

Durant le processus de synthèse, différentes interprétations possibles:

- ❖ flattened instances
- ❖ composant synthétisé une fois. Seule la frontière est re-synthétisée pour chaque instance
- ❖ composant synthétisé une fois et dupliqué pour chaque instance



VHDL logic synthesis

- Performances

Timing

- Estimation des retards induits par les éléments combinatoires, en particuliers détection des "chemins critiques"
- Estimation des retards induits par les éléments des mémoire
- Estimation du temps de cycle de l'horloge

Surface

- Estimation en fonction des composants utilisées:
 - ❖ Standard cells (ASIC)
 - ❖ LUT, FF, DSPslices, BRam ... (FPGA)

Consommation

Testabilité, fiabilité, "manufacturabilité"



VHDL logic synthesis

- Timing constraints

4 catégories de contraintes temporelles peuvent être introduites pour optimiser un circuit avec temps minimums ou maximums entre différents points du circuit:

- ❖ Entrées - registres
- ❖ Registres - sorties
- ❖ Entrées - sorties
- ❖ Registres - registres

Définition de la période de l'horloge globale $T_{\text{période}}$ + le temps additionnel sur les entrées T_{in} et le temps additionnel sur les sorties T_{out}

- ❖ T_{out} - information sur la charge équivalente sur chaque sortie $\Rightarrow$ *fan-out*
- ❖ T_{in} - information sur la puissance de sortie du composant connecté en entrée
- ❖ $T_{\text{période}}$:
 - information de "skew" = déphasage maximal entre les arrivées de l'horloge sur les bascules
 - information sur la latence = temps maximal entre la commutation de l'horloge et la dernière bascule recevant l'horloge.



VHDL logic synthesis

- Timing optimisations

- Permet d'améliorer les caractéristiques de temps de traversée et de fréquence d'horloge
- Les outils de CAO ne modifient pas le nombre de bascules du circuits lors de l'optimisation
- Les outils CAO optimisent la logique combinatoire interne
- Il faut isoler le chemin le plus long de traversée de la logique combinatoire, c'est le **chemin critique** ⇒ **OPTIMISATION DU CHEMIN CRITIQUE**
 - ❖ Toute logique combinatoire partagée entre le chemin critique et d'autres chemins de logique est dupliquée pour permettre une optimisation poussée sur le chemin critique,
 - ❖ Augmentation de la taille des circuits après une optimisation temporelle.

- additional resources

ENSSAT Lannion | VHDL logic synthesis

http://people.rennes.inria.fr/Olivier.Sentieys/teach/VHDL_Logic_Synthesis_2019.pdf

Open source synthesis tools (verilog)

<https://github.com/YosysHQ/yosys>


Open FPGA loader (programmer)

<https://github.com/trabucayre/openFPGALoader>

Plan

Part II - Synthesis for FPGA targets

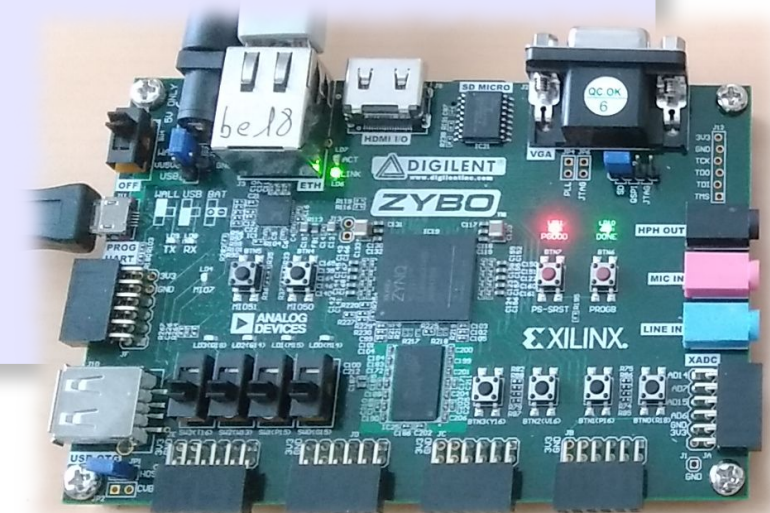- Introduction,
- VHDL logic synthesis,
- Xilinx Zynq,
- GoWin GW1NSR-4C (cortex M3+FPGA),



Digilent Zybo, Xilinx Zynq 7010

Xilinx Zynq (Zybo-Z7)

- Digilent Zybo Z7-20 (Xilinx Zynq 7020)

μSDcard (down side)

MIPI CSI-2 piCamera support :)

HDMI-in

+5VDC
2.5a

Gigabit

HDMI-out

PS_CLK
33.3333MHz osc

Zynq 7020 -1CLG400

1GB DDR3
512M top +
512M bottom

USB + μ USB (down side)

Boot modes


- QSPI flash
- JTAG
- SDcard

**128Mbit
QSPI flash**
(down side)

PMODs

Xilinx Zynq (Zybo)

- Digilent Zybo (Xilinx Zynq 7010)

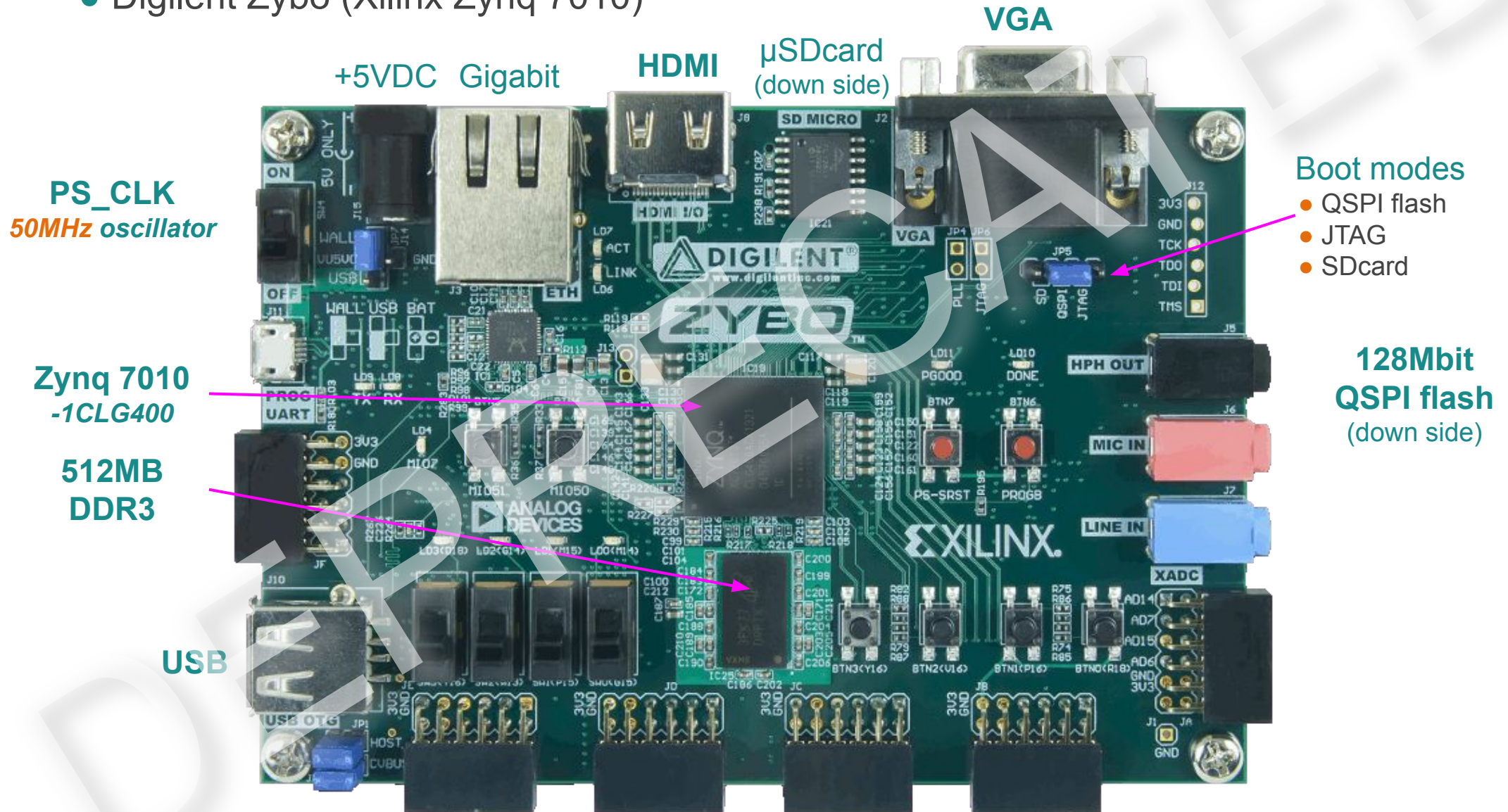



Xilinx Zynq*

* part of series-7 architecture (Artix-7, Virtex7, Spartan7 ...)

- SOC that combines CPU + FPGA

- ❖ For decades, FPGAs get connected through external buses to a main CPU
PCI, PCI express, SPI ...

- ❖ ... then Xilinx invents the Zynq SOC: CPU combined with a FPGA

- ❖ Using **FSBL** and **Uboot** ⇒ Linux booting :)

- ❖ dynamic reconfiguration of the FPGA while Linux is running !

cat bit_file > /dev/xdevcfg

- ❖ 2015, Intel acquired FPGA company Altera ⇒ Xeon D started to feature FPGA to overcome the crowded CPU instructions extensions !

SSE2, SSE3, SSE4 ... SSExx ! instead of fixed extended instructions that won't ever match all specific apps, FPGA enables tailored instructions to perfectly fit your needs !

Xilinx Zynq

- Zynq architecture overview

PS area

hard IP dual ARM9 with numerous IO controllers.

AHB

Amba High-performance Bus

PL area


The FPGA part that gets connected through AXI bus to the PS area.

APB

Amba Peripheral Bus

AXI

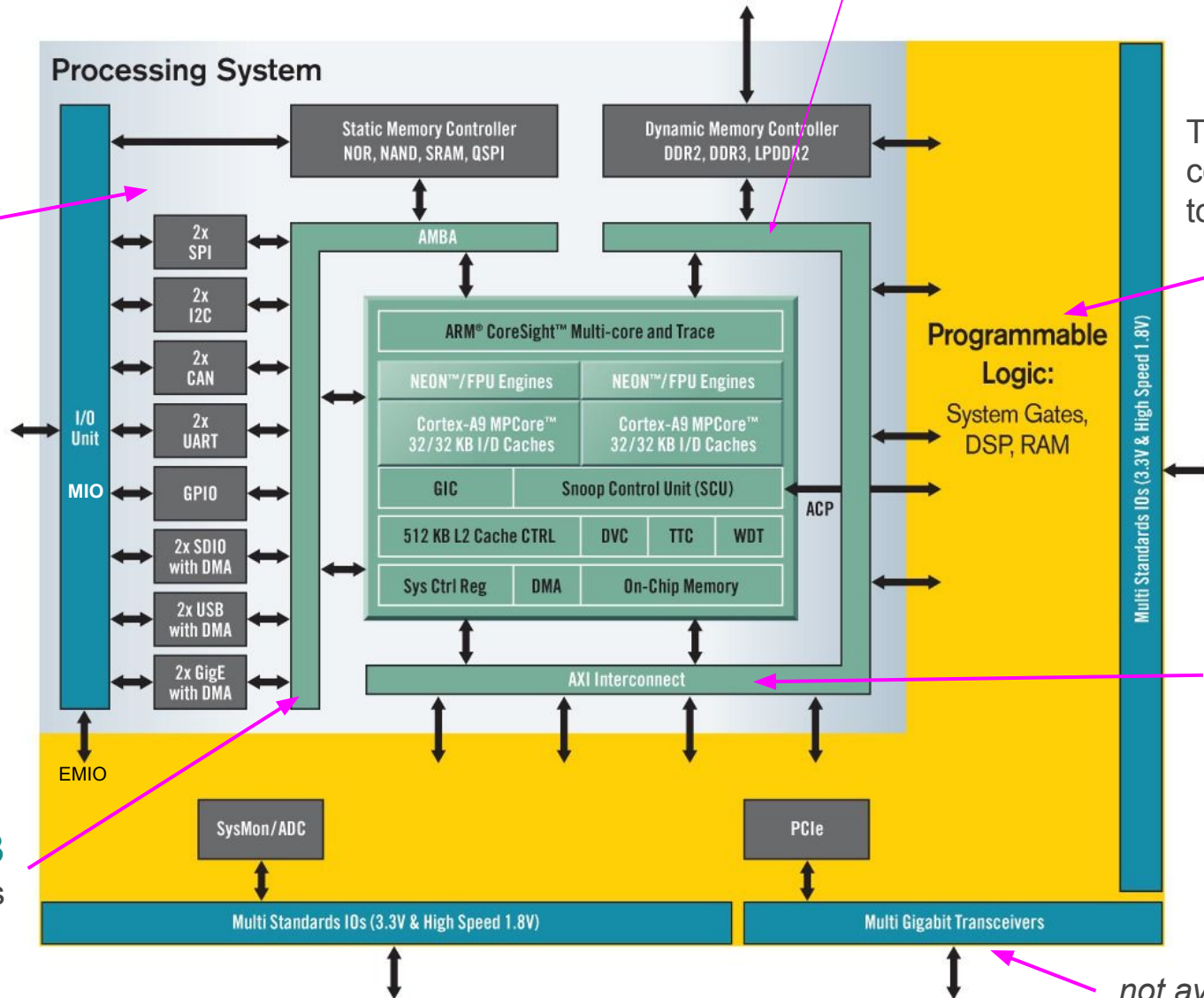
interconnect through
● AHB bridge
● APB bridge



not available on all releases!


Xilinx Zynq

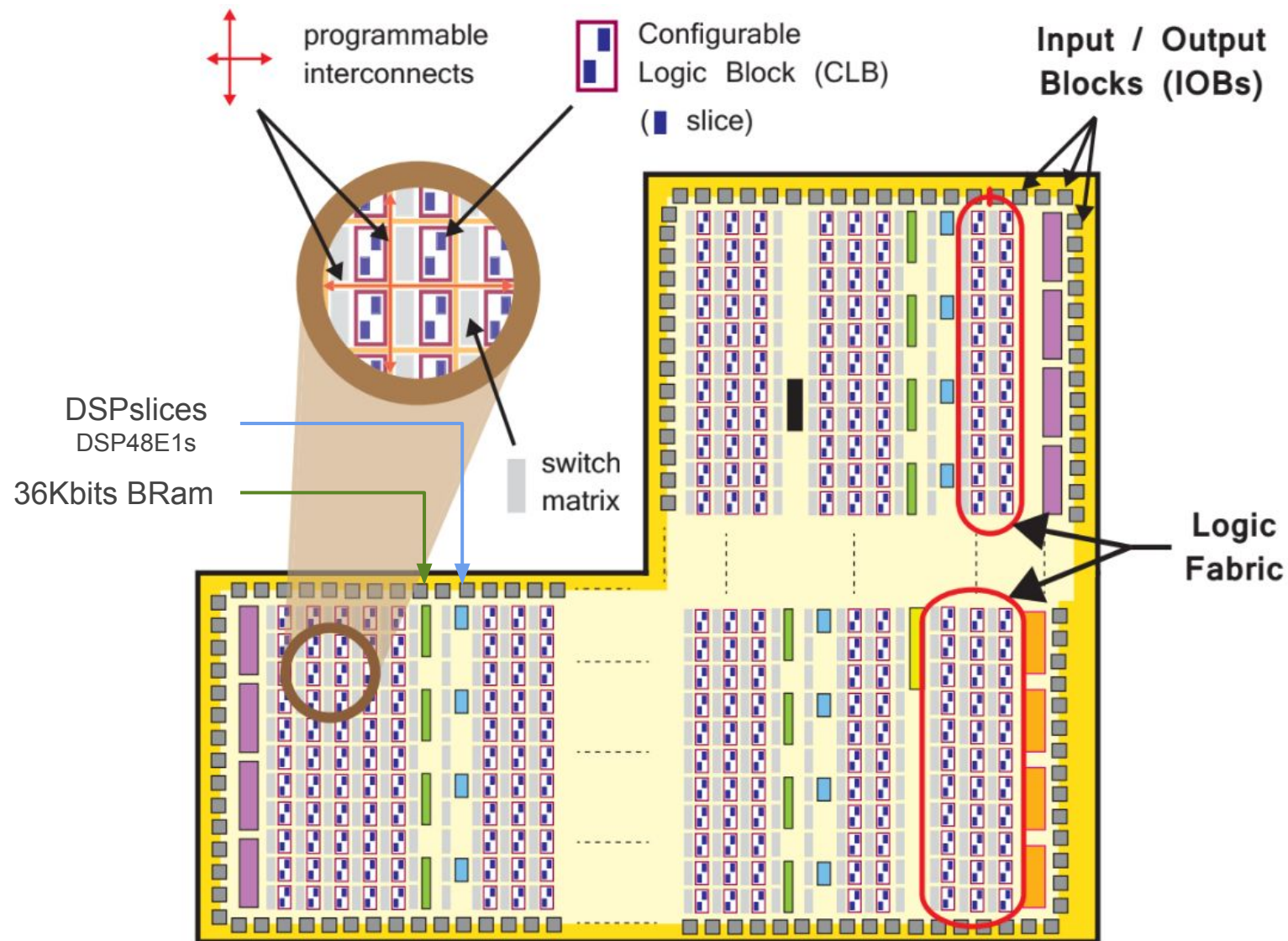- Zynq architecture overview - **PL area**




Xilinx Zynq

- Zynq architecture - **CLBs**

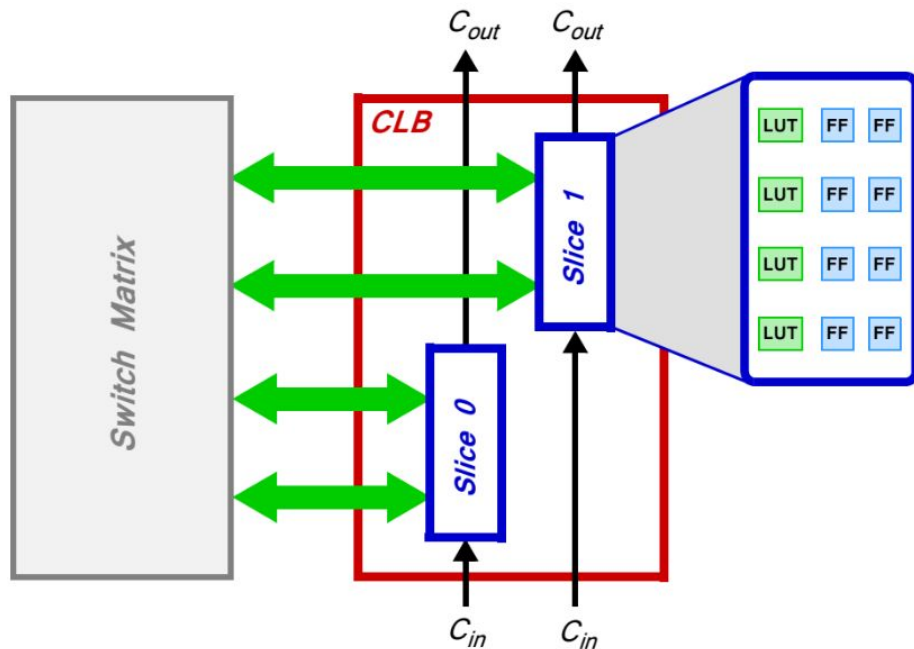

- Zynq architecture - **DSPslices**

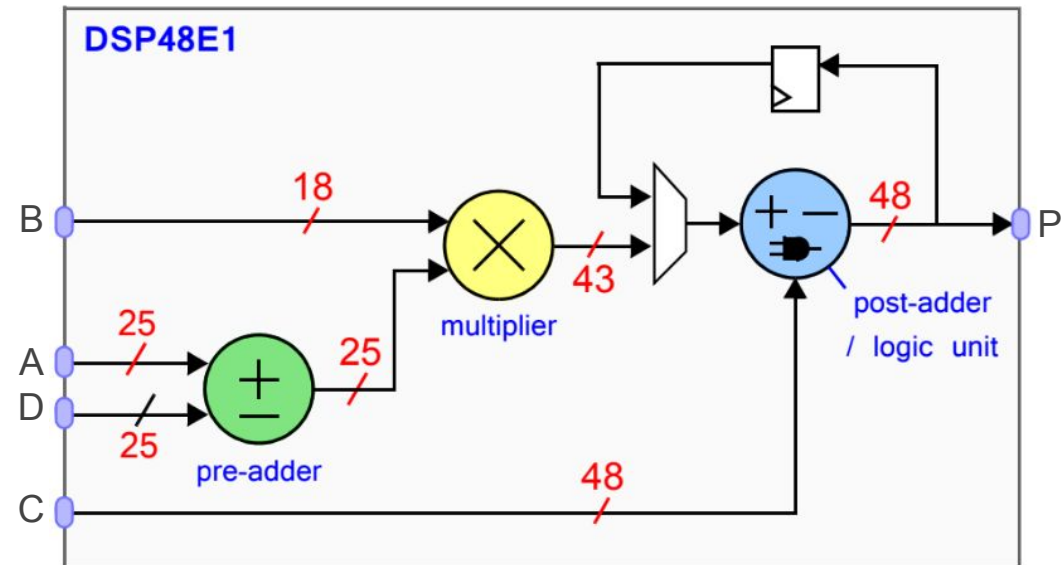
The **MAC** function: **M**ultiply **A**nd **aC**cumulate
 $P = (A+D)*B$ or $P = P' + C$



Xilinx Zynq

- Zynq architecture - **Block RAM (BRAM)**

- ❖ 36K**bits** configurable as single/dual banks (i.e 36 Kb or 2 x 18 Kb)
- ❖ may get configured with **single** or **dual** read/write ports
- ❖ independent **synchronous read** and write accesses
- ❖ integrated **bypass** policy
its named WRITE_FIRST
- ❖ may get used as **FIFOs**
embeds all necessary logic to achieve this.
- ❖ **NO NEED FOR AN EXPLICIT inference !**
side example of RAMB36 that can get automagically inferred.

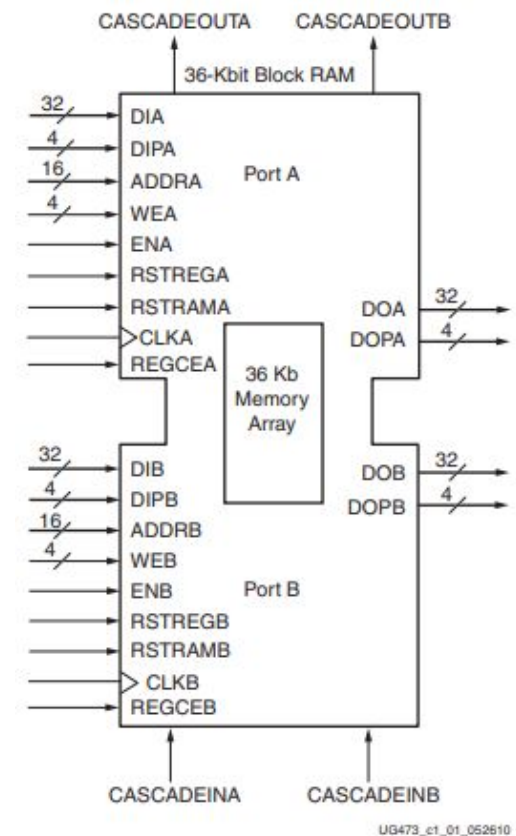

ug473 Memory Resources user guide

ug901 synthesis guide refers as **distributed RAM** vs **Block RAM** inferences.

→ Distributed RAM consumes LUTs, is a bit faster than dedicated Block RAM but only usable for small amount of RAM

Zynq-7000 SoC Family

Zynq®-7000 SoC Family

		Cost-Optimized Devices						Mid-Range Devices			
Device Name		Z-7007S	Z-7012S	Z-7014S	Z-7010	Z-7015	Z-7020	Z-7030	Z-7035	Z-7045	Z-7100
Part Number		XC7Z007S	XC7Z012S	XC7Z014S	XC7Z010	XC7Z015	XC7Z020	XC7Z030	XC7Z035	XC7Z045	XC7Z100
Processing System (PS)	Processor Core	Single-Core ARM® Cortex™-A9 MPCore™ Up to 766MHz			Dual-Core ARM Cortex-A9 MPCore Up to 866MHz			Dual-Core ARM Cortex-A9 MPCore Up to 1GHz ⁽¹⁾			
	Processor Extensions	NEON™ SIMD Engine and Single/Double Precision Floating Point Unit per processor									
	L1 Cache	32KB Instruction, 32KB Data per processor									
	L2 Cache	512KB									
	On-Chip Memory	256KB									
	External Memory Support ⁽²⁾	DDR3, DDR3L, DDR2, LPDDR2									
	External Static Memory Support ⁽²⁾	2x Quad-SPI, NAND, NOR									
	DMA Channels	8 (4 dedicated to PL)									
	Peripherals	2x UART, 2x CAN 2.0B, 2x I2C, 2x SPI, 4x 32b GPIO									
	Peripherals w/ built-in DMA ⁽²⁾	2x USB 2.0 (OTG), 2x Tri-mode Gigabit Ethernet, 2x SD/SDIO									
Security ⁽³⁾		RSA Authentication of First Stage Boot Loader, AES and SHA 256b Decryption and Authentication for Secure Boot									
Processing System to Programmable Logic Interface Ports (Primary Interfaces & Interrupts Only)		2x AXI 32b Master, 2x AXI 32b Slave 4x AXI 64b/32b Memory AXI 64b ACP 16 Interrupts									
Programmable Logic (PL)	7 Series PL Equivalent	Artix®-7	Artix-7	Artix-7	Artix-7	Artix-7	Artix-7	Kintex®-7	Kintex-7	Kintex-7	Kintex-7
	Logic Cells	23K	55K	65K	28K	74K	85K	125K	275K	350K	444K
	Look-Up Tables (LUTs)	14,400	34,400	40,600	17,600	46,200	53,200	78,600	171,900	218,600	277,400
	Flip-Flops	28,800	68,800	81,200	35,200	92,400	106,400	157,200	343,800	437,200	554,800
	Total Block RAM	1.8Mb	2.5Mb	3.8Mb	2.1Mb	3.3Mb	4.9Mb	9.3Mb	17.6Mb	19.2Mb	26.5Mb
	(# 36Kb Blocks)	(50)	(72)	(107)	(60)	(95)	(140)	(265)	(500)	(545)	(755)
	DSP Slices	66	120	170	80	160	220	400	900	900	2,020
	PCI Express®	—	Gen2 x4	—	—	Gen2 x4	—	Gen2 x4	Gen2 x8	Gen2 x8	Gen2 x8
	Analog Mixed Signal (AMS) / XADC ⁽²⁾	2x 12 bit, MSPS ADCs with up to 17 Differential Inputs									
	Security ⁽³⁾	AES & SHA 256b Decryption & Authentication for Secure Programmable Logic Config									
Speed Grades	Commercial	-1			-1			-1			-1
	Extended	-2			-2,-3			-2,-3			-2
	Industrial	-1, -2			-1, -2, -1L			-1, -2, -2L			-1, -2, -2L



Links

- additional resources

The Zynq book

<http://www.zynqbook.com/>

Zynq Tutorials Handbook

<http://www.zynqbook.com/download-tuts.html>

Digilent Zybo reference manual

https://www.xilinx.com/content/dam/xilinx/support/documentation/university/XUP%20Boards/XUPZYBO/documentation/ZYBO_RM_B_V6.pdf

<https://m2siame.univ-tlse3.fr/teaching/francois/UE-VHDL/ZYBO-Z7-reference-manual-B.pdf>

ug901: Xilinx synthesis guide

https://www.xilinx.com/content/dam/xilinx/support/documentation/sw_manuals/xilinx2021_2/ug901-vivado-synthesis.pdf

Understanding the Xilinx Zynq **F**irst **S**tage **B**oot **L**oader (FSBL)

<https://www.xilinx.com/video/soc/understanding-the-zynq-fsbl.html>

*(very first step, then **U-boot** as second step on way to booting Linux for example :D)*


IUT Nantes / GEii / Eric Peronnin Youtube channel

<https://www.youtube.com/c/EricPeronnin/videos>

Découverte de Vivado part2 <https://www.youtube.com/watch?v=djMAXkvw7UI>


Part II - Synthesis for FPGA targets

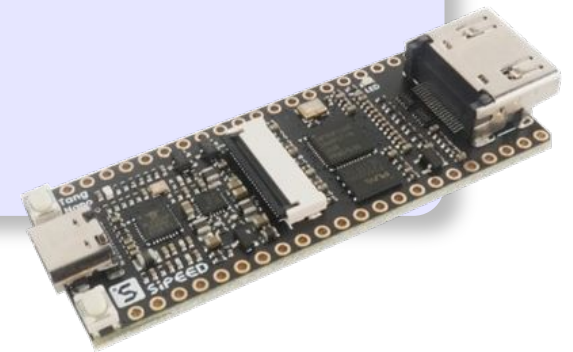- Introduction,
- VHDL logic synthesis,
- Xilinx Zynq,
- GoWin GW1NSR-4C (cortex M3+FPGA),



Sipeed Tang Nano 4K, GoWin GW1NSR-LV4C

GoWIN MiniStar dev. kit

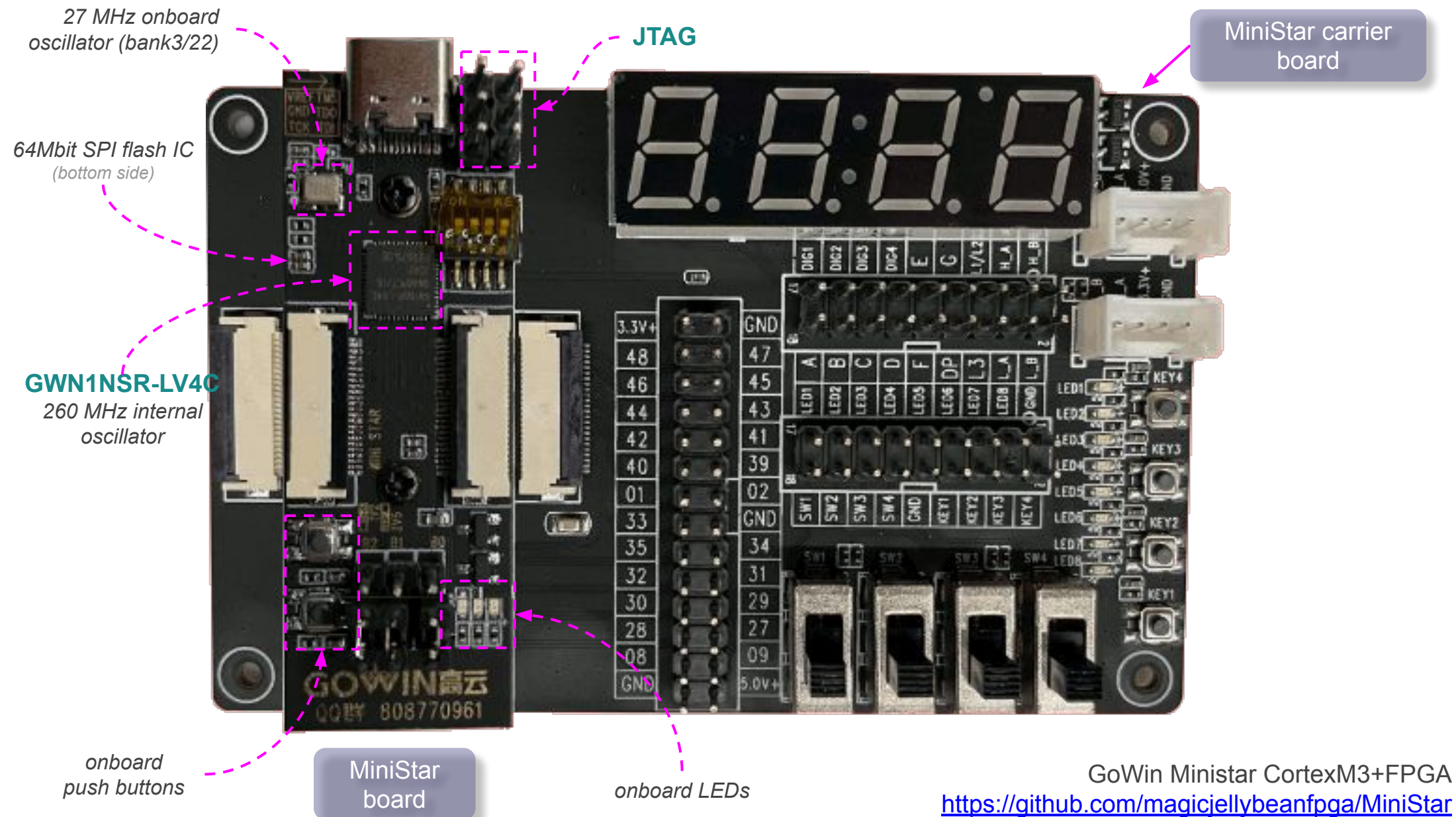

Sipeed Tang Nano 4K



Learn more at
<https://tangnano.sipeed.com>

TANG NANO 4K


PINOUT

- Power
- GND
- Control
- Physical Pin
- Bank Pin
- MSPI Mode Pin
- Debug Pin
- Camera Pin
- HDMI Pin
- User Key Pin
- Flash pin
- PLL Input Pin
- Clock Pin
- BANK0, $V_{IO}=3.3V$
- BANK1, $V_{IO}=3.3V$
- BANK2, $V_{IO}=2.5V$
- BANK3, $V_{IO}=1.8V$

GWN1NSR-LV4C

HDMI


CSI cam support :D

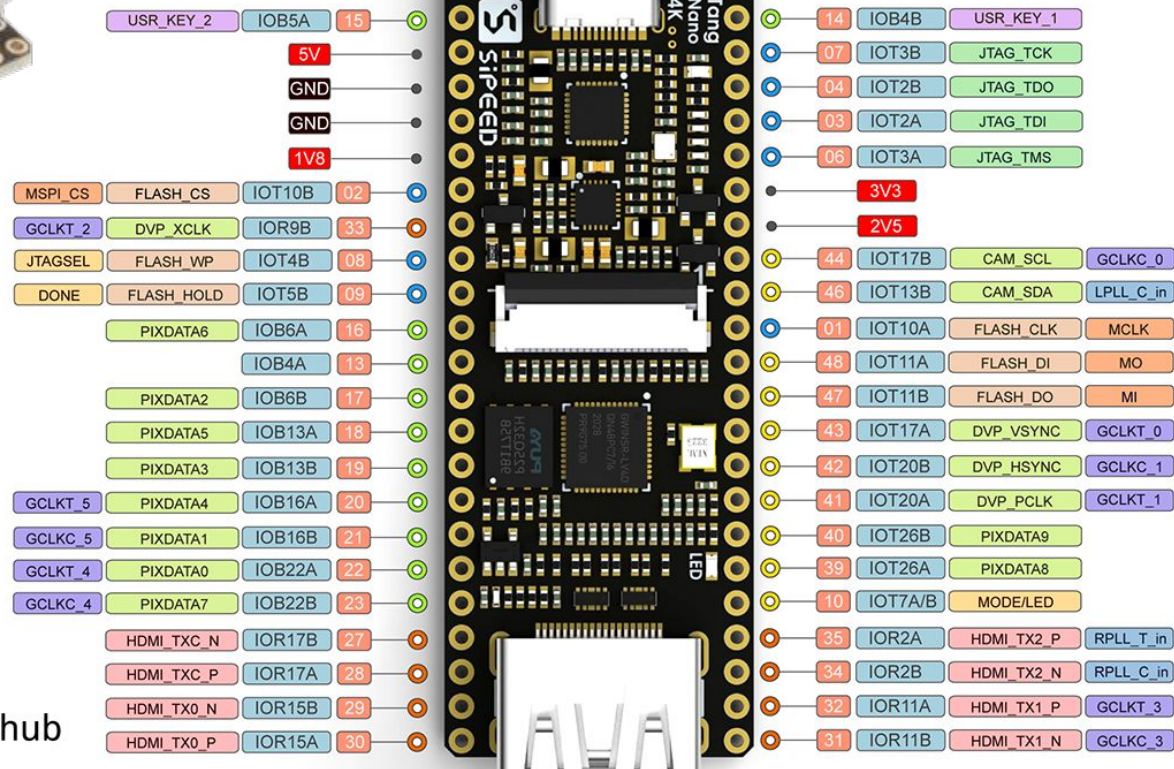


GoWin GW1NSR-4C

- entry-level SOC that combines ARM CortexM3 + FPGA
- ❖ Please note this is a **preliminary course support** about this device,
- ❖ You can use our GoWIN floating license server, even from home :)
secil.univ-tlse3.fr:10559
- ❖ [2023] new RISC-V hard IP @ FPGA → GW5AST (AE350_SOC),
- ❖ [2025] new 'gowin_gmd' linux toolchain to build Cortex M3 embedded apps


GoWIN FPGA IDE

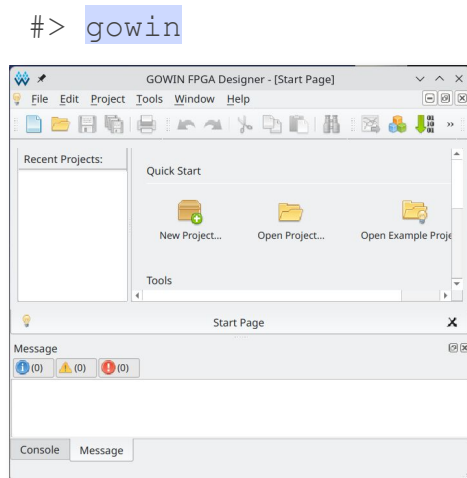

GoWIN Uploader

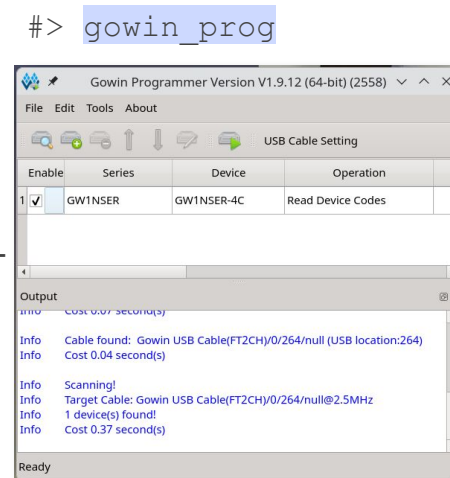

GoWIN MCU IDE

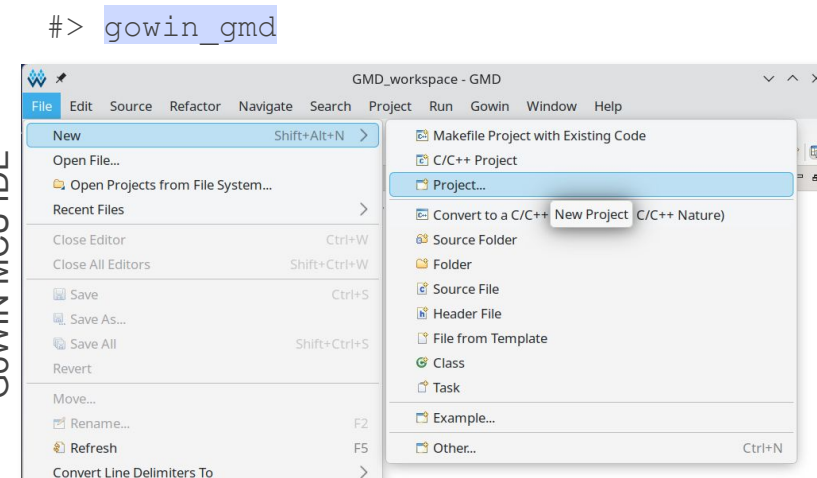

Note: 'openFPGALoader' as an alternative

GoWin GW1NSR-xC

Device	GW1NSR-2	GW1NSR-2C	GW1NSR-4	GW1NSR-4C
LUT4	1,728	1,728	4,608	4,608
Flip-Flop (FF)	1,296	1,296	3,456	3,456
Block SRAM BSRAM (bits)	72K	72K	180K	180K
BSRAM quantity BSRAM	4	4	10	10
18 x 18 Multiplier			16	16
User Flash (bits)	1M	1M	256K	256K
PSRAM (bits)	32M	32M	64M	64M
HyperRAM(bits)	-	-	-	64M
NOR FLASH (bits)	-	-	-	32M
PLLs+DLLs	1+2	1+2	2+2	2+2
OSC	1,±5% accuracy	1, ±5% accuracy	1,±5% accuracy	1,±5% accuracy
Hard core processor	-	Cortex-M3	-	Cortex-M3
USB PHY	USB 2.0 PHY	USB 2.0 PHY	-	-
ADC ¹	1	1	-	-
Total number of I/O banks	4	4	4	4
Max. I/O	102	102	106	106
Core voltage	1.2V	1.2V	1.2V	1.2V

optional PSRAM / HyperRAM and NOR FLASH

[dec.21] excerpt from GoWin GW1NSR handbook

- additional resources

FAE Redtree solution GoWIN introduction

<https://redtree-solutions.com/images/pdf/fpga-pld-basics-Gowin-webex-202106.pdf>

GW1NSR datasheets

<http://cdn.gowinsemi.com.cn/DS861E.pdf>

[Risc-V] AE350_SOC

<https://github.com/riscv-software-src/opensbi/blob/master/docs/platform/andes-ae350.md>

● RISC-V additional resources

RISC-V open specifications

<https://riscv.org/technical/specifications/>

RISC-V ISA (2019) <https://github.com/riscv/riscv-isa-manual/releases/download/Ratified-IMAFDQC/riscv-spec-20191213.pdf>

alibaba to open its RISC-V implementations (verilog) !

<https://github.com/T-head-Semi>

<https://www.cnx-software.com/2021/10/20/alibaba-open-source-risc-v-cores-xuantie-e902-e906-c906-and-c910/>

Microchip HelloFPGA

<https://www.microchip.com/en-us/products/fpgas-and-plds>

Microchip Mi-V Risc-V SOC FPGA architecture

Thales RISC-V softCore contest

CVA6 risc-v synthesis to Zybo z7-7020 target

<https://github.com/ThalesGroup/cva6-softcore-contest>

OpenHwGroup, Ariane/CVA6 Risc-V core, linux capable, 6 stages pipeline, out-of-order

<https://github.com/openhwgroup/cva6>

PicoRV32 - a size optimized RISC-V

<https://github.com/YosysHQ/picorv32>

RISC-V software sources to build various platforms

e.g Andes AE-350 (Gowin GW5AST)

<https://github.com/riscv-software-src/opensbi/blob/master/docs/platform/andes-ae350.md>

Traces team involved !




Part IIa - [Advanced] Xilinx Zynq architecture

- Zynq architecture overview,
- AXI bus,
- Hands-on lab: my first **soft IP**,
- Next lab: RISC-V integration ?



Zynq architecture overview

- Zynq SoC block diagram


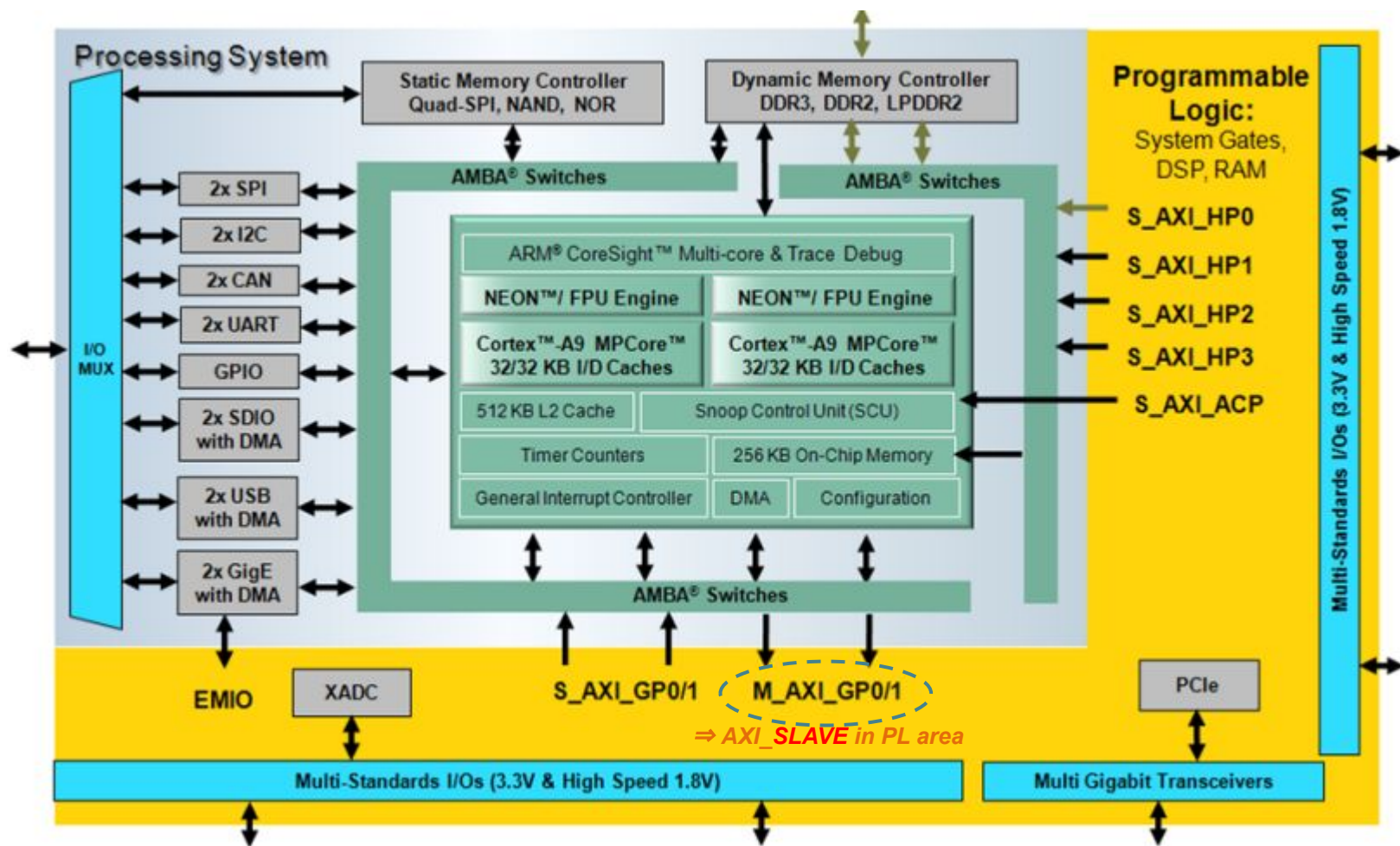


MIO / EMIO

- Multiplexed IO (MIO) are PS dedicated I/O

- ❖ 54 dedicated pins
- ❖ Software configurable
- ❖ IO banks 500 & 501

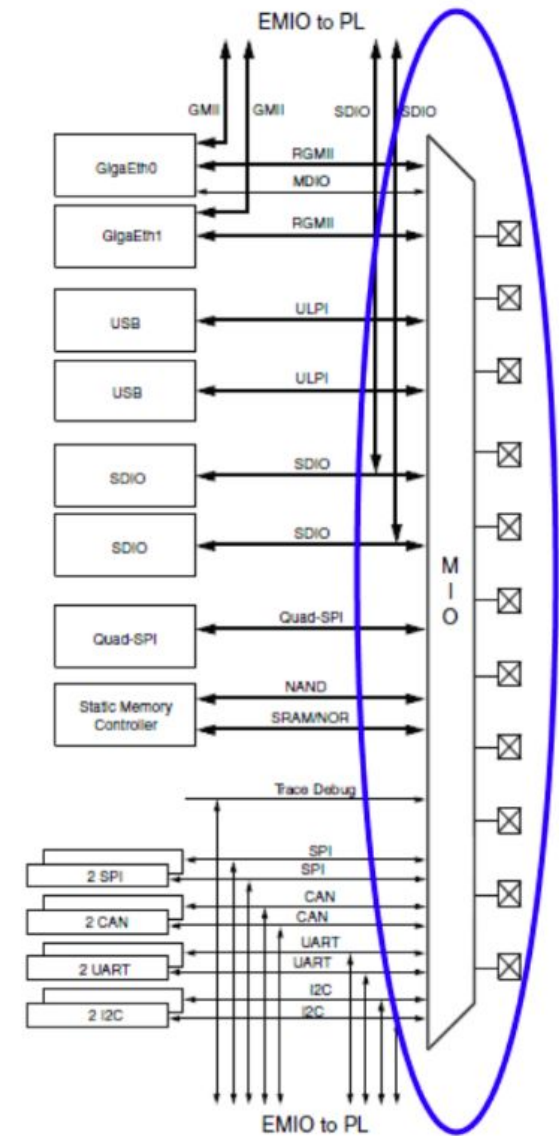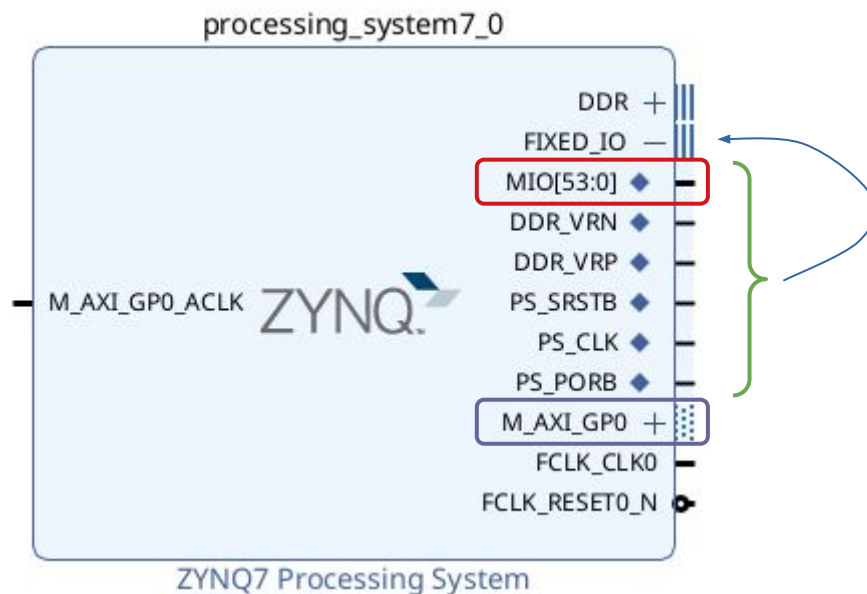https://secil.univ-tlse3.fr/teaching/francois/UE-M2-VHDL/ZYBO-Z7_schematic-D1.pdf





excerpt from Xilinx Zynq architecture slides

MIO / EMIO

- Extended Multiplexed IO (EMIO) enables PL access to PS I/O ports

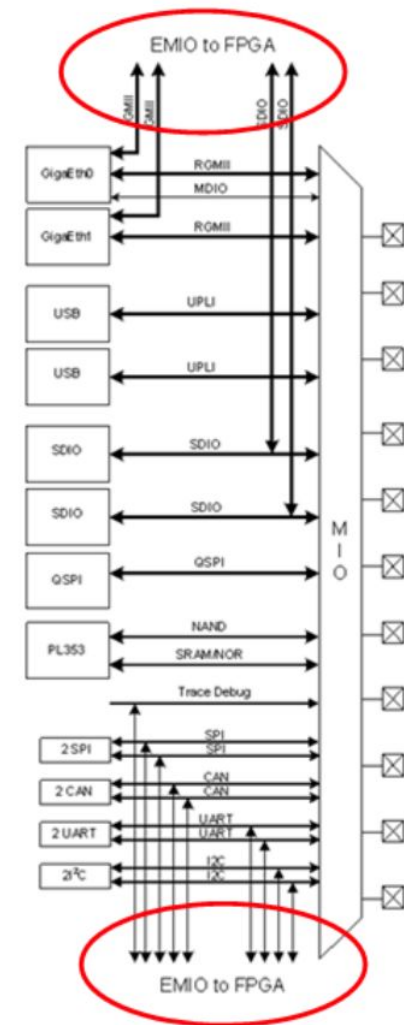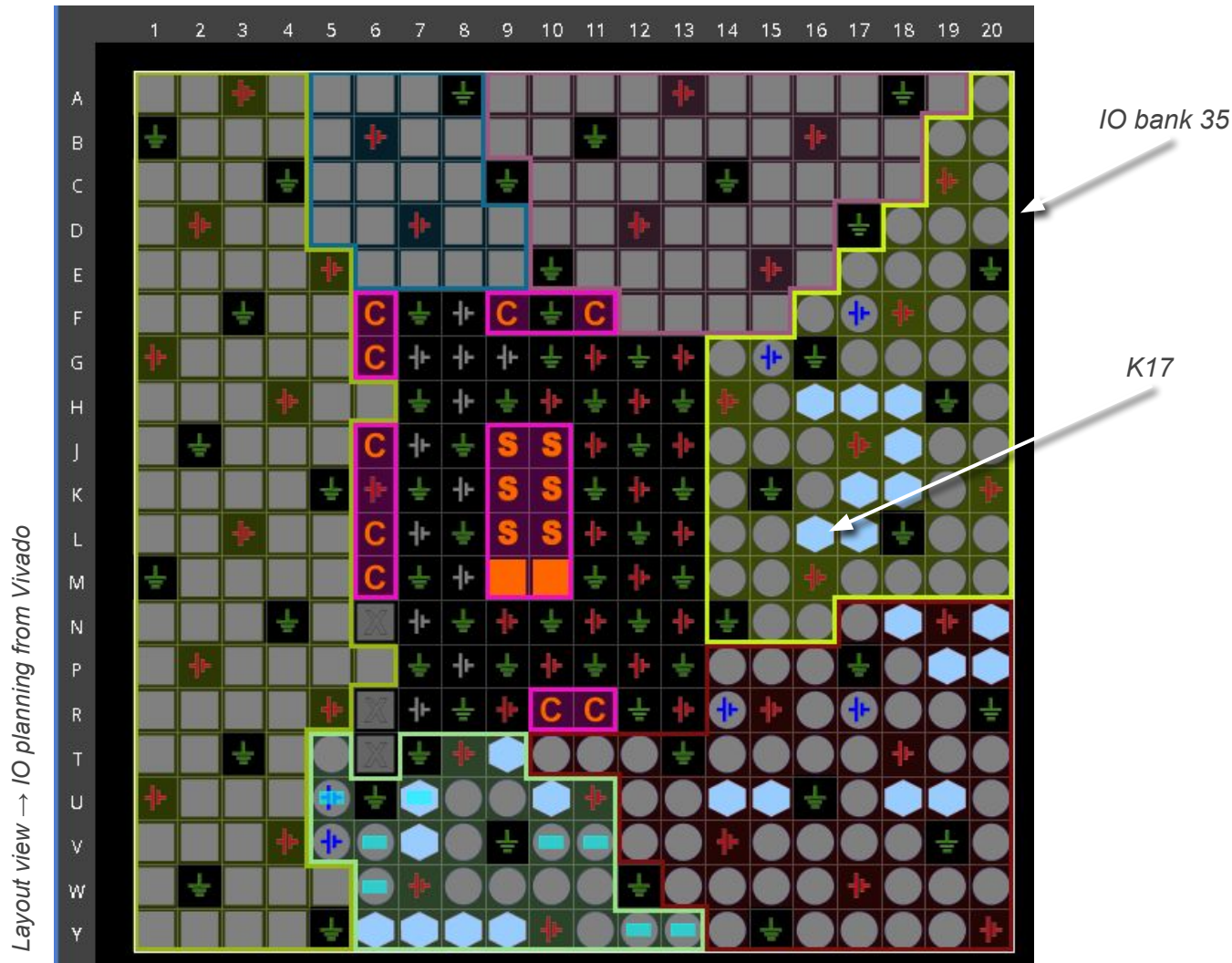❖ Broader range of I/O through PL accessible banks



excerpt from Xilinx Zynq architecture slides


Part IIa - [Advanced] Xilinx Zynq architecture

- Zynq architecture overview,
- AXI bus,
- Hands-on lab: my first **soft IP**,
- Next lab: RISC-V integration ?




AXI bus

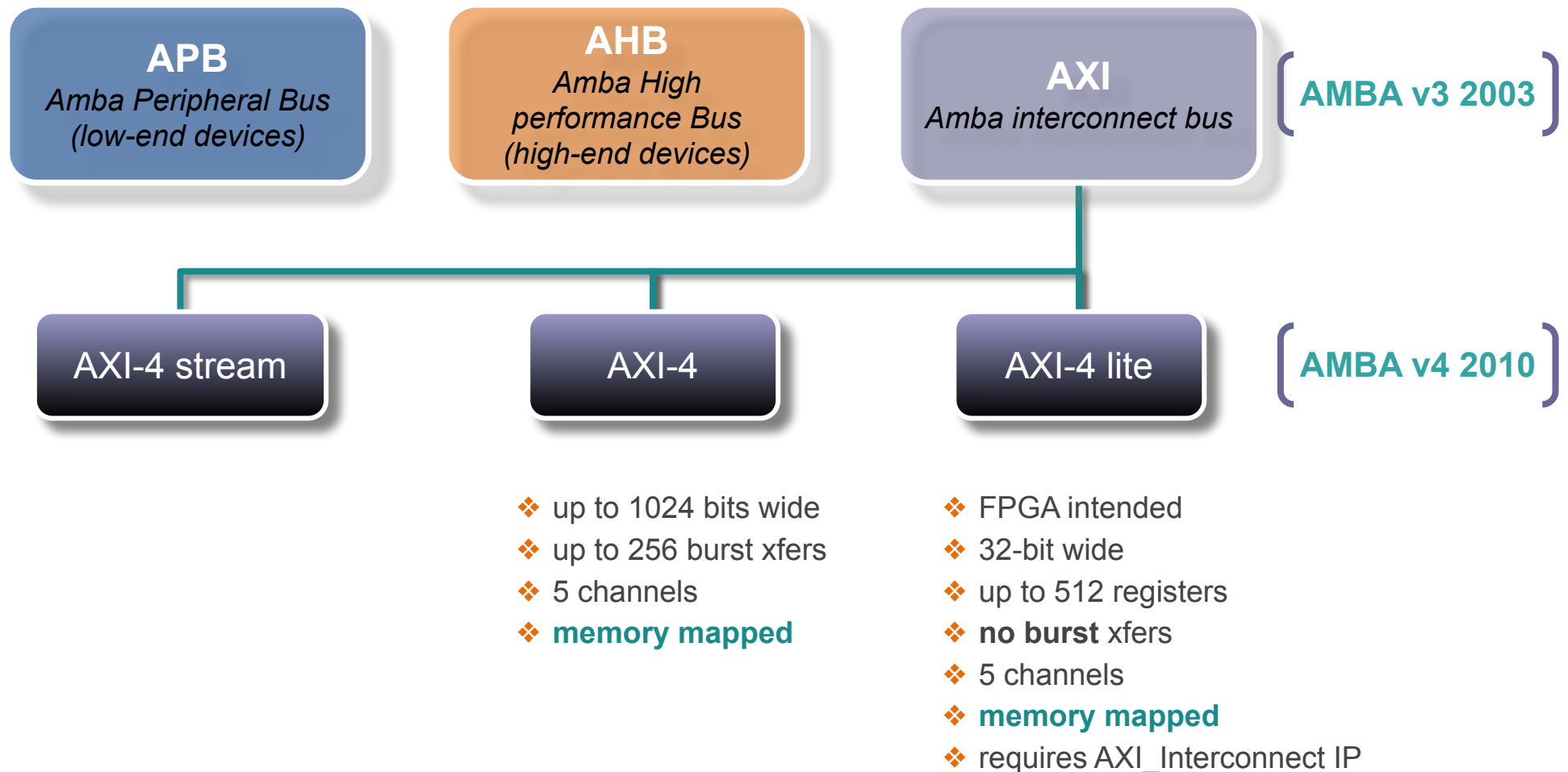- The Advanced Microcontroller Bus Architecture (AMBA) bus



AXI bus @ Zynq

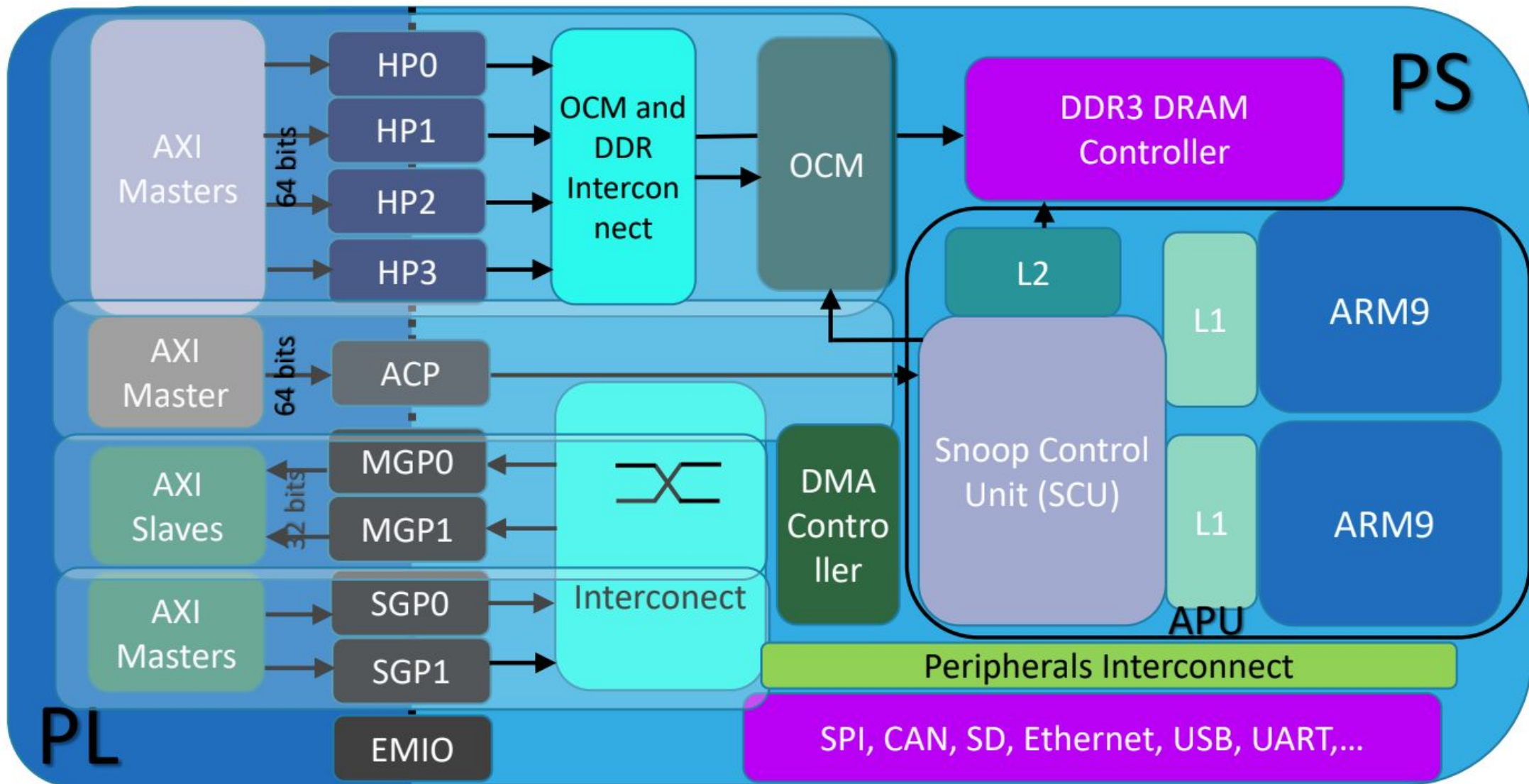

Excerpt from Cristian Sisterna slide 21 https://secil.univ-tlse3.fr/teaching/francois/UE-M2-VHDL/Sisterna_Zynq-architecture_C7T.pdf



AXI bus @ Zynq

- PS - PL interface: the **AXI** bus
 - ❖ AMBA evolution
 - ❖ memory mapped registers

AXI high-performance slave ports (HP0-HP3)

- ❖ Configurable 32-bit or 64-bit data width
- ❖ Access to OCM and DDR only
- ❖ Conversion to processing system clock domain
- ❖ AXI FIFO Interface (AFI) are FIFOs (1KB) to smooth large data transfers

AXI general-purpose ports (GP0-GP1)

- ❖ Two masters from PS to PL
- ❖ Two slaves from PL to PS
- ❖ 32-bit data width
- ❖ Conversion and sync to processing system clock domain

AXI bus @ Zynq


- PS - PL **AXI** interfaces synthesis

Interface Name	Interface Description	Master	Slave
M_AXI_GP0	General Purpose (AXI_GP)	PS	PL
M_AXI_GP1		PS	PL
S_AXI_GP0	General Purpose (AXI_GP)	PL	PS
S_AXI_GP1		PL	PS
S_AXI_ACP	Accelerator Coherency Port (ACP), cache coherent transaction	PL	PS
S_AXI_HP0	High Performance Ports (AXI_HP) with read/write FIFOs. (Note that AXI_HP interfaces are sometimes referred to as AXI Fifo Interfaces, or AFIs).	PL	PS
S_AXI_HP1		PL	PS
S_AXI_HP2		PL	PS
S_AXI_HP3		PL	PS

Excerpt from https://m2siame.univ-tlse3.fr/teaching/francois/UE-M2-VHDL/The_Zynq_Book_ebook_3.pdf p.32

AXI bus @ Zynq


- AXI4 and AXI4-lite bus channels

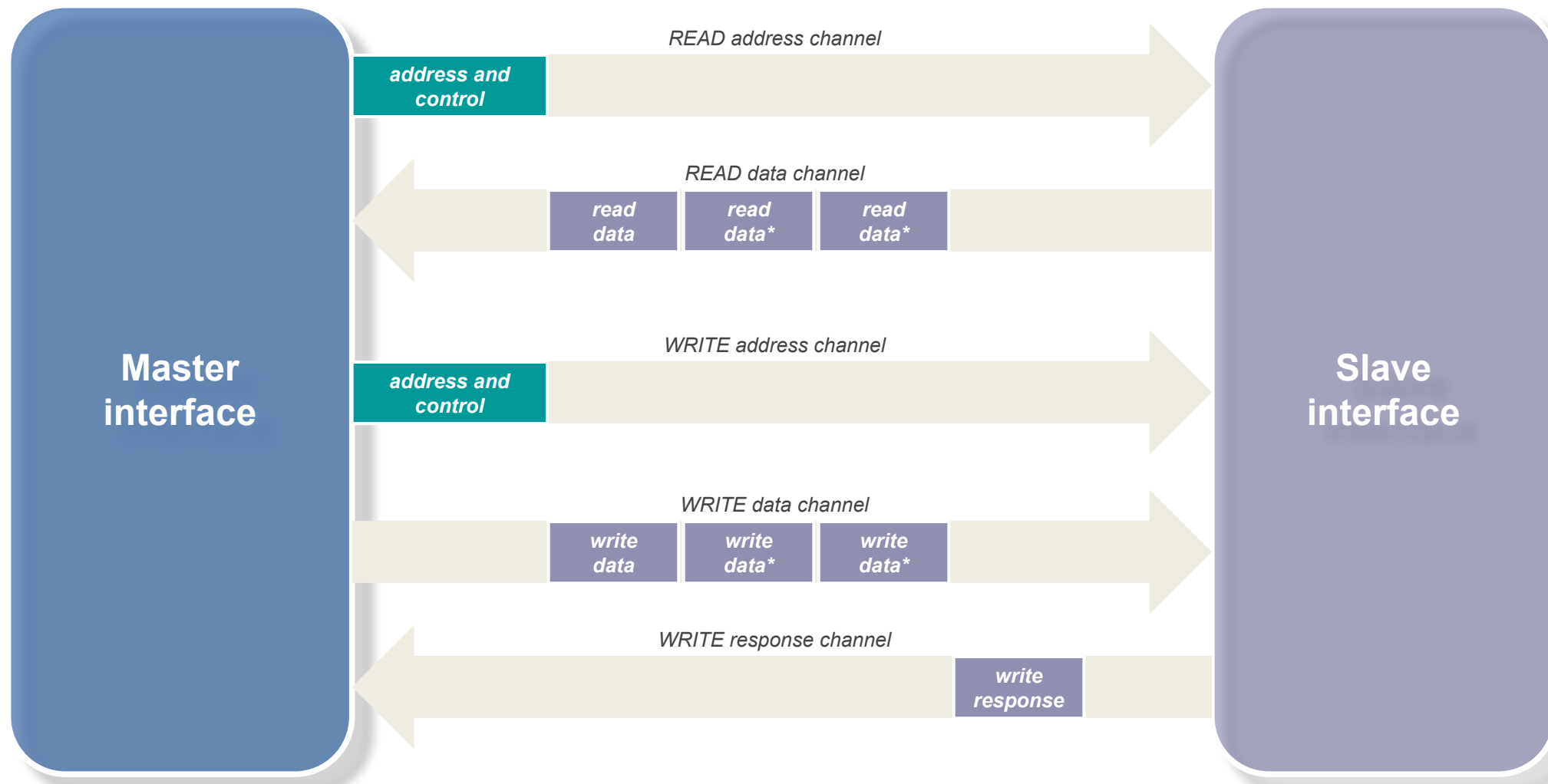

* no burst mode for AXI4-lite

AXI bus @ Zynq

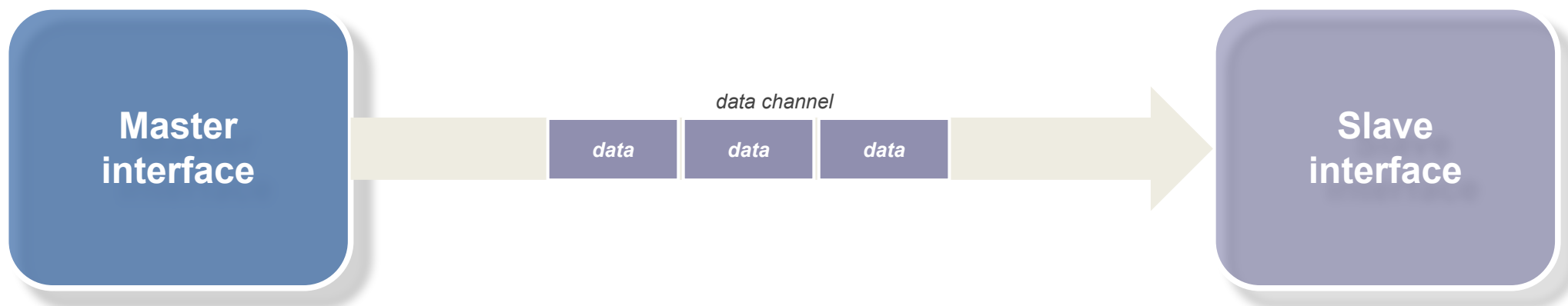- AXI4-stream bus channels
 - ❖ AXI4 "write data" channel
 - ❖ unlimited burst length





AXI bus @ Zynq

- AXI VHDL interface

Fixing Xilinx's Broken AXI-lite Design in VHDL


<https://zipcpu.com/blog/2021/05/22/vhdlaxil.html>

[sample] https://github.com/ZipCPU/wb2axip/blob/master/bench/formal/xlnxdemo_2020_2.vhd

DRAFT


Zynq PS-PL

- AXI bus @ Vivado

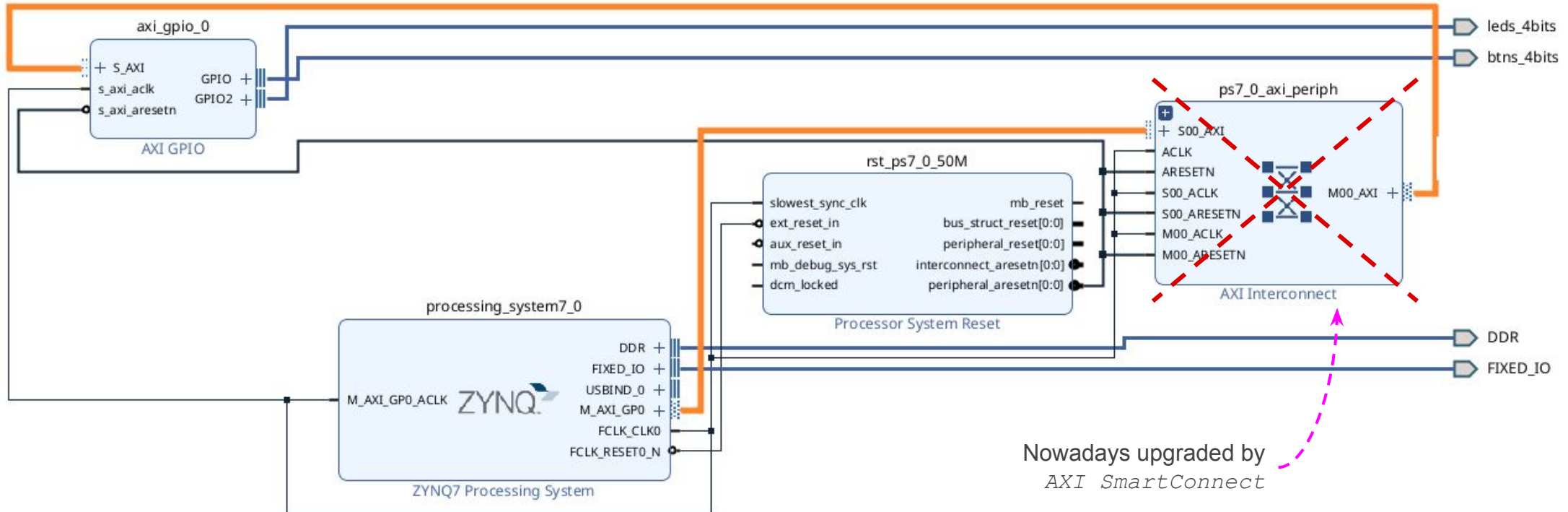

Zynq PS-PL

- AXI bus @ Vivado | new **AXI_smc** + AXI_slave <https://www.youtube.com/watch?v=UZ3yEFdgFVs>

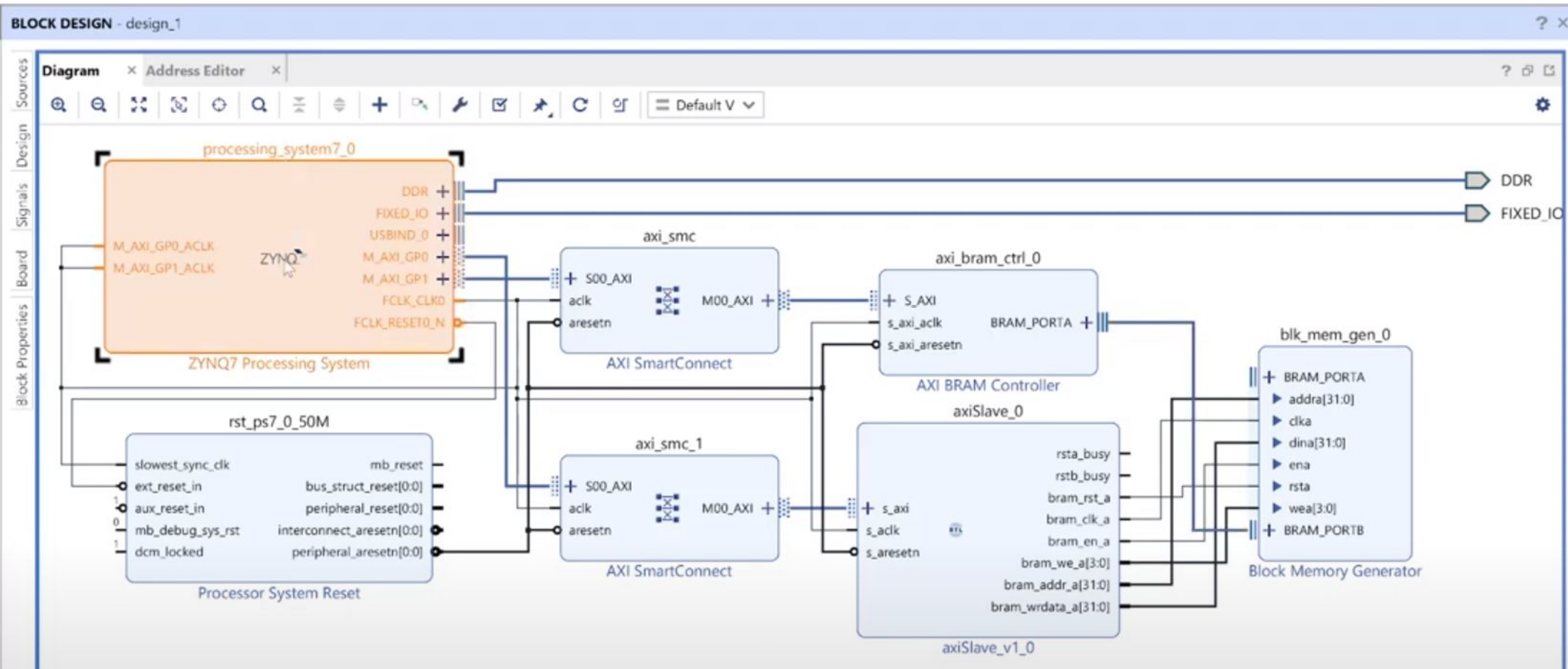

AXI SmartConnect (axi_smc)

<https://www.xilinx.com/products/intellectual-property/smartconnect.html>

AXI_smc is the AXI_Interconnect successor

WARNING: axi_smc is not intended to AXI4-lite !

Zynq PS Memory Map

● Memory Map


- The Cortex-A9 processor uses 32-bit addressing
- All PS peripherals and PL peripherals are memory mapped to the Cortex-A9 processor cores
- All slave PL peripherals will be located between 4000_0000 and 7FFF_FFFF (connected to GP0) and 8000_0000 and BFFF_FFFF (connected to GP1)

FFFC_0000 to FFFF_FFFF	OCM
FD00_0000 to FFFB_FFFF	Reserved
FC00_0000 to FCFF_FFFF	Quad SPI linear address
F8F0_3000 to FBFF_FFFF	Reserved
F890_0000 to F8F0_2FFF	CPU Private registers
F801_0000 to F88F_FFFF	Reserved
F800_1000 to F880_FFFF	PS System registers,
F800_0C00 to F800_0FFF	Reserved
F800_0000 to F800_0BFF	SLCR Registers
E600_0000 to F7FF_FFFF	Reserved
E100_0000 to E5FF_FFFF	SMC Memory
E030_0000 to E0FF_FFFF	Reserved
E000_0000 to E02F_FFFF	IO Peripherals
C000_0000 to DFFF_FFFF	Reserved
8000_0000 to BFFF_FFFF	PL (MAXI_GP1)
4000_0000 to 7FFF_FFFF	PL (MAXI_GP0)
0010_0000 to 3FFF_FFFF	DDR(address not filtered by SCU)
0004_0000 to 000F_FFFF	DDR(address filtered by SCU)
0000_0000 to 0003_FFFF	OCM

Zynq PS Memory Map

- AXI IP Memory Map setup

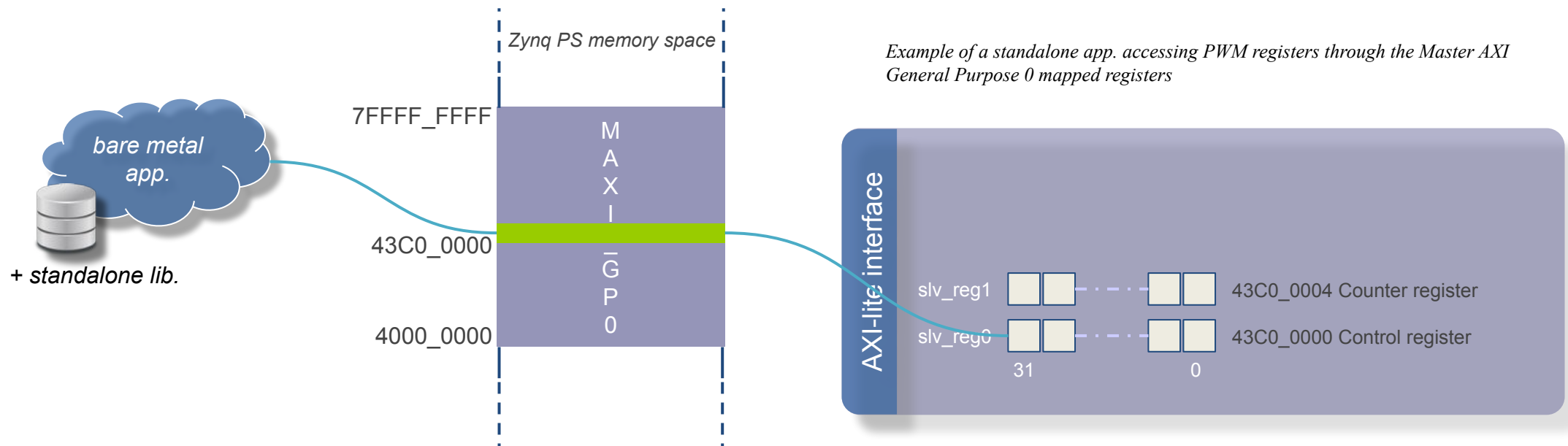- ❖ we'll setup base address of an AXI4 IP
- ❖ then we'll define the number of mapped registers
- ❖ hence accessing hardware is just a matter of memory accesses :)



- **Xilinx** additional related links

AXI IP creation

<https://indico.ictp.it/event/a14283/session/62/contribution/252/material/slides/2.pdf>

Create Custom AXI Cores

<https://www.hackster.io/cospan/create-custom-axi-cores-part-1-straight-to-the-finish-line-a70e5e>

Designing a Custom AXI IP on Vitis (software part while Vivado is HW part)

<https://www.hackster.io/pablotrujillojuan/designing-a-custom-axi-ip-on-vitis-a0ad06>

Zybo-z7-20 AXI_SMC + AXI_SLAVE (2022)

<https://www.youtube.com/watch?v=UZ3yEFdgFVs>

Master SECIL additional resources

<https://secil.univ-tlse3.fr/teaching/francois/UE-VHDL/>

→ have a look to Cristian Sisterna's slides and the "Xilinx Zynq Architecture" slides from Xilinx

Part IIa - [Advanced] Xilinx Zynq architecture

- Zynq architecture overview,
- AXI bus,
- Hands-on labs: my first **soft IP**,
- Next lab: RISC-V integration ?




[Lab] PWM generator


- generate a 1s pulse from the 125 MHz Ethernet clock @ Zybo

❖ adjustable duty cycle + enable/disable cmd

hint: you may use Zybo's switches

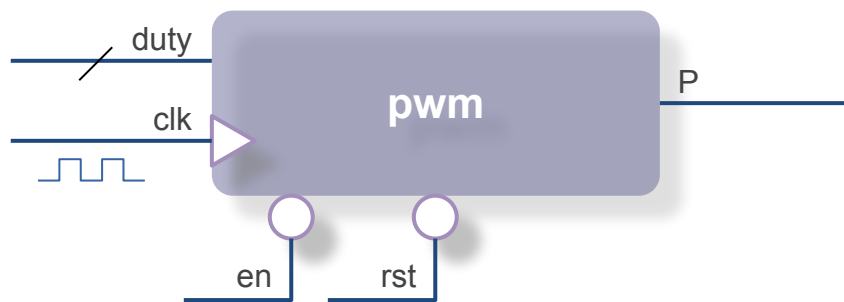

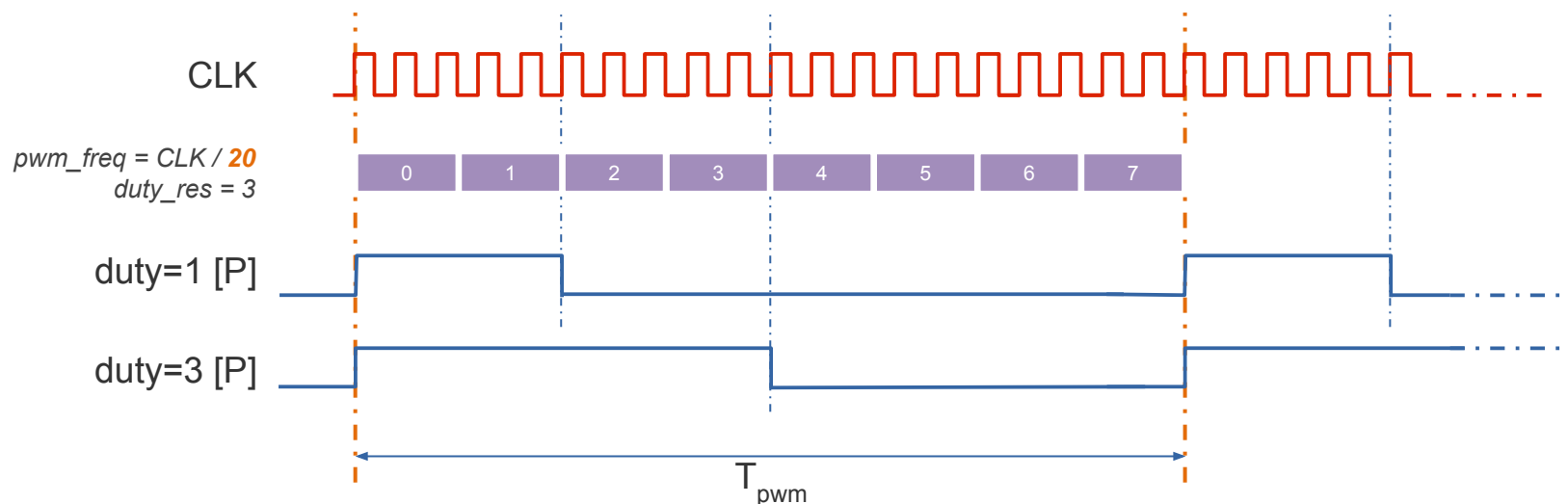
```
entity pwm is
  generic(
    sys_clk : natural := 1_000_000; --system clock in Hz
    pwm_freq: natural := 1E5; --PWM frequency in Hz
    duty_res : natural := 8 --duty-cycle resolution
  );
  port( RST,EN,CLK:in std_logic;
        DUTY: in std_logic_vector(duty_res-1 downto 0);
        P:out std_logic );
end pwm;
```



[Lab] PWM generator

- generate a 1s pulse from the 125 MHz Ethernet clock @ Zybo


inputs

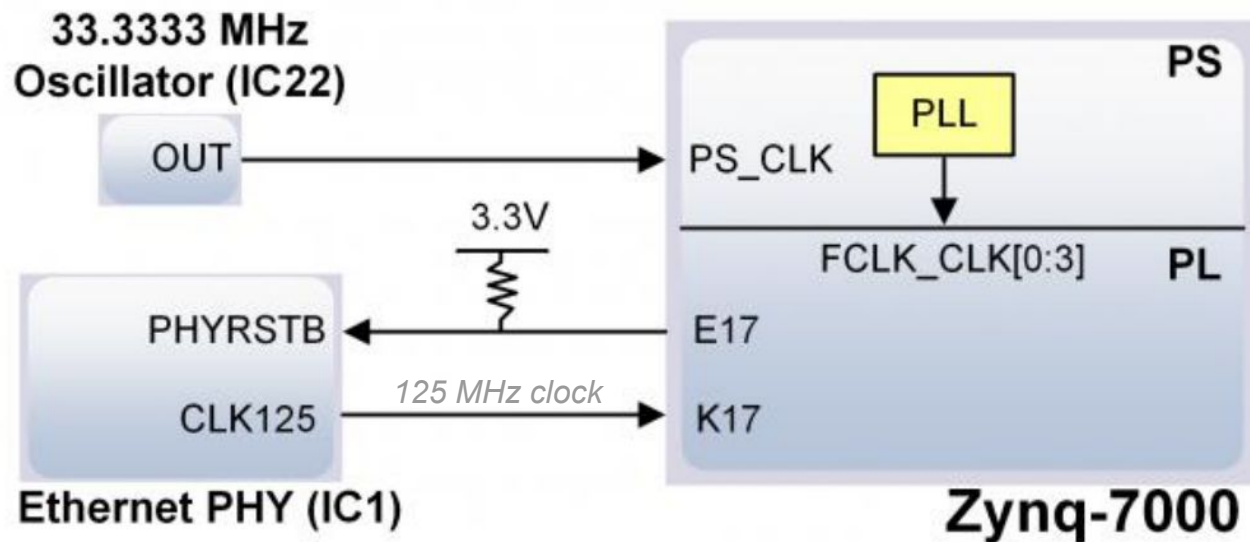

onboard
switches

output

onboard leds

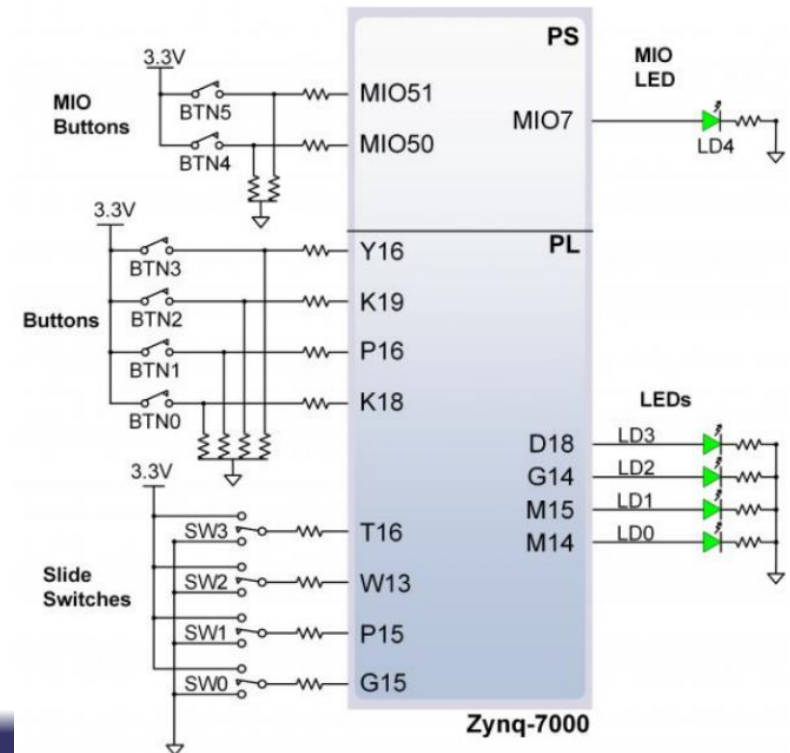



[Lab] PWM generator

- generate a 1s pulse from the 125 MHz Ethernet clock @ Zybo

pwm.xdc constraint file

```
# Master Clock timing constraint
create_clock -period 8.000 -name CLK -waveform {0.000 4.000} [get_ports CLK]
set_property PACKAGE_PIN K17 [get_ports CLK]
set_property IOSTANDARD LVCMOS33 [get_ports CLK]


set_property PACKAGE_PIN K18 [get_ports EN]
set_property IOSTANDARD LVCMOS33 [get_ports EN]
set_property PACKAGE_PIN P16 [get_ports RST]
set_property IOSTANDARD LVCMOS33 [get_ports RST]

set_property PACKAGE_PIN G15 [get_ports {DUTY[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DUTY[0]}]
set_property PACKAGE_PIN P15 [get_ports {DUTY[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DUTY[1]}]
set_property PACKAGE_PIN W13 [get_ports {DUTY[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DUTY[2]}]
set_property PACKAGE_PIN T16 [get_ports {DUTY[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {DUTY[3]}]

set_property PACKAGE_PIN D18 [get_ports P]
set_property IOSTANDARD LVCMOS33 [get_ports P]
```

[Lab] PWM generator Soft-IP

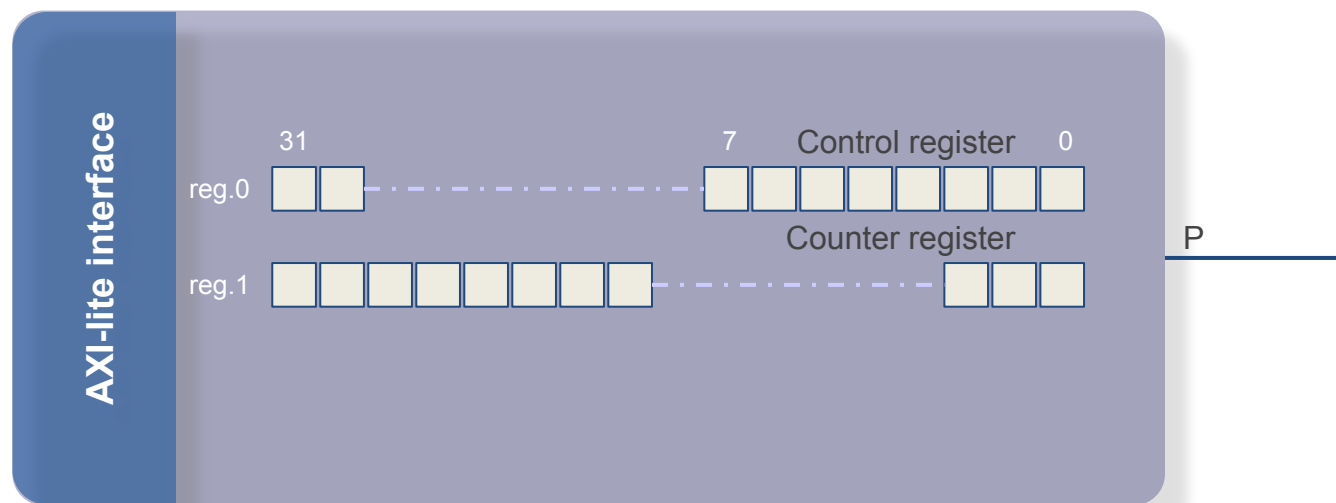- AXI compliant PWM generator
 - ❖ AXI-enabled internal registers to control and monitor




AXI IP creation

<https://indico.ictp.it/event/a14283/session/62/contribution/252/material/slides/2.pdf>

[Lab] PWM generator Soft-IP


● AXI-PWM IP internals

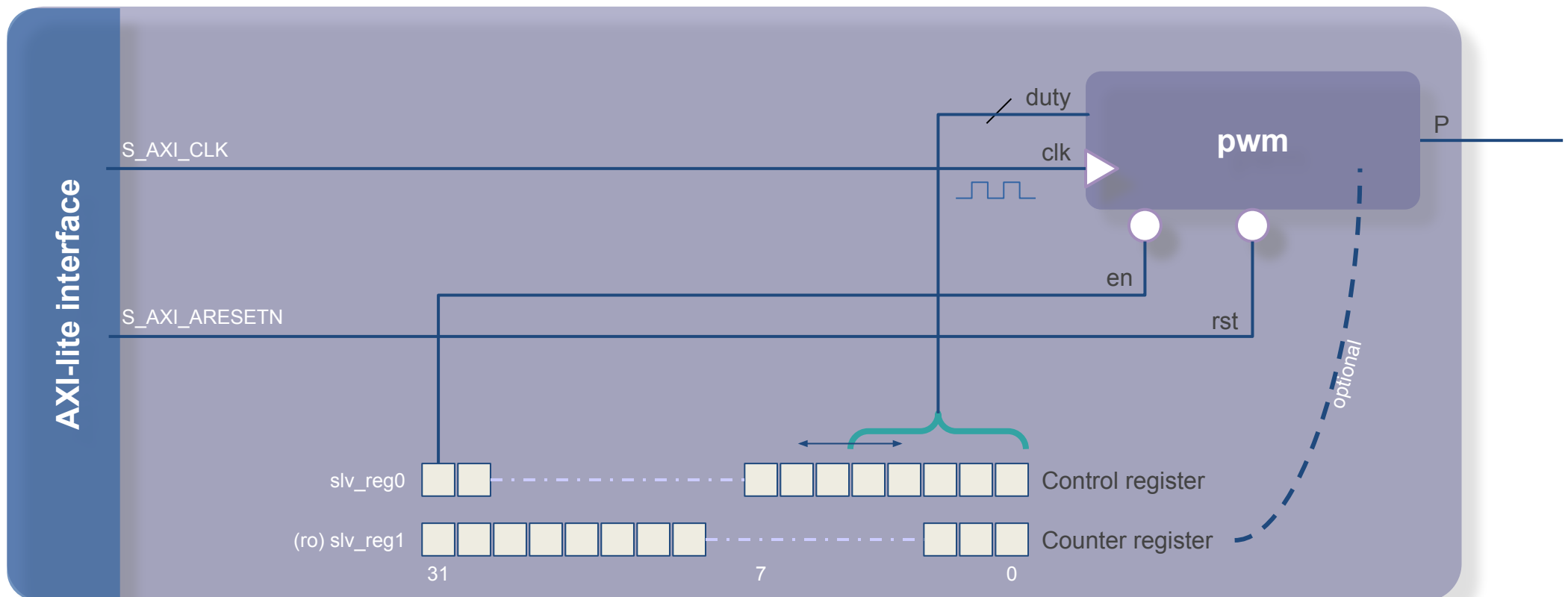- ❖ [reg.0] control register **duty-bits** size depends on generic parameter
- ❖ [reg.0] bit 31 is enable(0) or disable(1)
- ❖ [reg.1] counter register (read-only) is your PWM tick counter*
* $2^{32} \Rightarrow \text{SYS_CLK max} > 4\text{GHz}$




[Lab] Soft-IP block design integration

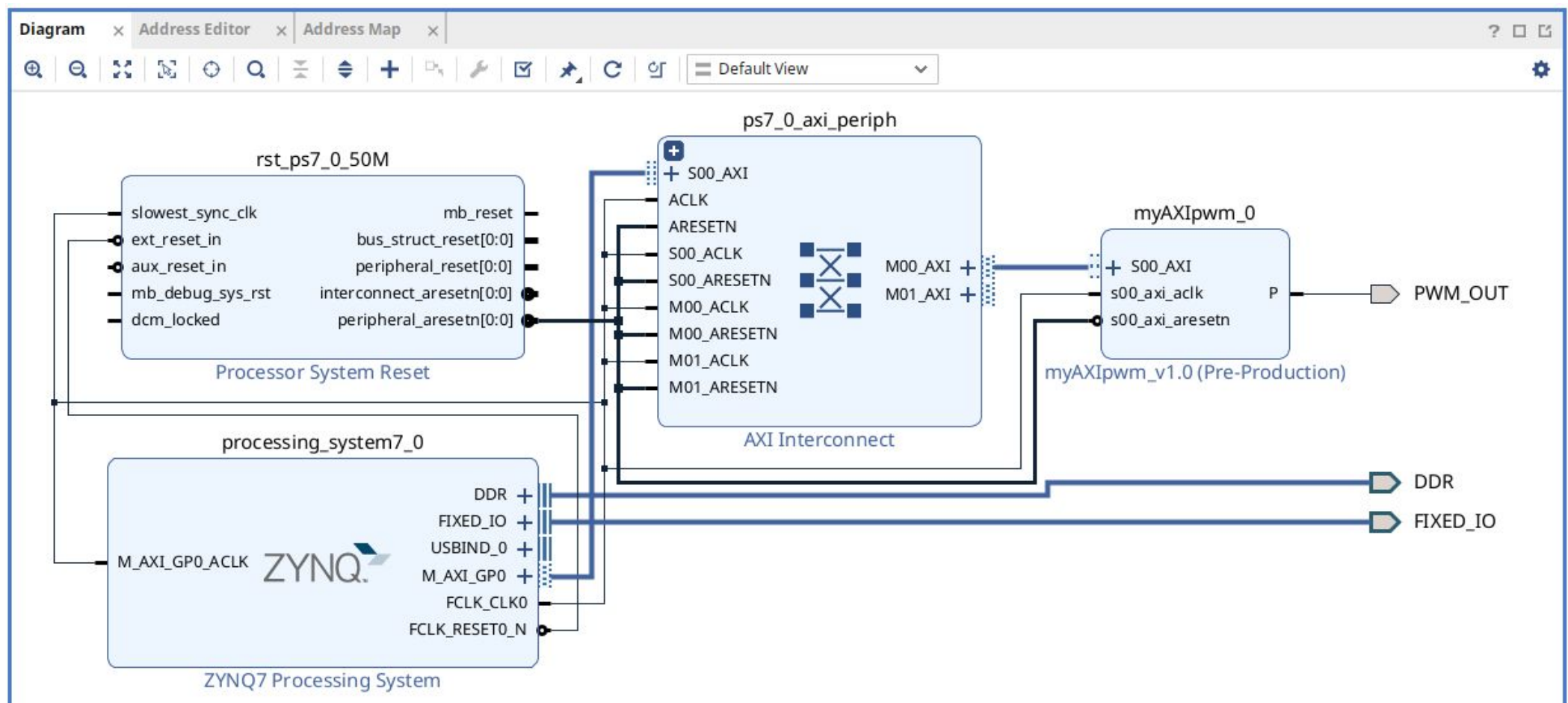- Generate a Block design featuring:
 - ❖ Zynq PS + *generate Block Design (BD)*
 - ❖ add your AXI-PWM **Soft-IP** + PWM_OUT port




[Lab] Soft-IP block design integration

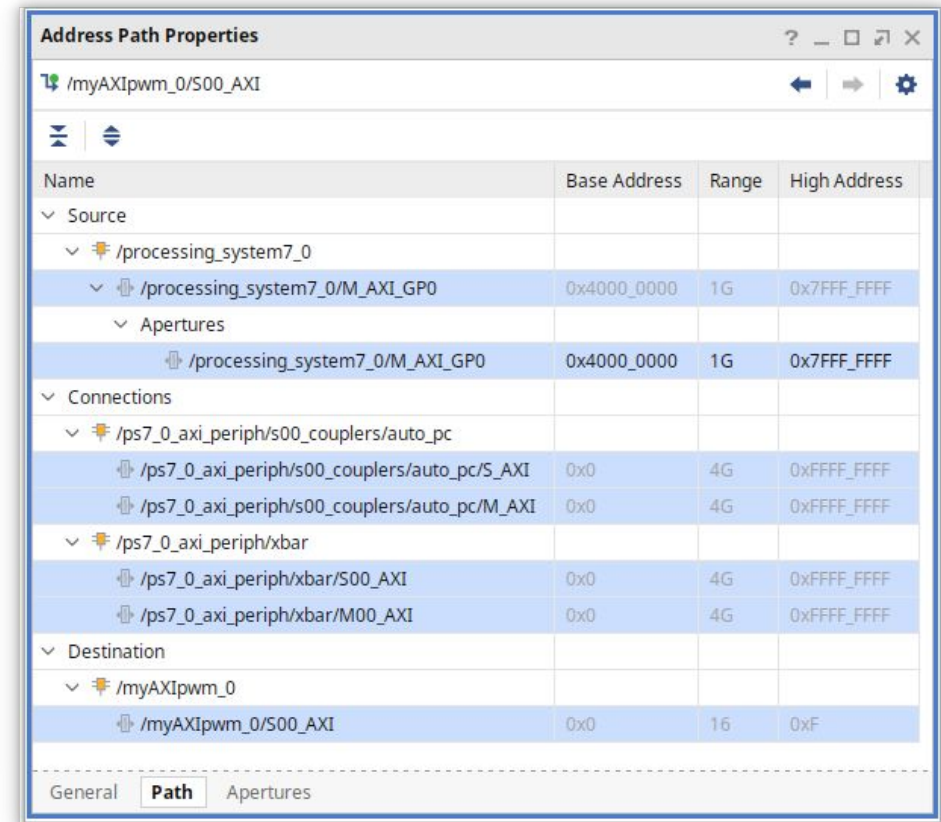- Block Design configuration:
 - ❖ PWM **Soft-IP** generic parameters
 - ❖ Memory mapped registers base address
 - ❖ add constraint: PWM_OUT → D18 pin



Name	Base Address	Range	High Address
Source			
/processing_system7_0			
/processing_system7_0/M_AXI_GP0	0x4000_0000	1G	0x7FFF_FFFF
Apertures			
/processing_system7_0/M_AXI_GP0	0x4000_0000	1G	0x7FFF_FFFF
Connections			
/ps7_0_axi_periph/s00_couplers/auto_pc			
/ps7_0_axi_periph/s00_couplers/auto_pc/S_AXI	0x0	4G	0xFFFF_FFFF
/ps7_0_axi_periph/s00_couplers/auto_pc/M_AXI	0x0	4G	0xFFFF_FFFF
/ps7_0_axi_periph/xbar			
/ps7_0_axi_periph/xbar/S00_AXI	0x0	4G	0xFFFF_FFFF
/ps7_0_axi_periph/xbar/M00_AXI	0x0	4G	0xFFFF_FFFF
Destination			
/myAXIpwm_0			
/myAXIpwm_0/S00_AXI	0x0	16	0xF

General Path Apertures

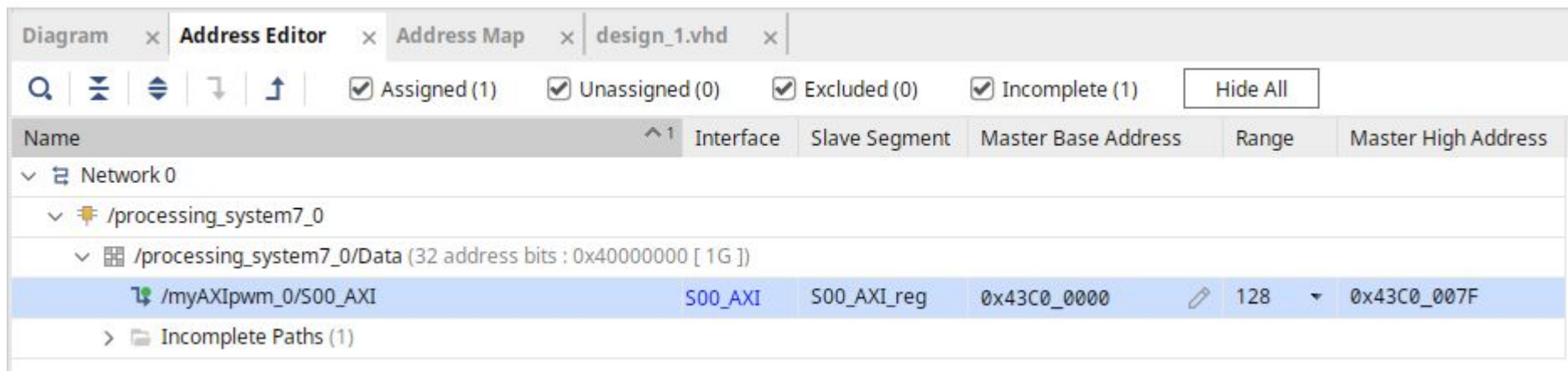

Name	Interface	Slave Segment	Master Base Address	Range	Master High Address
Network 0					
/processing_system7_0					
/processing_system7_0/Data (32 address bits : 0x40000000 [1G])					
/myAXIpwm_0/S00_AXI	S00_AXI	S00_AXI_reg	0x43C0_0000	128	0x43C0_007F
> Incomplete Paths (1)					


[Lab] Soft-IP block design integration

- Synthesis

You'll need to create a HDL-wrapper since your design does not feature any top-level component (right-click)



- Implementation

- Bit stream

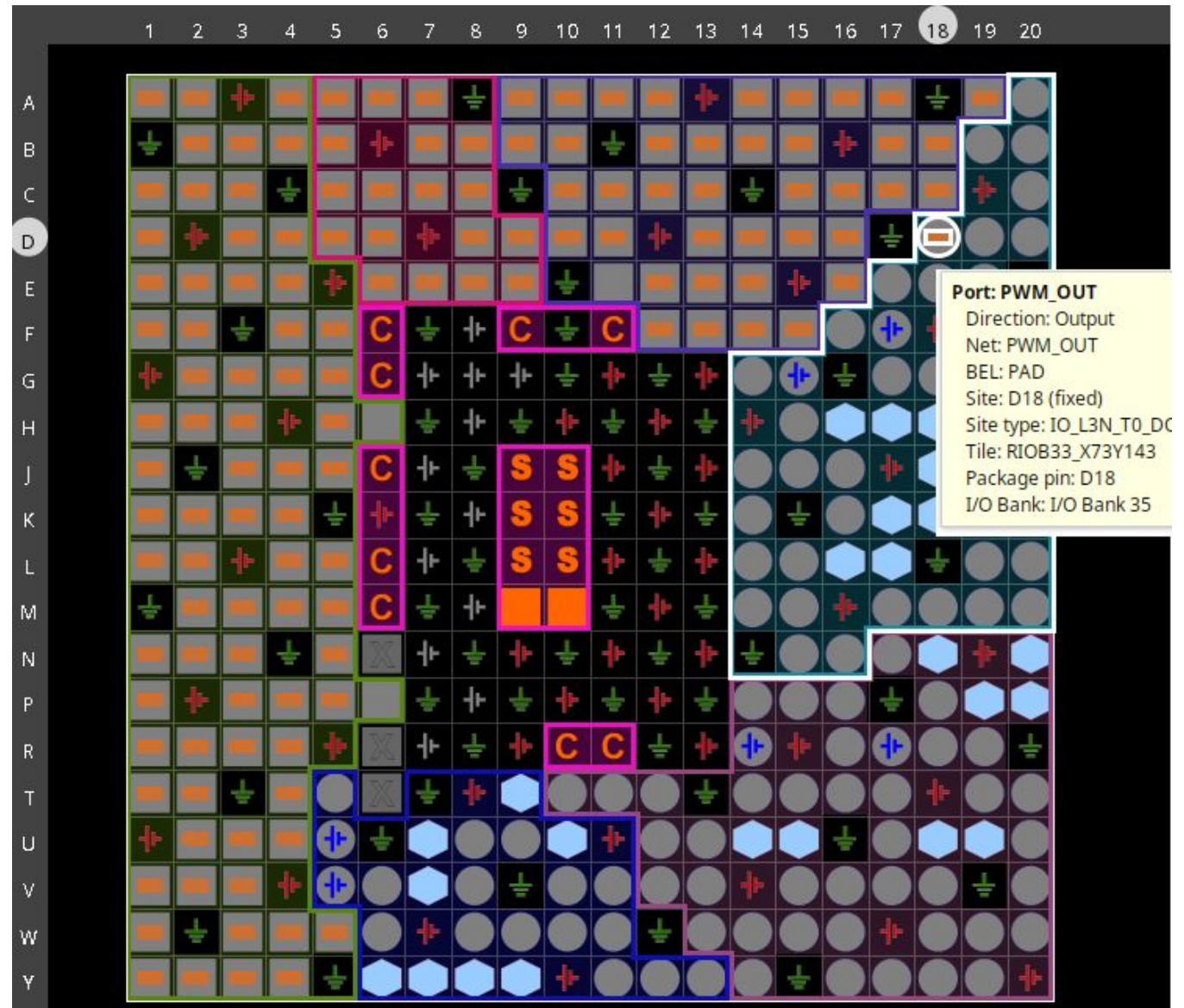




[Lab] PWM generator app.

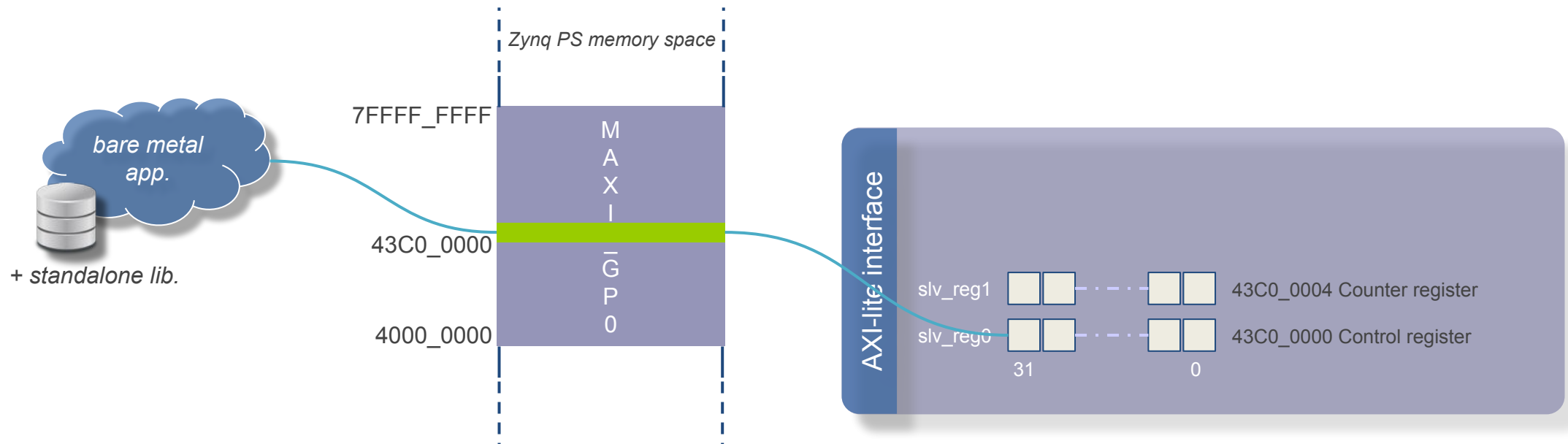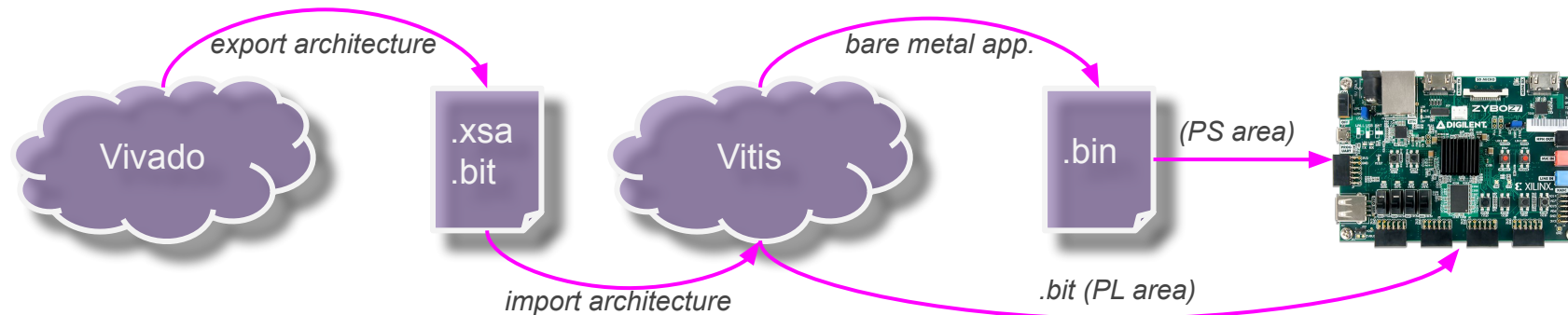- CPU interactions with your AXI-enabled PWM generator



[Lab] Rotary encoder

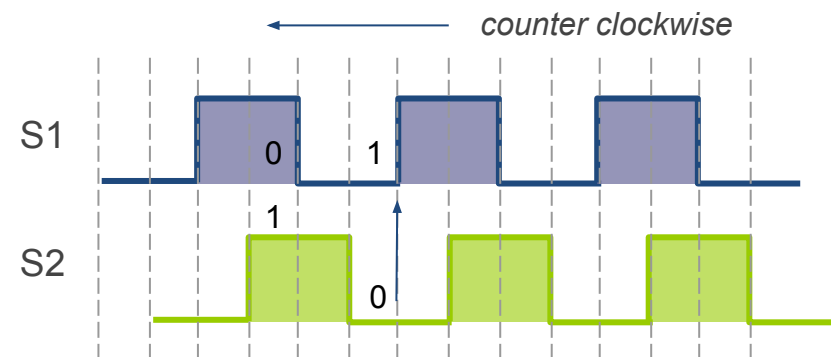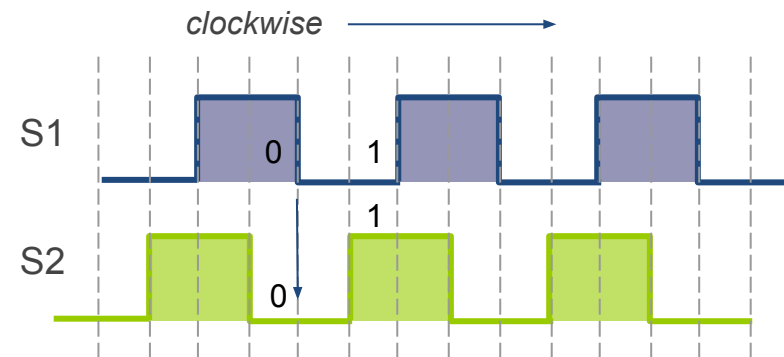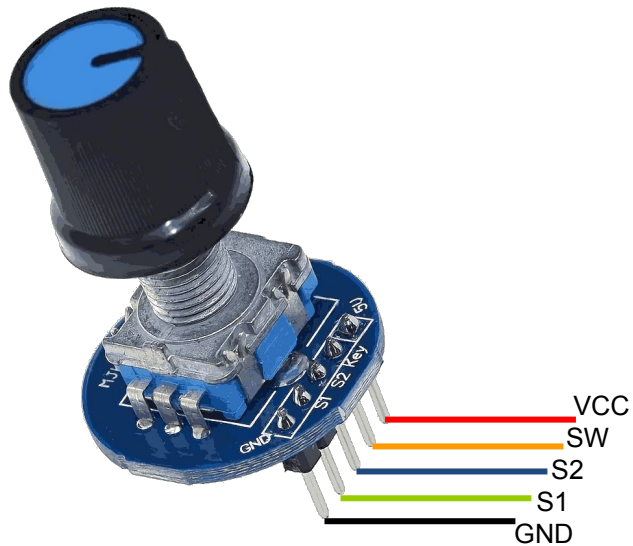- IP rotary encoder
an endless rotary knob



<https://lastminuteengineers.com/rotary-encoder-arduino-tutorial/>

<https://howtomechatronics.com/tutorials/arduino/rotary-encoder-works-use-arduino/>

<https://github.com/Yourigh/Rotary-encoder-VHDL-design>

[Lab] Rotary encoder

- Pmod connection

- ❖ MIO signals from PS part
- ❖ JE pins are 200ohm protected
- ❖ High speed Pmod ports only for fast differential signaling

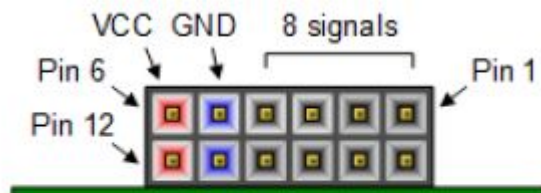
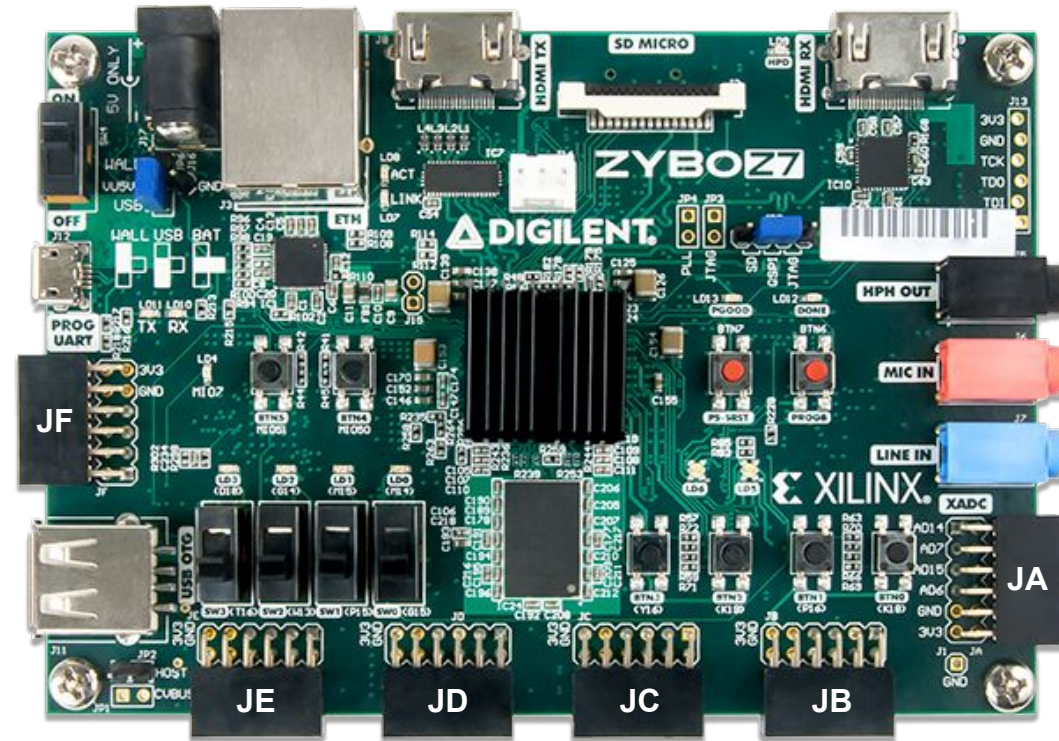



Figure 20. PMOD connectors; front view, as loaded on PCB.

	Pmod JA	Pmod JB*	Pmod JC	Pmod JD	Pmod JE	Pmod JF
Pmod Type	XADC	High-Speed	High-Speed	High-Speed	Standard	MIO
Pin 1	N15	V8	V15	T14	V12	MIO-13
Pin 2	L14	W8	W15	T15	W16	MIO-10
Pin 3	K16	U7	T11	P14	J15	MIO-11
Pin 4	K14	V7	T10	R14	H15	MIO-12
Pin 7	N16	Y7	W14	U14	V13	MIO-0
Pin 8	L15	Y6	Y14	U15	U17	MIO-9
Pin 9	J16	V6	T12	V17	T17	MIO-14
Pin 10	J14	W6	U12	V18	Y17	MIO-15

MIO signals are related to the PS part

[Lab] Soft-IP Rotary encoder

- AXI compliant Rotary Encoder IP block

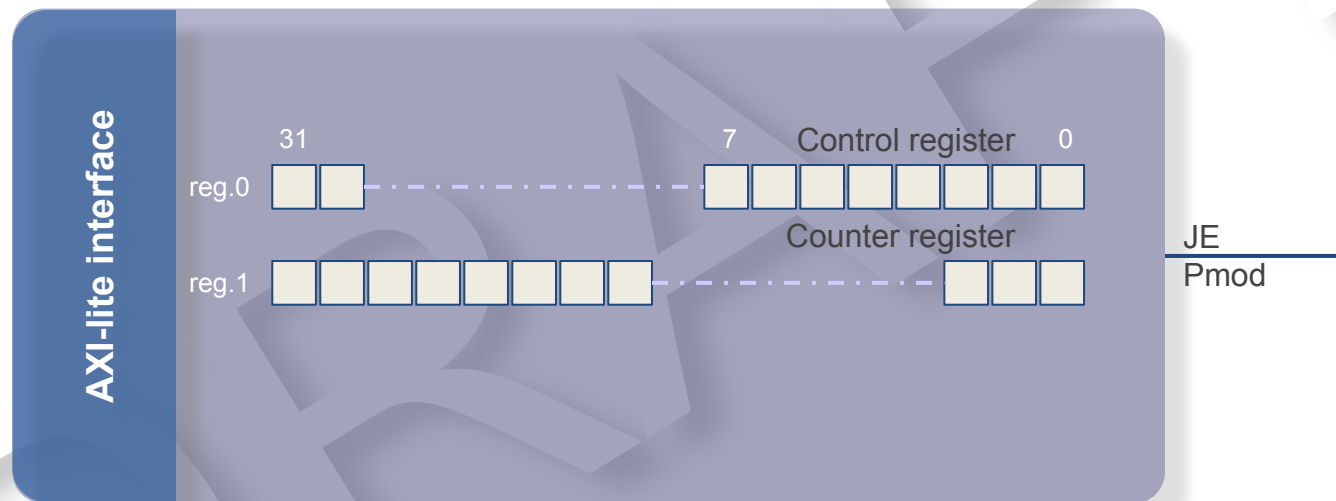



[Lab] Soft-IP Brushless controller

- AXI compliant Brushless engine controller IP block

DRAFT



[Lab] Zybo booting Linux :D

- Petalinux or ARMBian

DRAFT



[Lab] Digilent Zybo resources

- Digilent getting started:
<https://digilent.com/reference/programmable-logic/guides/start>
[Zybo-Z7] <https://digilent.com/reference/programmable-logic/zybo-z7/start>
- Vivado & Vitis for Bare Metal Software Projects
<https://digilent.com/reference/programmable-logic/guides/getting-started-with-ipi>
- Zybo-Z7-Petalinux
<https://digilent.com/reference/programmable-logic/zybo-z7/demos/petalinux>
<https://github.com/Digilent/Zybo-Z7/tree/20/Petalinux/master>


[Lab] Ministar 7-segments

- **[7 segments display]** Ministar dev. board | hardware setup

❖ IO cabling

7seg.	FPGA	GPIO*
a	30	[0]
b	32	[1]
c	35	[2]
d	33	[3]
e	42	[4]
f	44	[5]
g	46	[6]
dp	40	[7]
dig1	34	[11]
dig2	31	[10]
dig3	29	[9]
dig4	27	[8]

* software only version

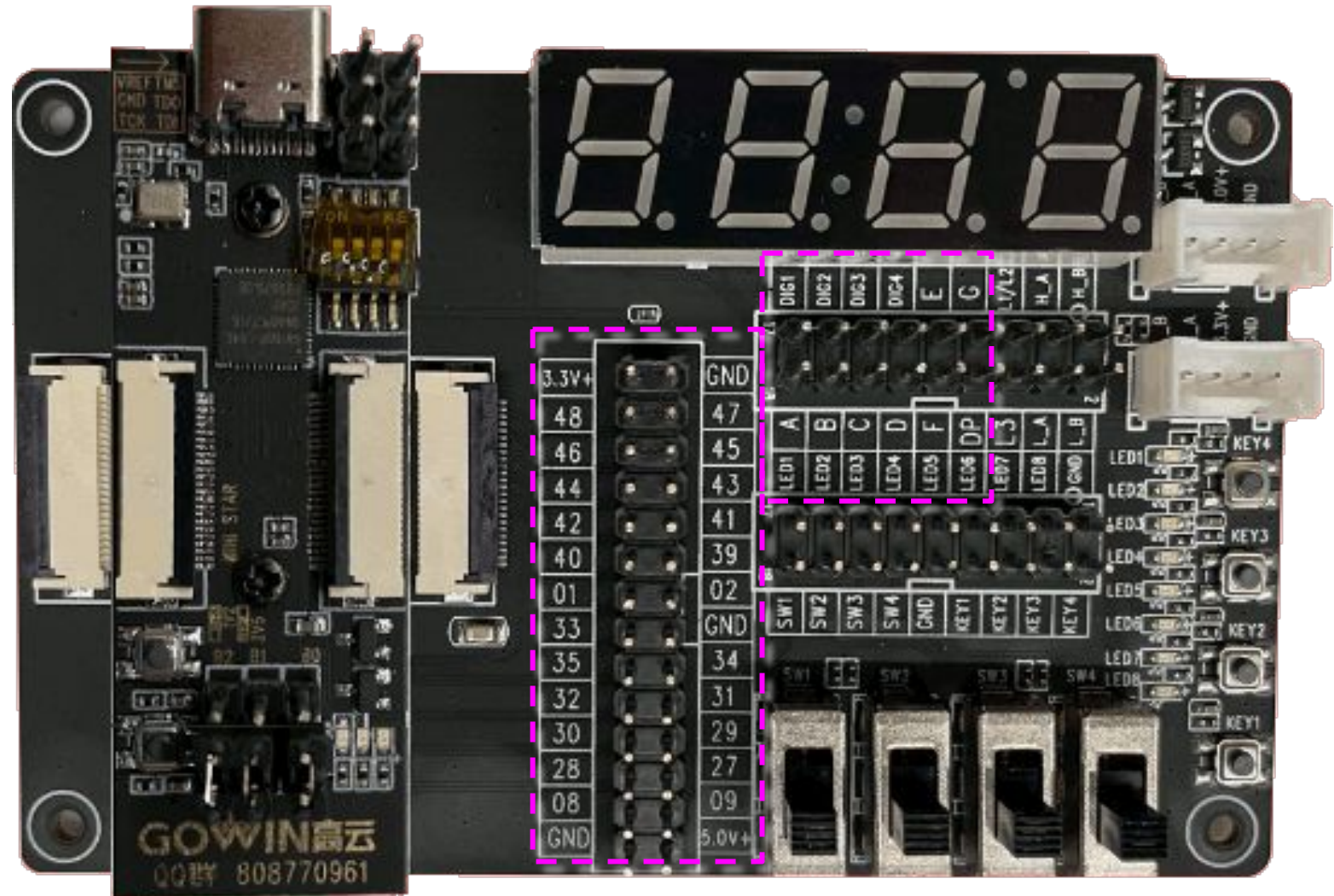


https://github.com/magicjellybeanfpga/MiniStar/tree/main/projects/Tutorials/Digital%20Tube%20Demo/seg_run



[Lab] Ministar 7-segments

- Ministar dev. board | 7 seg. displays

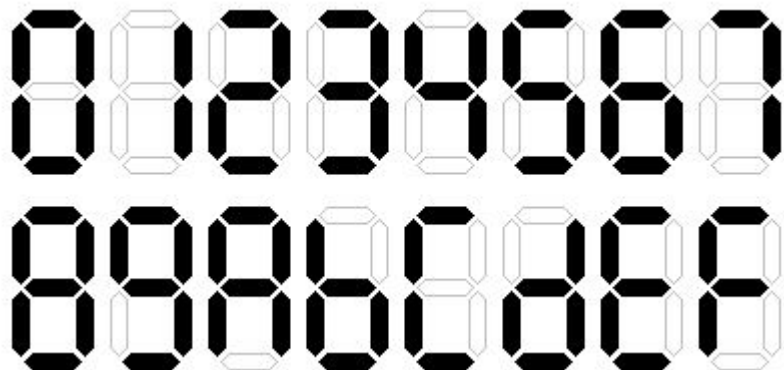- ❖ Inverted logic (7 seg. leds)
- ❖ can display hex values




Note: you may add the temperature symbol

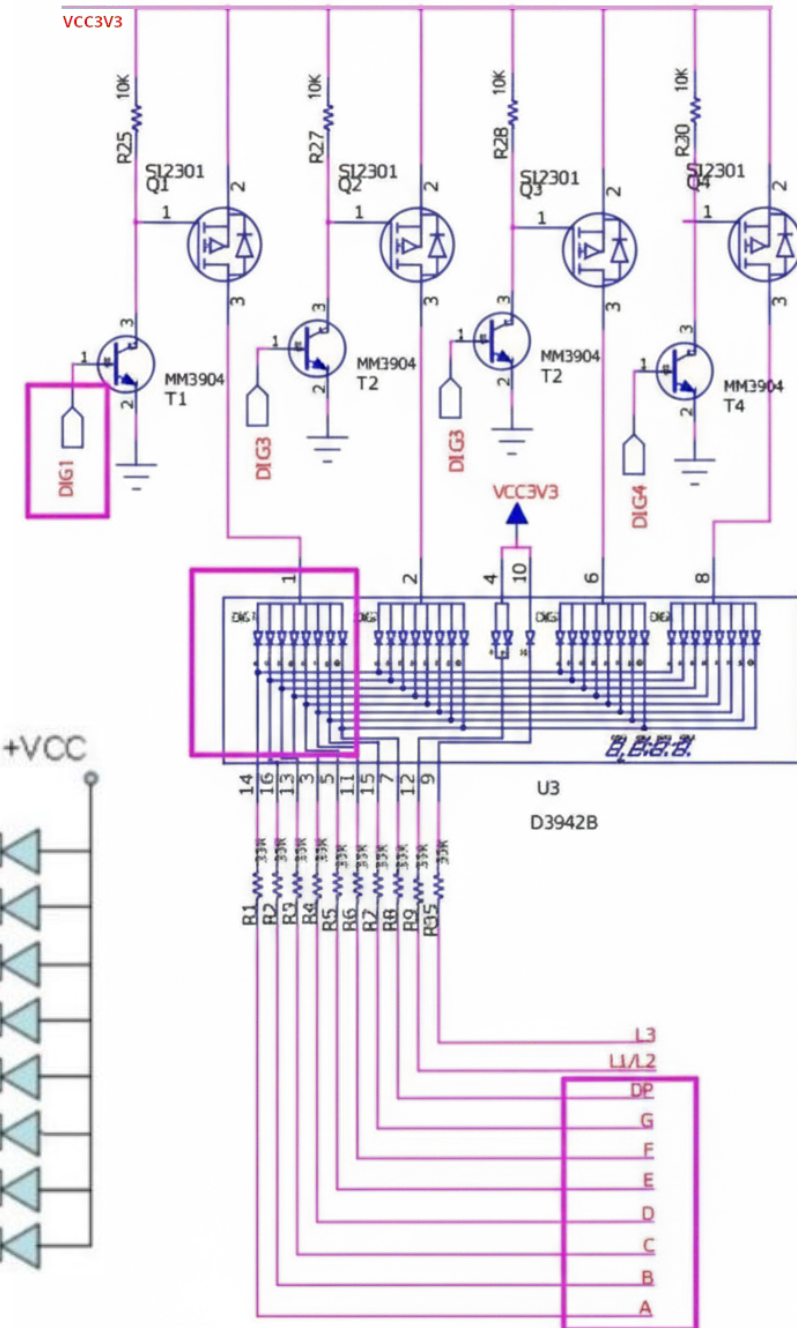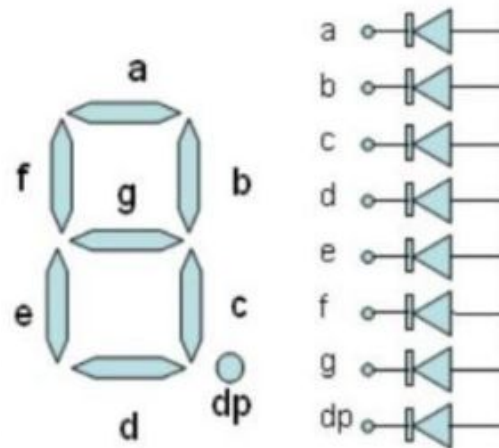

[Lab] Ministar 7-segments

[Part1] 7 segment:
GPIO tutorial

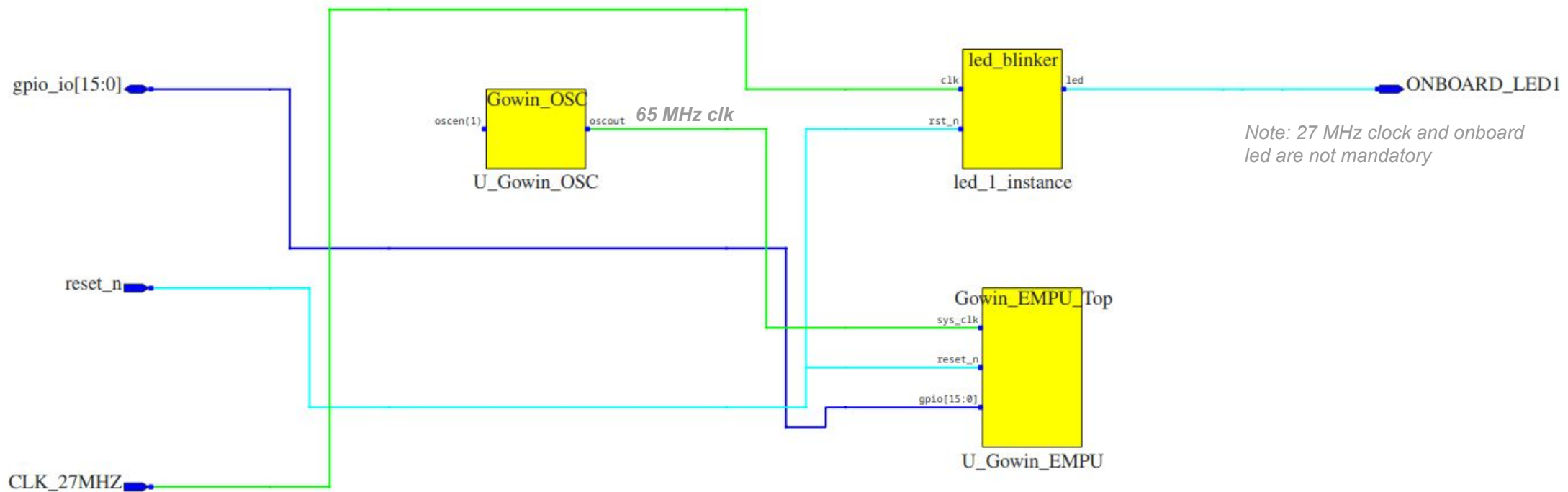- [FPGA] EMPU GPIO driven 7 seg. digits
 - ❖ EMPU = Cortex M3 + AHB-GPIO interface + **4KB** SRAM
 - ❖ OSC = Fosc (260MHz) / 4 $\Rightarrow$ 63 MHz EMPU clock
 - ❖ Make use of one of the onboard push buttons as 'reset_n' signal




[Lab] Ministar 7-segments

[Part1] 7 segment:
GPIO tutorial

- [EMPU] EMPU GPIO driven 7 seg. digits

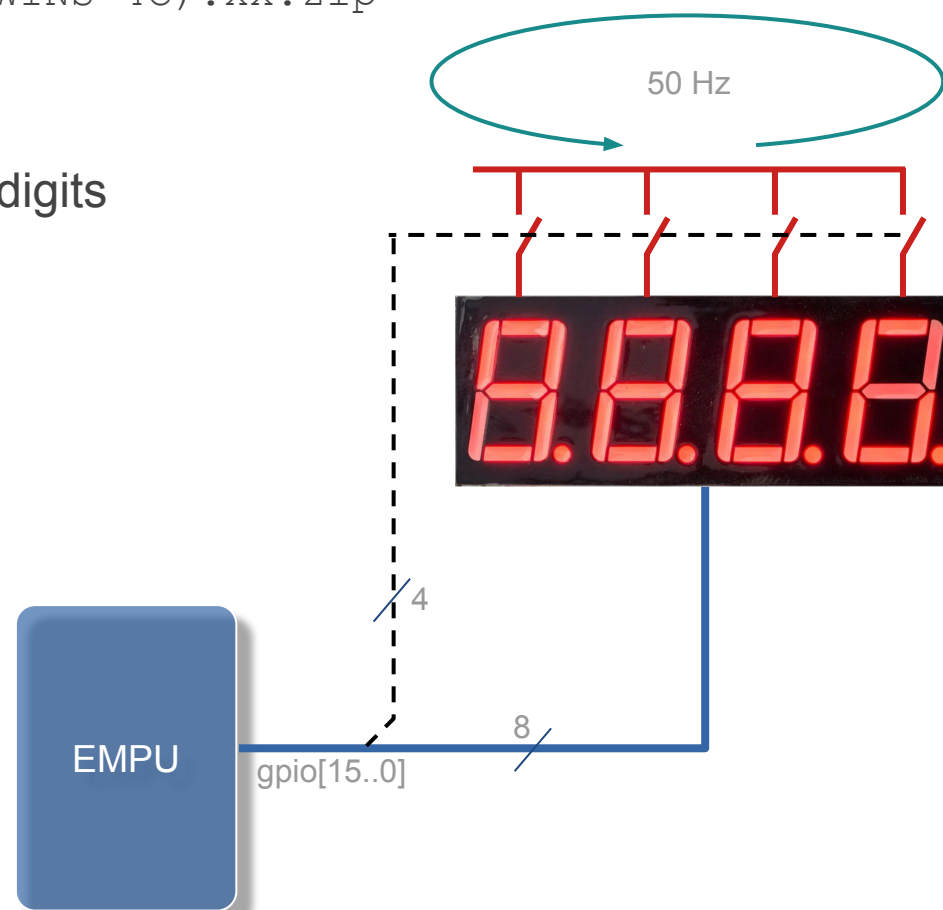
- ❖ Make use of installed GW1NS-4C libraries
i.e EMPU's libraries files → make use of GOWIN_EMPU_GW1NS_4C env. var.
or extract your own from 'Gowin_EMPU (GW1NS-4C) .xx.zip'
- ❖ Launch 'gowin_gmd' IDE
- ❖ Write an app. that will cycle through the digits



[Lab] Ministar 7-segment Soft-IP

[Part2] 7 segment:
Soft-IP

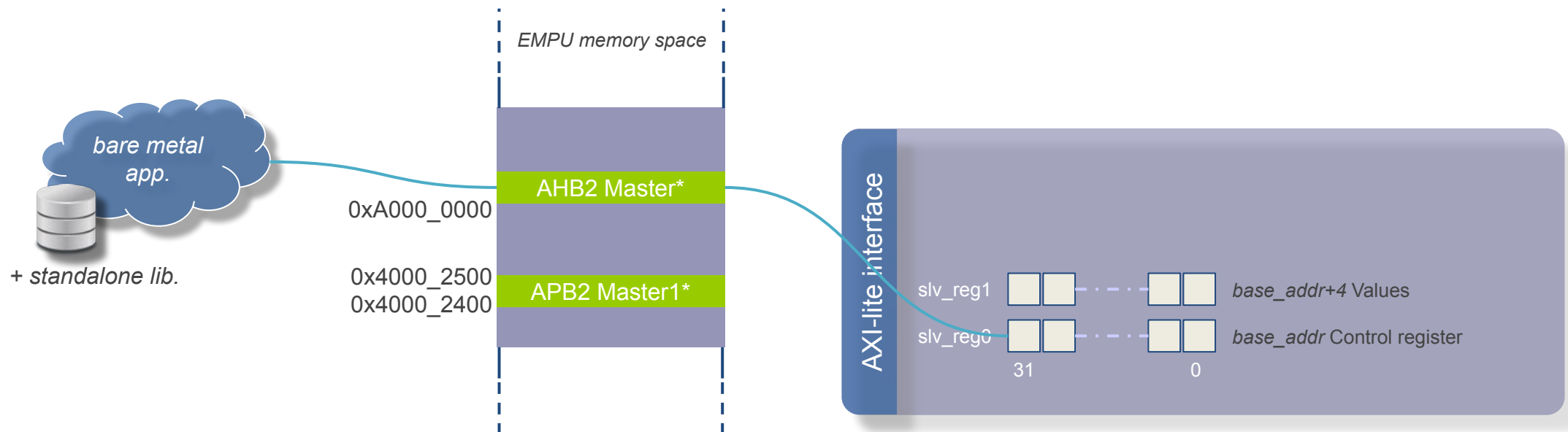- custom **Soft-IP** & EMPU as 7 segments driver :)
 - ❖ Write an AXI or APB module that will manage the 7 segments displays
AXI IP $\Rightarrow$ AHB to AXI bridge & EMPU IP block config
APB IP $\Rightarrow$ enable APB MasterX & EMPU IP block config
 - ❖ EMPU app. will write 32 bits values to a register
 - ❖ IP will provides control over the enabled/disabled digits and refresh frequency



* GoWIN EMPU Software Programming Reference Manual p.14



[Lab] Ministar 7-segment Soft-IP

● Resources

- ❖ GoWIN AHB to AXI
https://www.gowinsemi.com/en/support/ip_detail/118/
- ❖ Gowin_EMPU(GW1NS-4C) Software Programming
[nov.25] [SECIL] [Gowin_EMPU\(GW1NS-4C\)_V2.2.1.zip](#)
- ❖ System Verilog Quick Ref. Sheet
https://courses.cs.washington.edu/courses/cse371/24sp/verilog/Verilog_CheatSheet.pdf
- ❖ GoWIN Ministar github
<https://github.com/magicjellybeanfpga/MiniStar>
- ❖ [TBC] Simulation using Icarus verilog (iverilog) + GTKwave

GoWIN resources@secil server <https://secil.univ-tlse3.fr/teaching/francois/UE-SSM/GoWIN/>

Part IIa - [Advanced] Xilinx Zynq architecture

- Zynq architecture overview,
- AXI bus,
- Hands-on lab: my first soft IP,
- Next lab: RISC-V integration ?



- RISC-V @ Zynq

PicoRV32 - a size optimized RISC-V
<https://github.com/YosysHQ/picorv32>

Part III - Electronics for dummies all :)


- Basics,
- CMOS transistors,
- Bipolar transistors,
- Sink / Source output modes,
- Operational Amplifier,
- Motors,
- Wavelengths,
- KiCad PCB software.

<https://www.electronics-tutorials.ws/>


<https://doc.lagout.org/electronics/Electronics%20for%20Dummies%20%282005%29.pdf>

Ohm's law and friends

Resistors

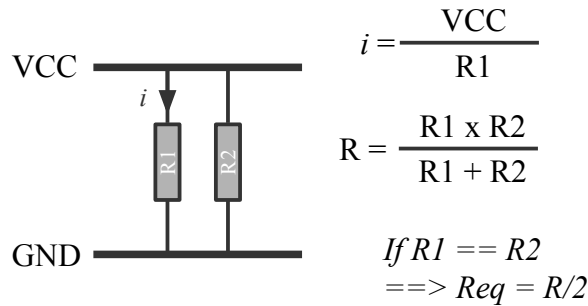

R-based adaptation levels

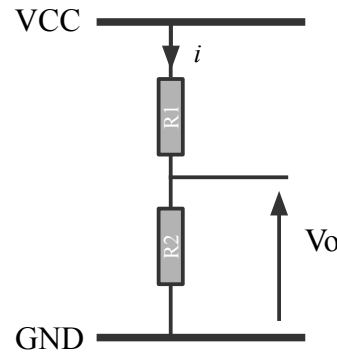


Q



Arduino features $VCC = 5v$ but we need to drive a 3.3v input of a Raspberry Pi

- Compute $R1$ and $R2$ values
- If $R1 == R2$, compute Vo

Capacitors

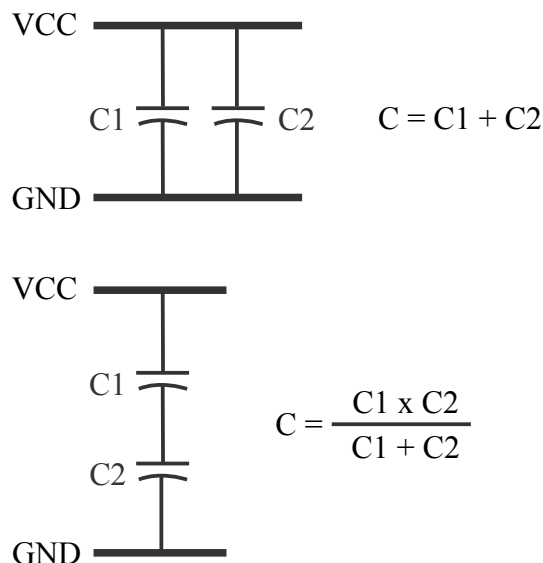

RC time constant

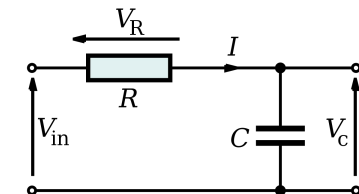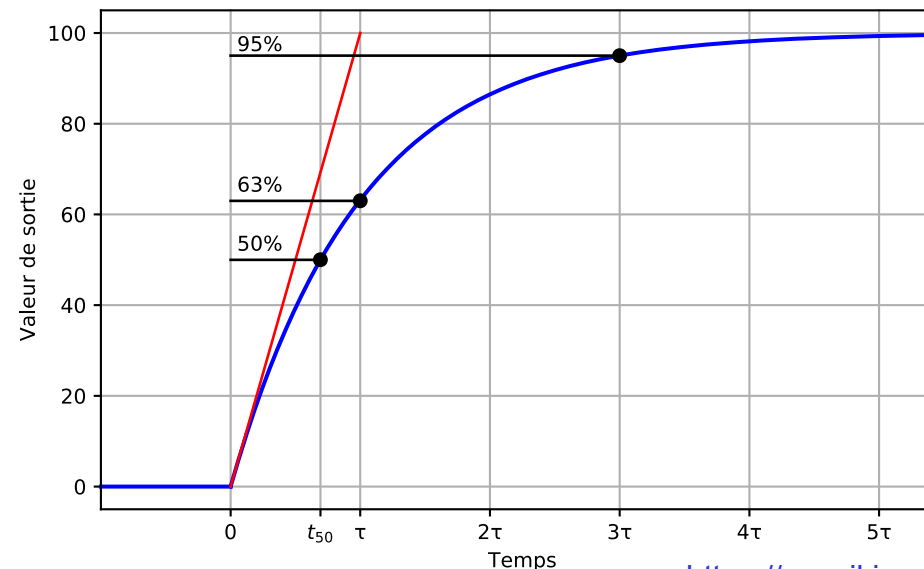


$$\tau = RC$$


https://en.wikipedia.org/wiki/RC_time_constant

Ohm's law and friends

Diodes ... almost unidirectional devices

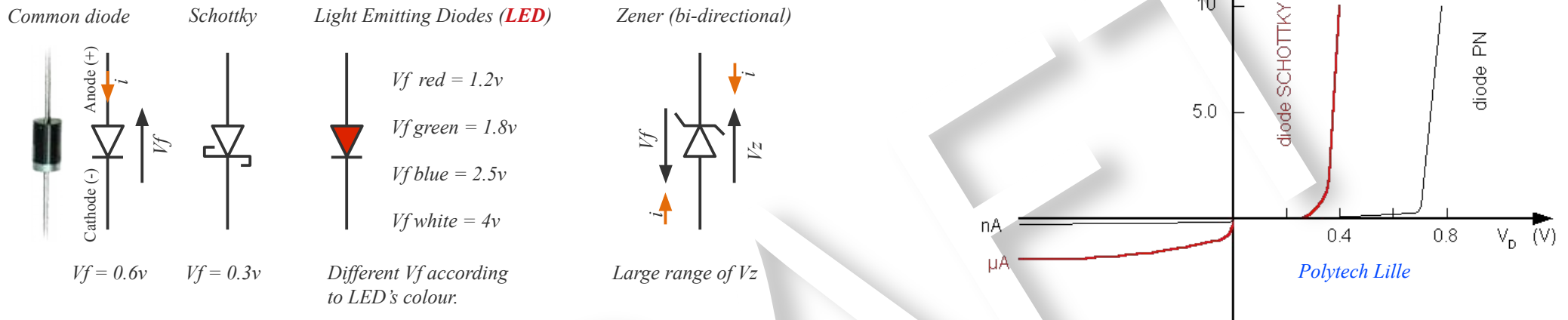


Bridge rectifier

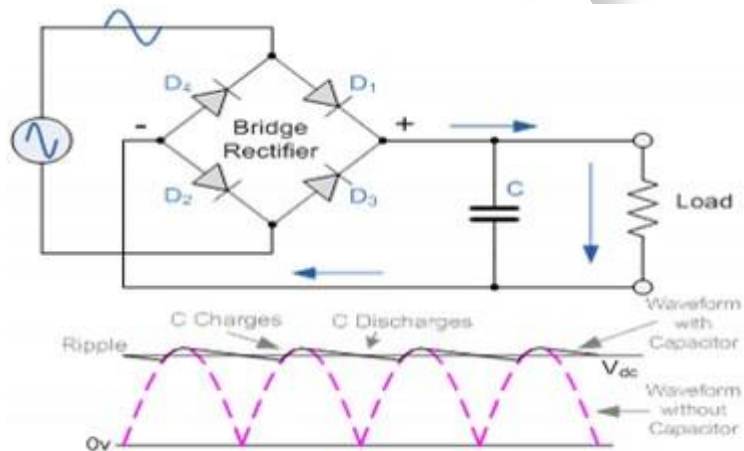

Self

CMOS transistors


- **Voltage** commanded transistors

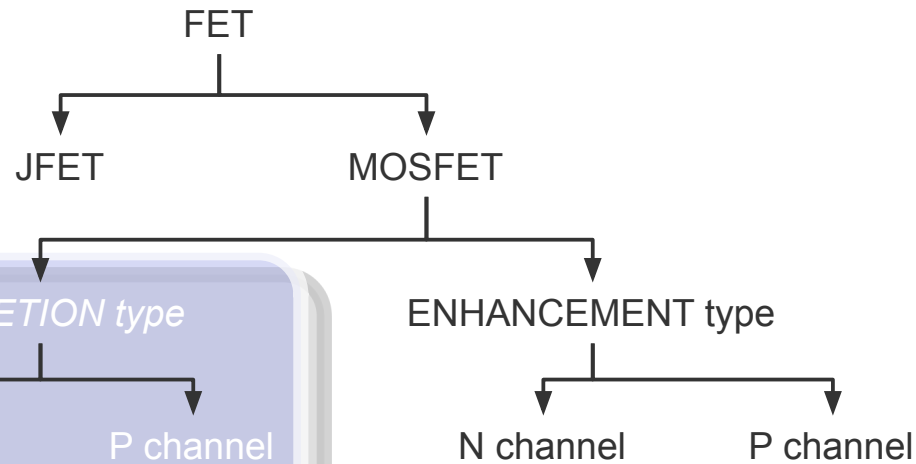

$V_{gs} = 0V \rightarrow$ Transistor ON


$V_{gs} > V_{gs\ threshold} \rightarrow$ Transistor ON

- Common symbols

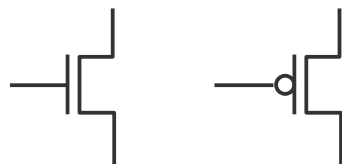

Nmos


Pmos

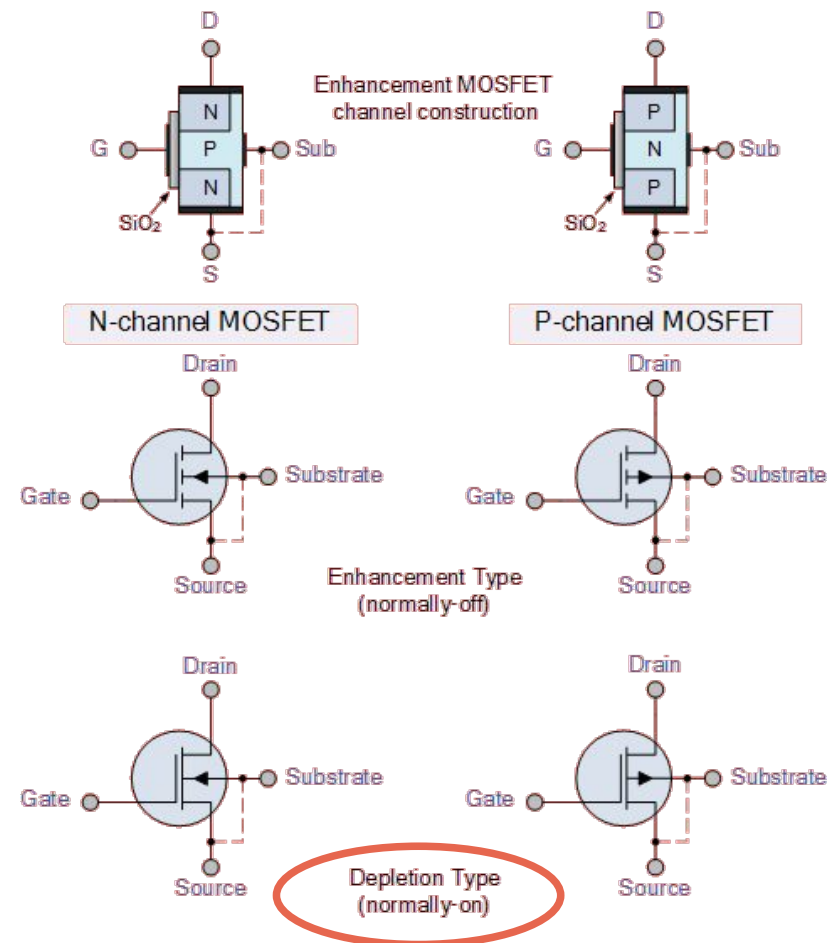

http://www.electronics-tutorials.ws/transistor/tran_1.html

CMOS transistors

- Example: motor driver

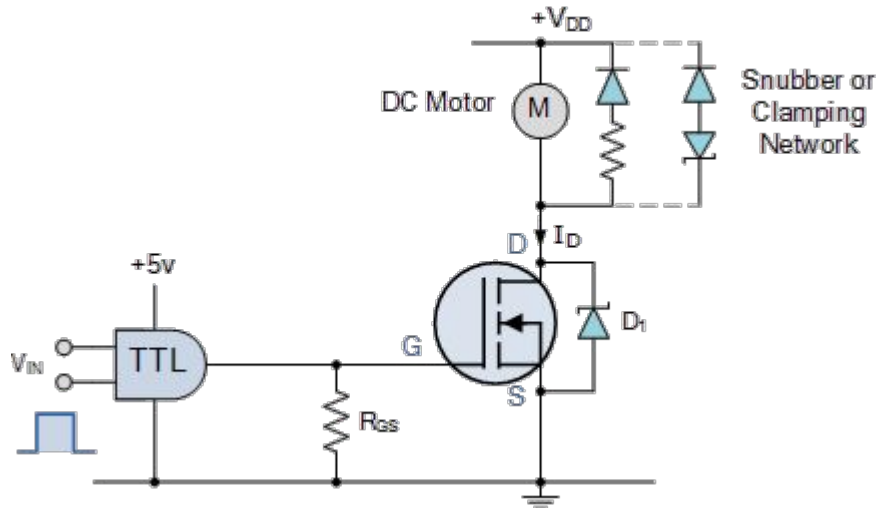


Considering a NMOS enhanced **2N7002** transistor:
(see datasheet link below)

Q


- Which applied Gate voltage will turn ON the actuator ?
- What R_{GS} resistor is useful for ?

http://www.electronics-tutorials.ws/transistor/tran_7.html

- Example: P-MOS driver

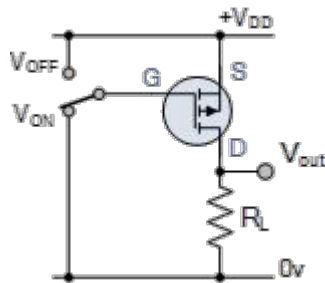

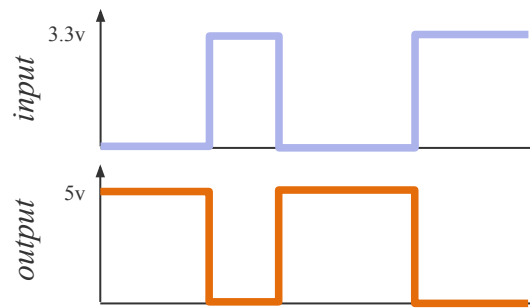- Your first electronic schematic: *Draw a signal inverter*





- 2N7002 datasheets

http://m2siame.univ-tlse3.fr/teaching/francois/NMOS-transistor_2N7002.pdf

... and what about a NAND gate ?

Bipolar transistors

- **Current** commanded transistors

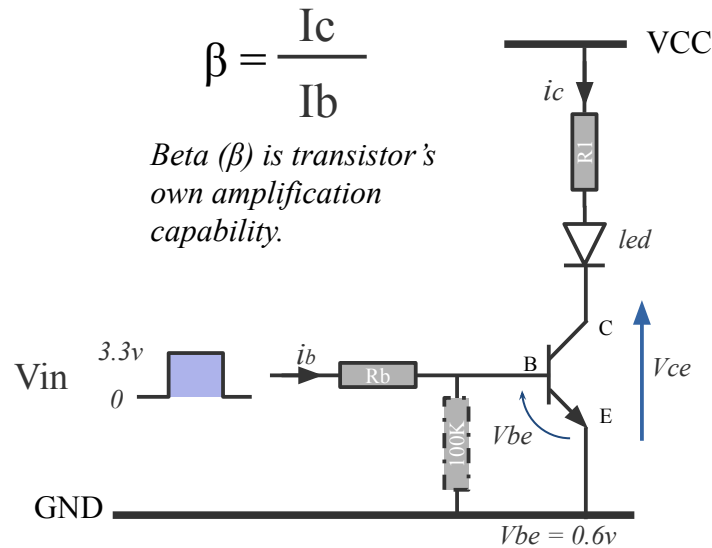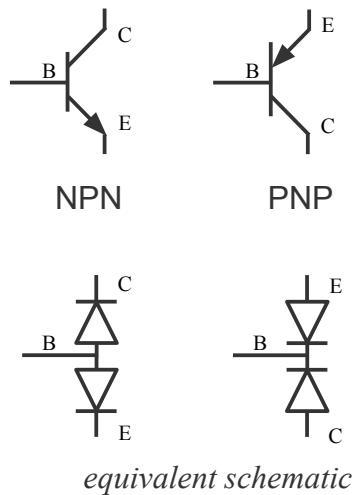

$$\beta = \frac{I_c}{I_b}$$

Beta (β) is transistor's own amplification capability.

Q

Considering a NPN BC547 transistor with $V_{fled} = 1.2v$, $i_c = 20mA$

- Compute R_l and R_b values

- Your own schematic to drive a led considering:

$V_{in}=0v \rightarrow led\ ON$

$V_{in}=V_{CC} \rightarrow led\ OFF$

[addon] What happens if $V_{CC} > V_{in}$?


- NPN BC547 datasheet

http://m2siame.univ-tlse3.fr/teaching/francois/NPN-transistor_BC547-BC550.pdf

http://www.electronics-tutorials.ws/transistor/tran_1.html


Sink or Source ??

- Totem-pole (*push-pull*) output

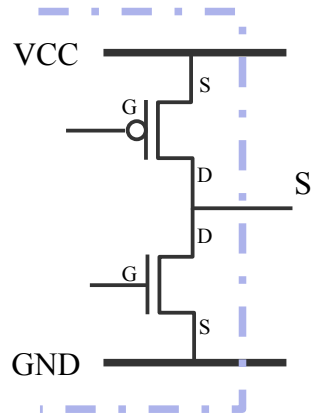


Note: same design with bipolar transistors

- Open-Drain / Open-Collector output

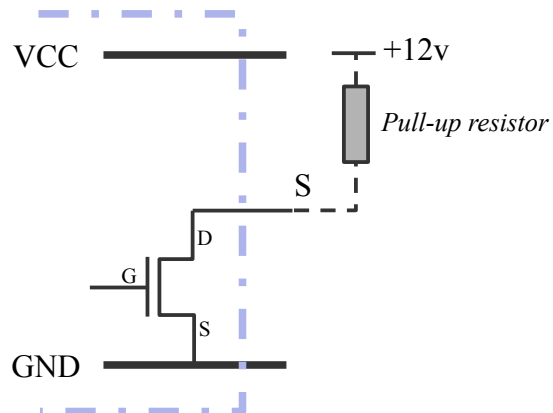


Note: same design with bipolar transistors

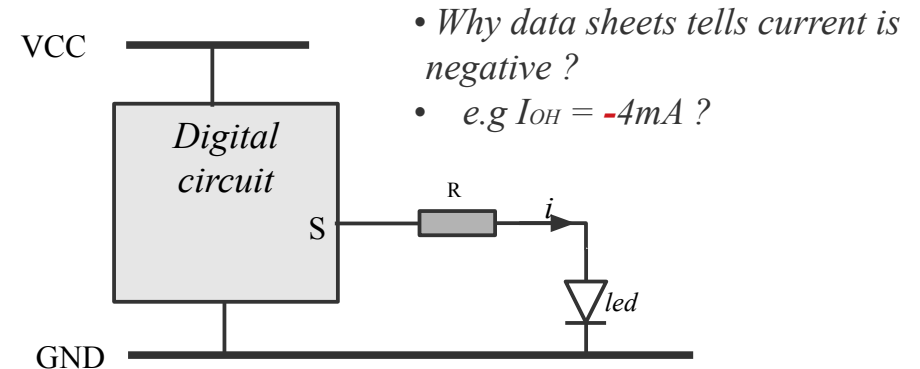- Source mode: Output *provides* power to the connected devices




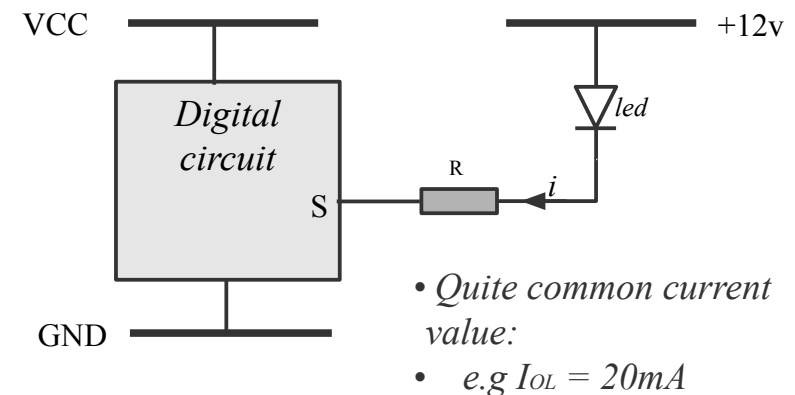- Sink mode: Output *absorbs* current from connected devices




Voltage thresholds

● Application to the I2C bus

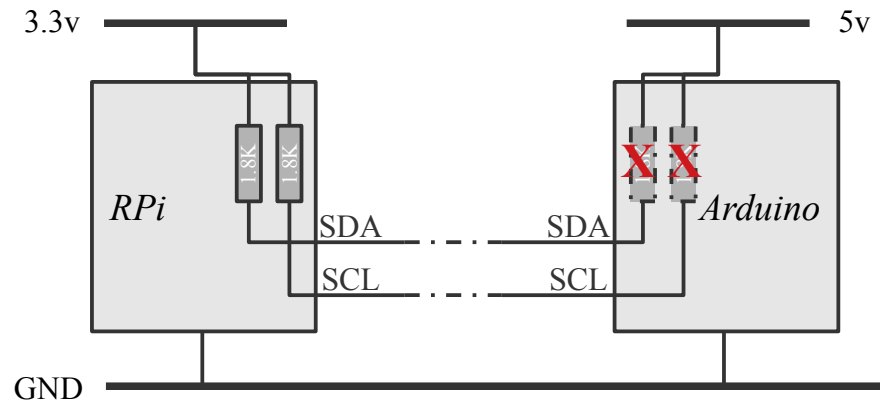

Remember: RPi's GPIO are 3.3v ONLY !!

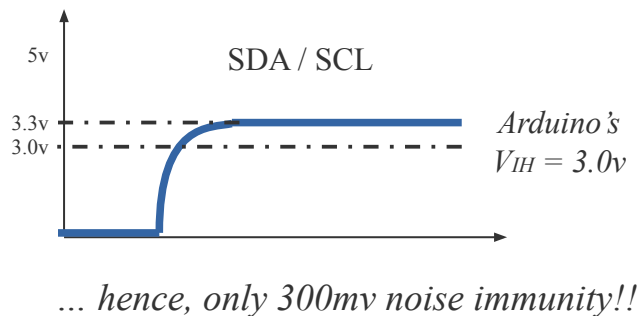


Q

I2C bus master: Raspberry Pi is 3.3v powered


I2C bus slave: Arduino is 5v powered

- *Why Arduino and RPi are able to communicate ?*
- *What happens if you don't remove Arduino's pull-up resistors ?*

● I2C level shifter

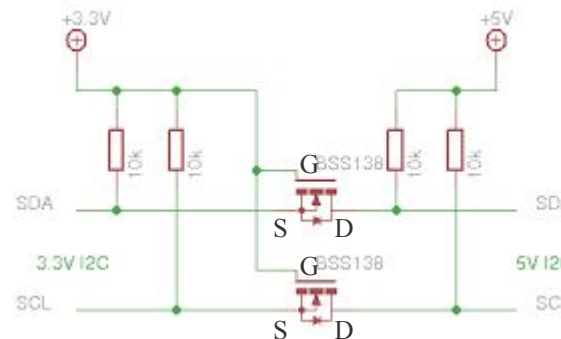


RPi side

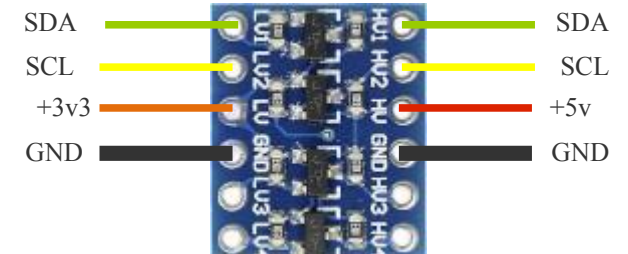

Operational Amplifier

- Comparator

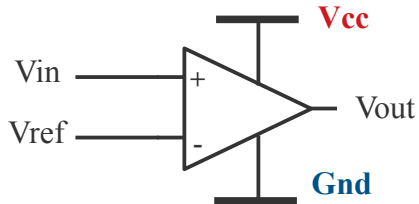


$$V_{out} = A_o (V_{+} - V_{-})$$

Note: A_o is open-loop gain

If $V_{in} > V_{ref}$ then
 $V_{out} = V_{CC}$
Else
 $V_{out} = GND$
Endif

- Follower (impedance adaptation level)

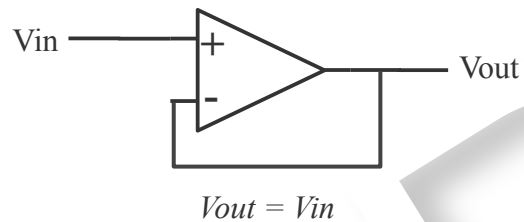

$$V_{out} = V_{in}$$

- Amplifier ...



Motors

- Servomotor

- H bridge

- Step-motor

- Brushless motor

DRAFT

Wavelengths

Antenna lengths calculation

$$\lambda = \frac{C}{f}$$

$$f = \frac{1}{T}$$

frequency (Hz) period (second)

Speeds

$$C = 300.000 \text{ km/s}$$




$$V = 280.000^* \text{ km/s}$$

cooper wire

e.g @ 1GHz $\lambda = 28\text{cm}$


**Electric field propagation in a 12AWG wire. Speed goes from 50 to 99% of C depending on velocity drift.
In a 14AWG → 97% of C*

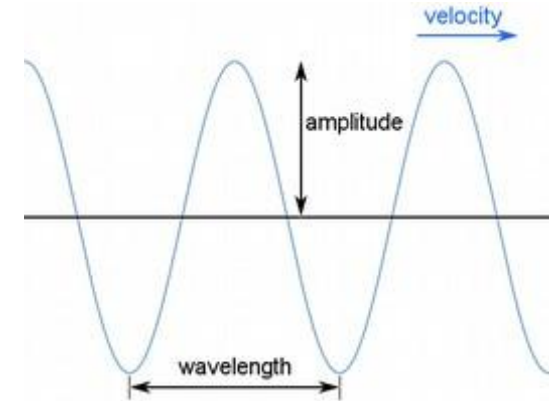λ (wavelength) represents the distance over which the wave's shape repeat.
(Wikipedia)





$\lambda / 4$ wire antenna:

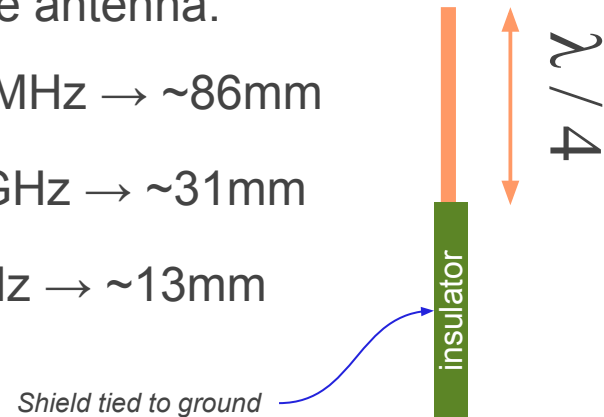- @868MHz → ~86mm
- @2.4GHz → ~31mm
- @6GHz → ~13mm




KiCad

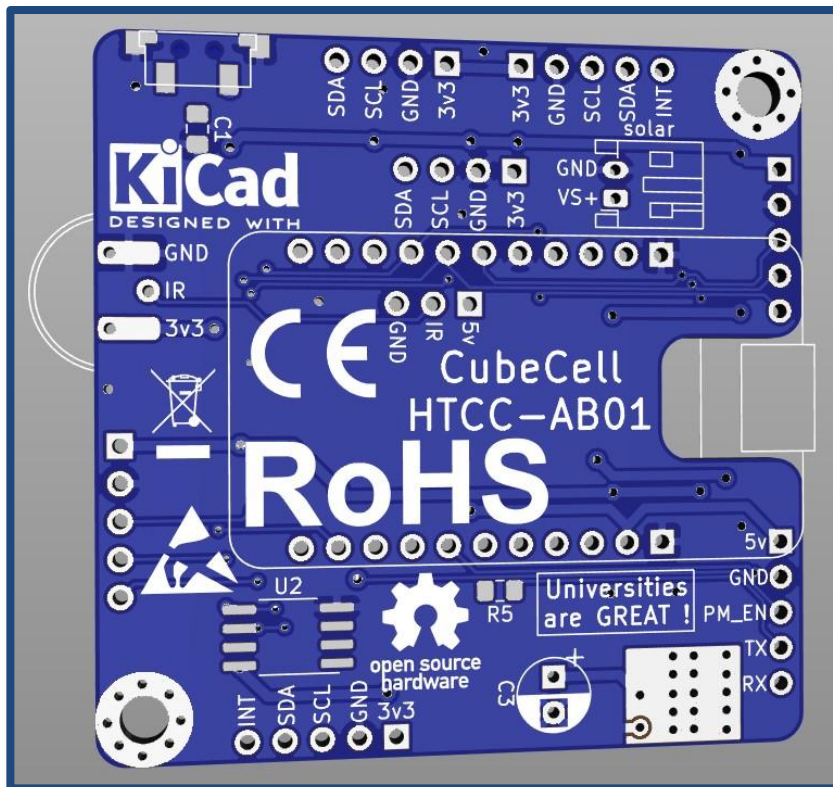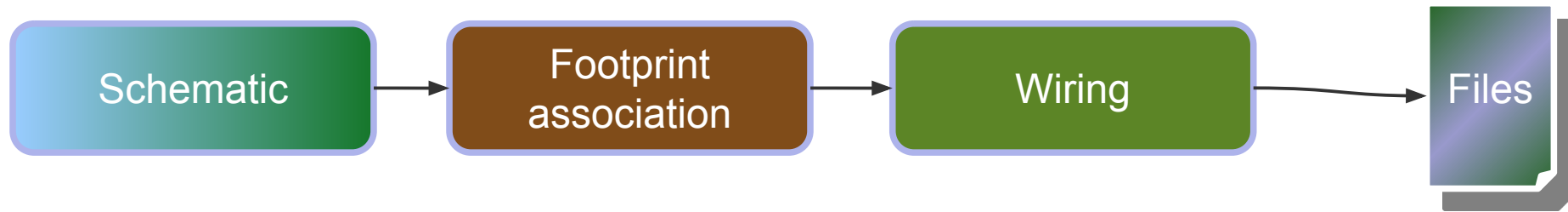- Creating your own **PCB** ... welcome to the master level !



Gerber files
(pads, wires ...)

Excellon files
(holes)

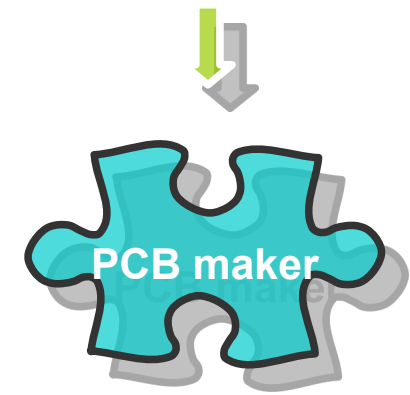



END

strong empathy for hardware

perseverance

some soldering sessions ;)

a bit of electronics

ghdl + gtkwave

secret ingredient*

linux



path to YOUR success in
the FPGA world !

**Po's father knows it!*